
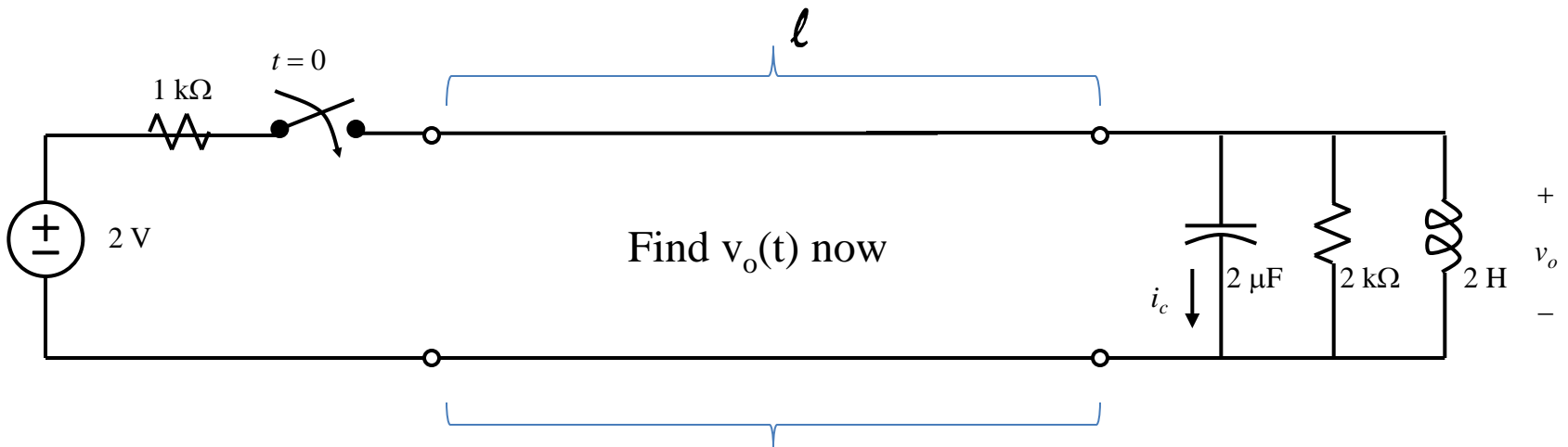


Transmission Lines

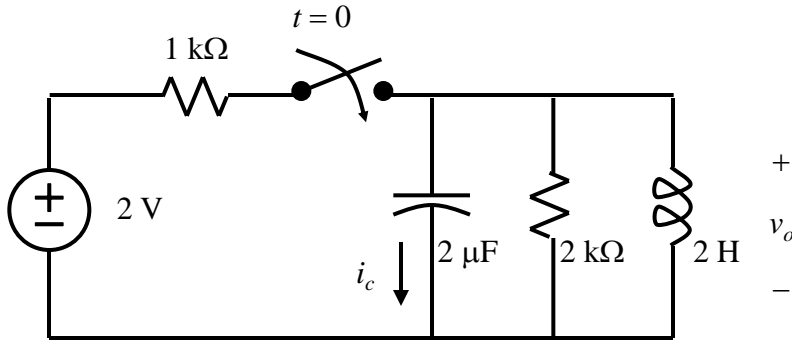



What if this is 25 km ???

It's a T-line if:

$$\frac{l}{\lambda} \sim \frac{fl}{c} \gtrsim 1\%$$




3 MHz ~ m's



3 GHz ~ mm's


One place where
E & M meets Circuits

Twisted Pair

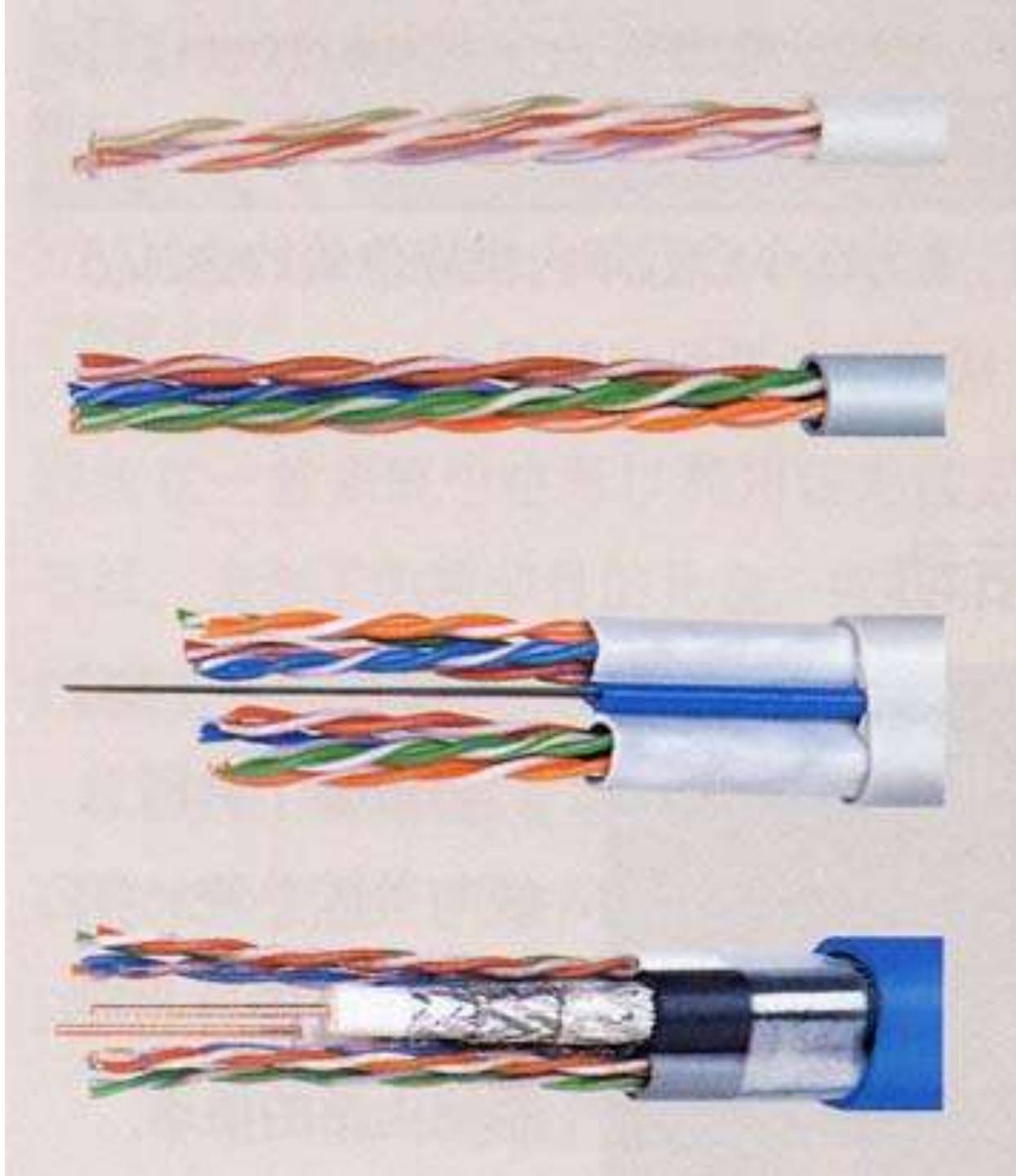

Coaxial (Co-Ax) Cable

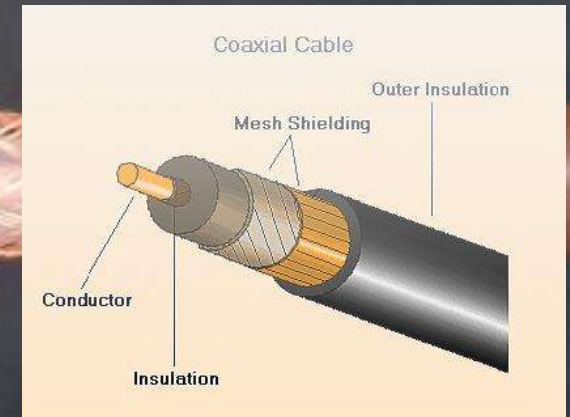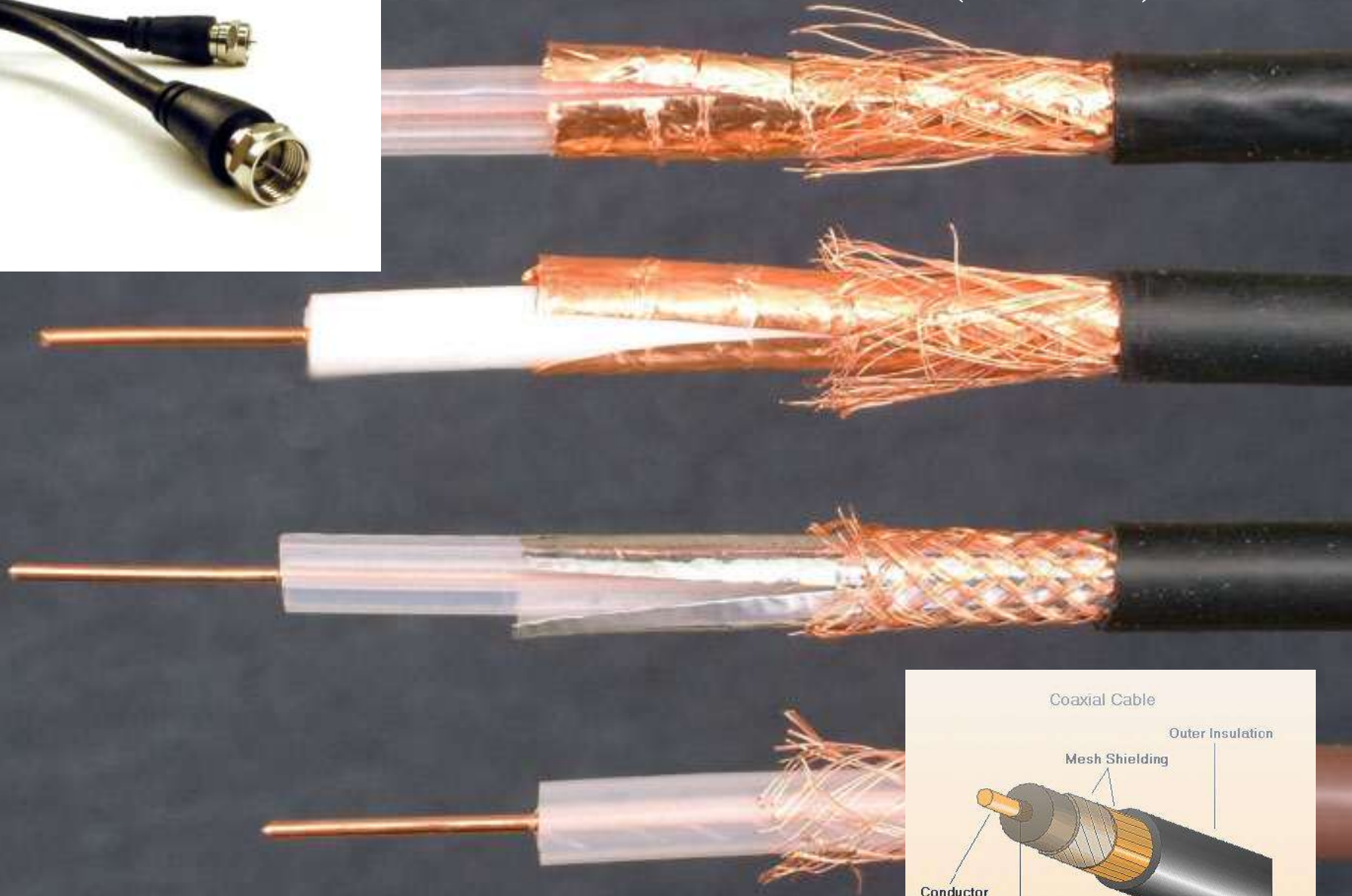

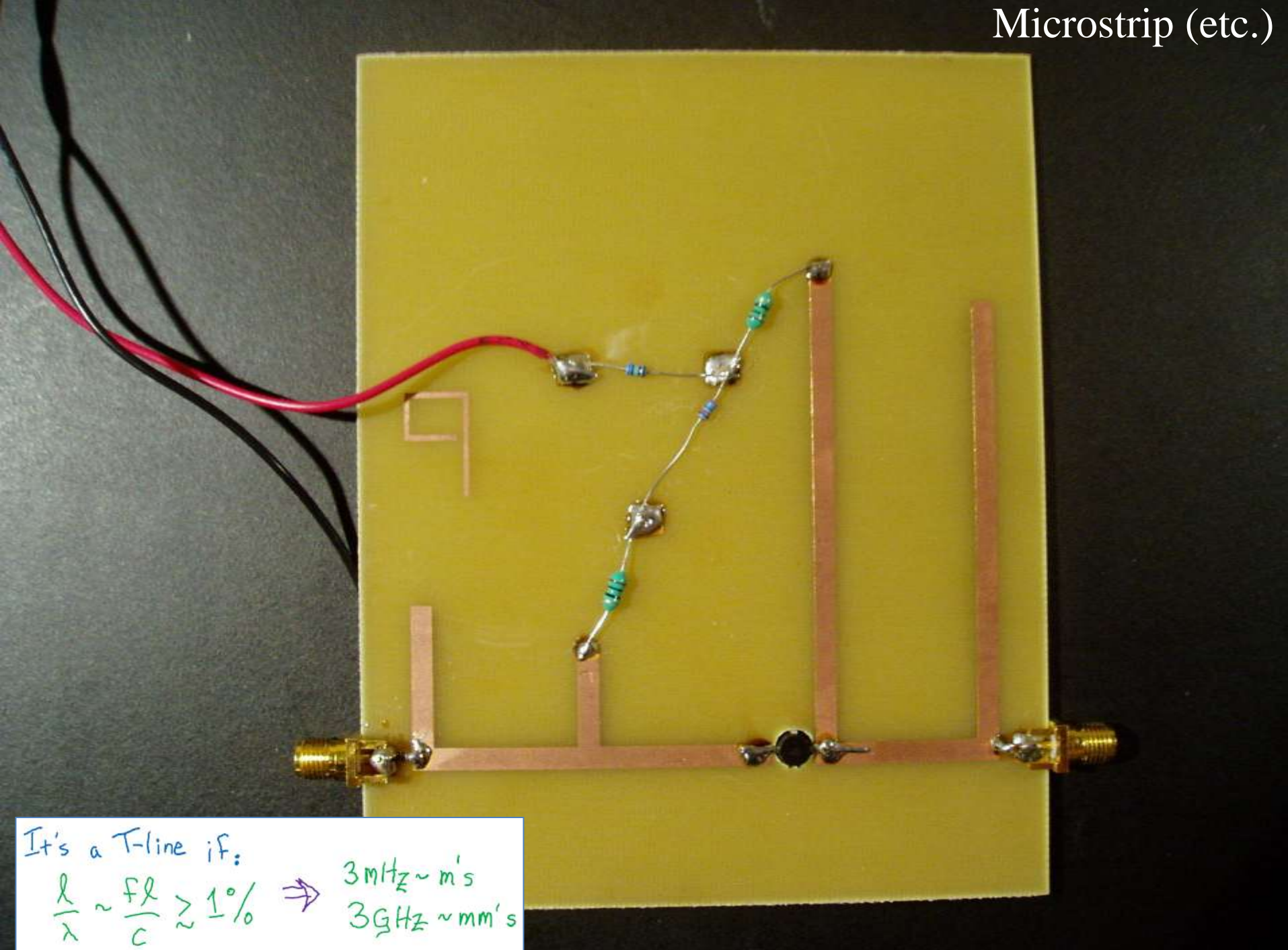

Waveguides



PRECISION TEST CABLES

now up to 40 GHz

Rugged, reliable, ready to ship, custom lengths on request!

High-quality data requires high-quality cables — and different models to meet different needs. Mini-Circuits Precision Test Cables have been designed with our 40 years of industry experience in mind, and tested beyond any others on the market. It's why we can back them with an unprecedented 6-month guarantee,* and customers can save time and money with fewer false rejects and less retesting.

Flex Test™ Our standard, triple-shielded CBL cables are so tough, we had to invent a new way to test them: Flex Test™. Even after more than 20,000 flex cycles, these cables deliver unimpaired performance from DC-18 GHz. Ideal for design labs or test benches, they're available in lengths up to 25 feet with SMA or N-type connectors.

Quick Lock For high-speed production efficiency and superior electrical & mechanical performance, our CBL cables are the answer. Just push them onto a standard female SMA connector and slide the collar forward to lock. You'll get proven high-integrity DC-18GHz connections, even after 20,000 flex and 20,000 mating cycles!

See minicircuits.com for cable lengths, specifications, performance data, and surprisingly low prices!

* Mini-Circuits will repair or replace your test cable at its option if the connector attachment fails within six months of shipment. This guarantee excludes cable or connector interface damage from misuse or abuse. K-Connector is a registered trademark of Aerflaw Company.

Mini-Circuits...we're redefining what VALUE is all about!

Mini-Circuits®
ISO 9001 ISO 14001 AS 9100


P.O. Box 350186, Brooklyn, New York 11235-0003 (718) 934-4000 Fax (718) 333-4661




The Design Engineers Search Engine finds the model you need. Instantly. For detailed performance specs & shipping online see minicircuits.com

IF/RF MICROWAVE COMPONENTS


401 rev B

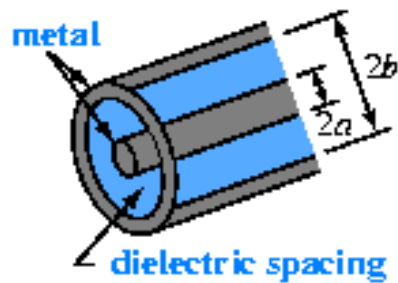


(a) Coaxial line

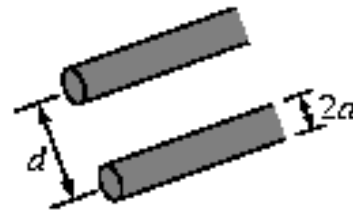


(b) Two-wire line

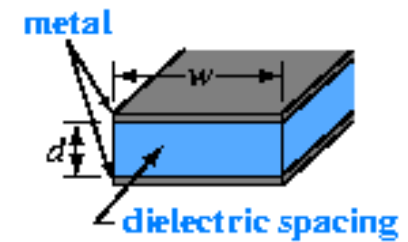

(c) Parallel-plate line

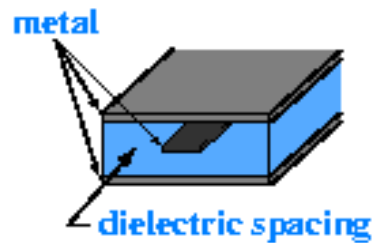


(d) Strip line

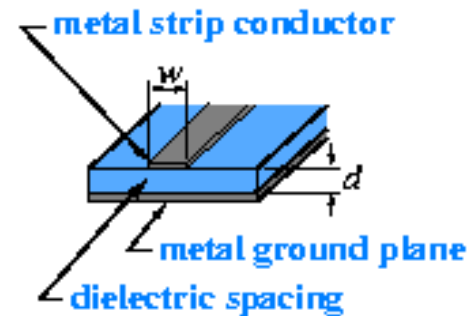


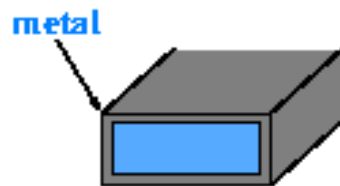(e) Microstrip line


Transverse Electro Magnetic \longrightarrow TEM Transmission Lines



(f) Rectangular waveguide

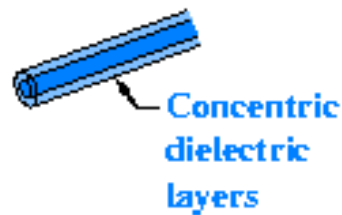


(g) Optical fiber

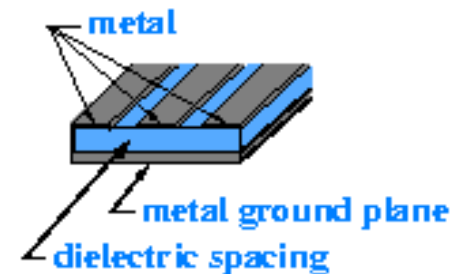


(h) Coplanar waveguide

Higher Order Transmission Lines

If it's AC, then can use *phasors* ...

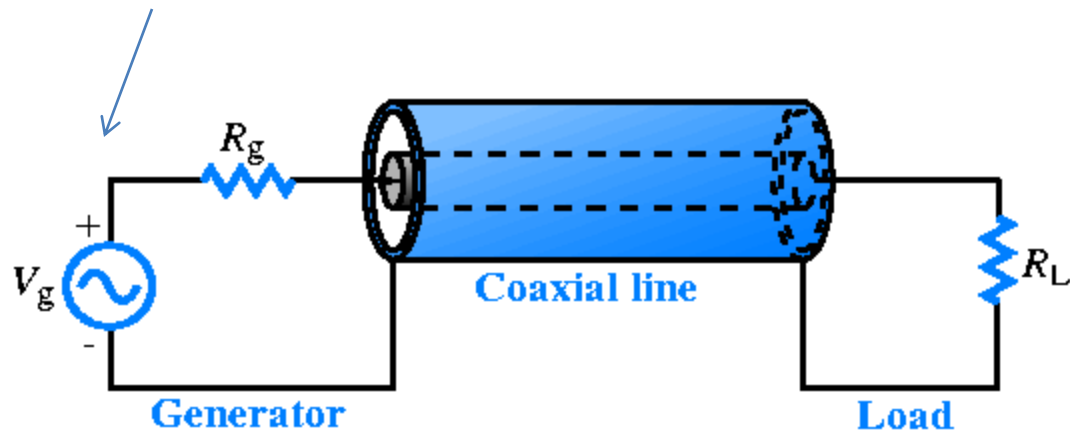


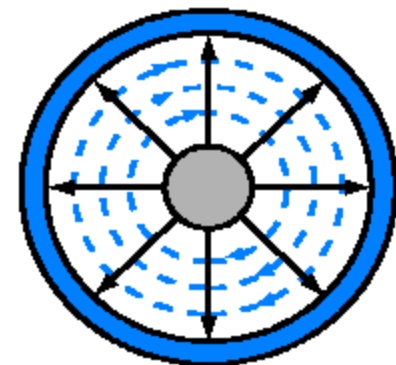--- Magnetic field lines
— Electric field lines



Cross section

Thévenin Equivalent



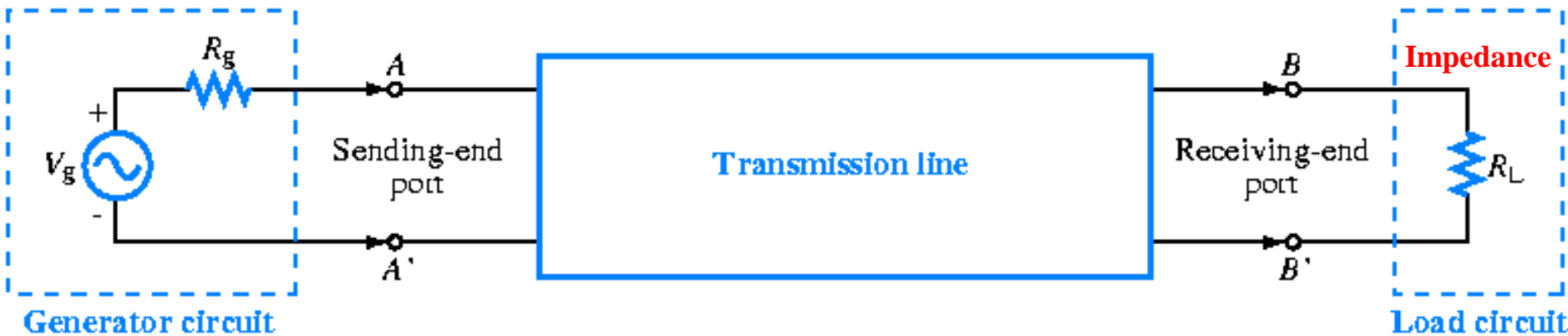


$V_{AA'} \neq V_{BB'}$
(phase delay)





In addition to phase delay,
T-lines exhibit power loss,
dispersion & reflections.

Kinda Like \sim or $\frac{1}{j}$ ☺

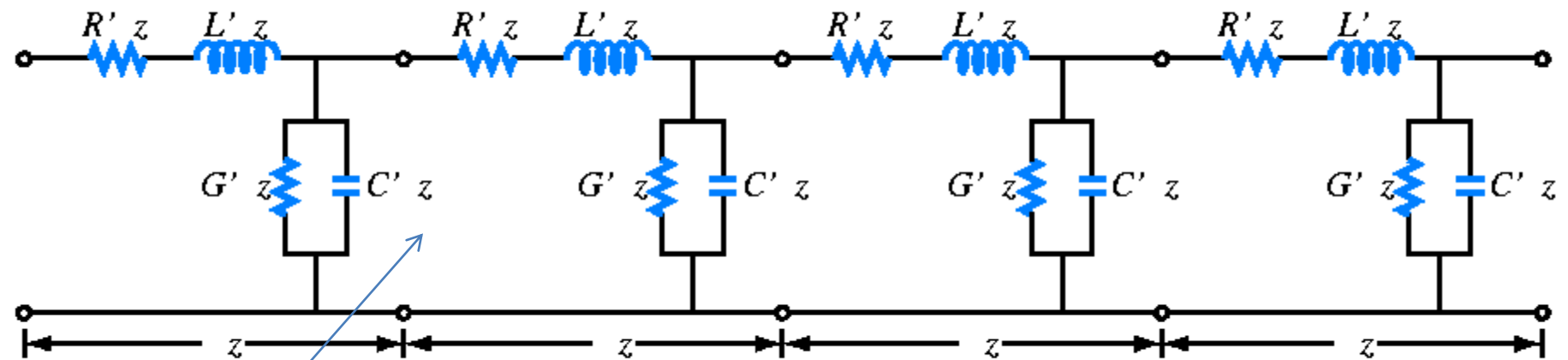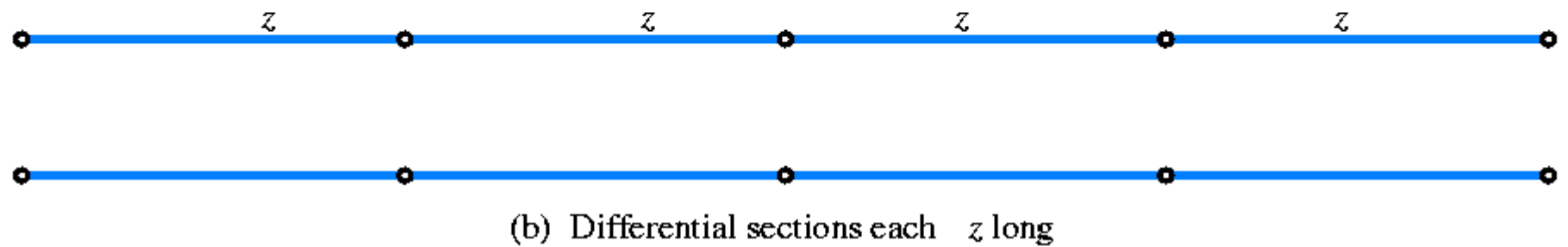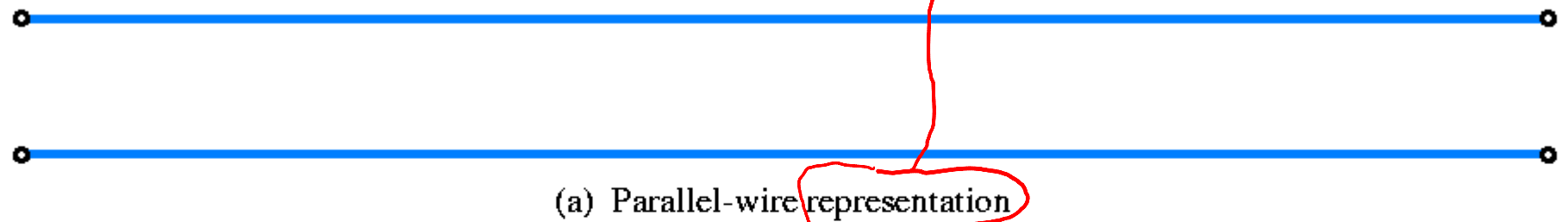


...kinda like Thévenin ☺

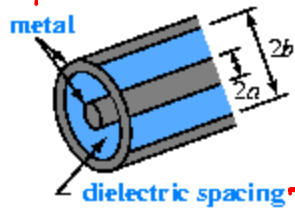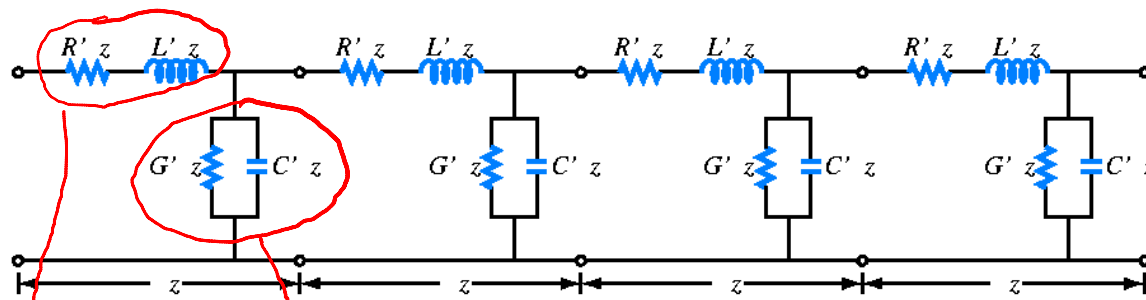
Note: not the only model, but the math is all the same



(a) Coaxial line

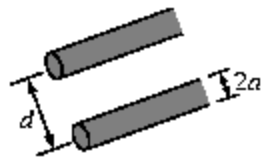

(b) Two-wire line

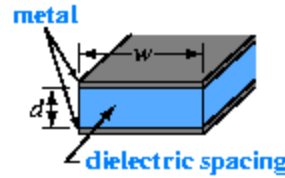

(c) Parallel-plate line

T-Line Parameters

$$\left. \begin{array}{l} R' \quad \Omega/\text{m} \\ L' \quad \text{H}/\text{m} \\ G' \quad \text{S}/\text{m} \\ C' \quad \text{F}/\text{m} \end{array} \right\} \text{Differential (per unit Length)}$$

| Parameter | Coaxial | Two Wire | Parallel Plate | Unit |
|-----------|---|---|------------------------|---------------------|
| R' | $\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$ | $\frac{R_s}{\pi a}$ | $\frac{2R_s}{w}$ | Ω/m |
| L' | $\frac{\mu}{2\pi} \ln(b/a)$ | $\frac{\mu}{\pi} \ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]$ | $\frac{\mu d}{w}$ | H/m |
| G' | $\frac{2\pi\sigma}{\ln(b/a)}$ | $\frac{\pi\sigma}{\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$ | $\frac{\sigma w}{d}$ | S/m |
| C' | $\frac{2\pi\epsilon}{\ln(b/a)}$ | $\frac{\pi\epsilon}{\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$ | $\frac{\epsilon w}{d}$ | F/m |

Notes: (1) Refer to Fig. 2-4 for definitions of dimensions. (2) μ, ϵ , and σ pertain to the insulating material between the conductors. (3) $R_s = \sqrt{\pi f \mu_c / \sigma_c}$. (4) μ_c and σ_c pertain to the conductors. (5) If $(d/2a)^2 \gg 1$, then $\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right] \simeq \ln(d/a)$.

- We can (and will) calculate these... (for now, plug & chug)
- ϵ, μ , and σ are measured, not derived...
- T-Line properties are frequency dependent!

Exercise 2.1 Use Table 2-1 to compute the line parameters of a two-wire air line whose wires are separated by a distance of 2 cm, and each is 1 mm in radius. The wires may be treated as perfect conductors with $\sigma_c = \infty$.

Solution: Two-wire air line: Because medium between wires is air, $\epsilon = \epsilon_0$, $\mu = \mu_0$ and $\sigma = 0$.

$$\epsilon_0 \cong 8.85 \times 10^{-12} \frac{\text{F}}{\text{m}}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$d = 2 \text{ cm}, \quad a = 1 \text{ mm}, \quad \sigma_c = \infty$$


$$R_s = \left[\frac{\pi f \mu_c}{\sigma_c} \right]^{1/2} = 0$$

$$R' = 0$$

$$\begin{aligned} L' &= \frac{\mu_0}{\pi} \ln \left[\left(\frac{d}{2a} \right) + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right] \\ &= \left(\frac{4\pi \times 10^{-7}}{\pi} \right) \ln \left[\left(\frac{20}{2} \right) + \sqrt{\left(\frac{20}{2} \right)^2 - 1} \right] \\ &= 4 \times 10^{-7} \ln[10 + \sqrt{99}] = 1.2 \text{ } (\mu\text{H/m}). \end{aligned}$$

$$G' = 0 \quad \text{because } \sigma = 0$$



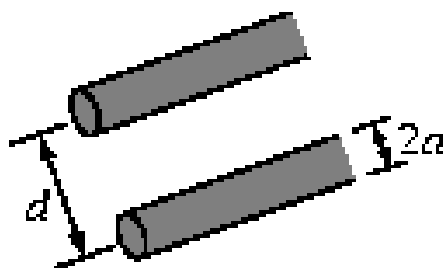
$$C' = \frac{\pi \epsilon_0}{\ln \left[\left(\frac{d}{2a} \right) + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right]} = \frac{\pi \times 8.85 \times 10^{-12}}{\ln[10 + \sqrt{99}]} = 9.29 \text{ (pF/m)}.$$



Power Loss




Dispersion*

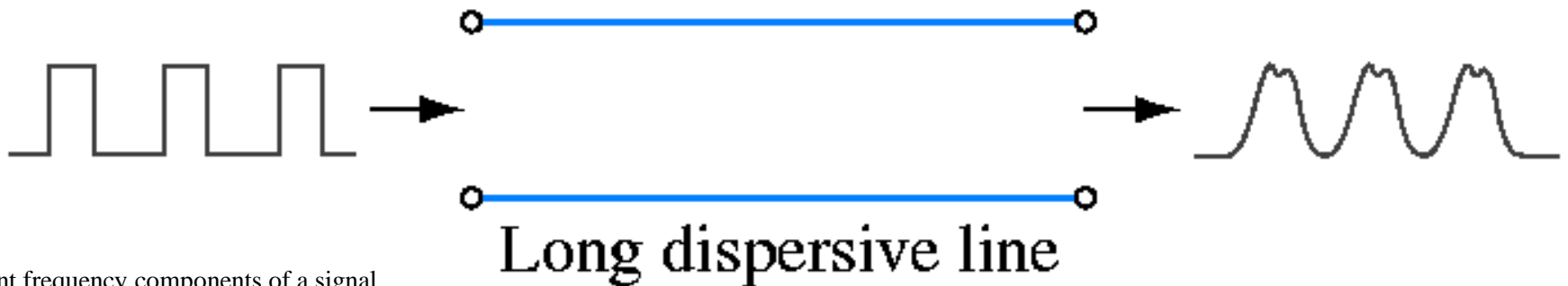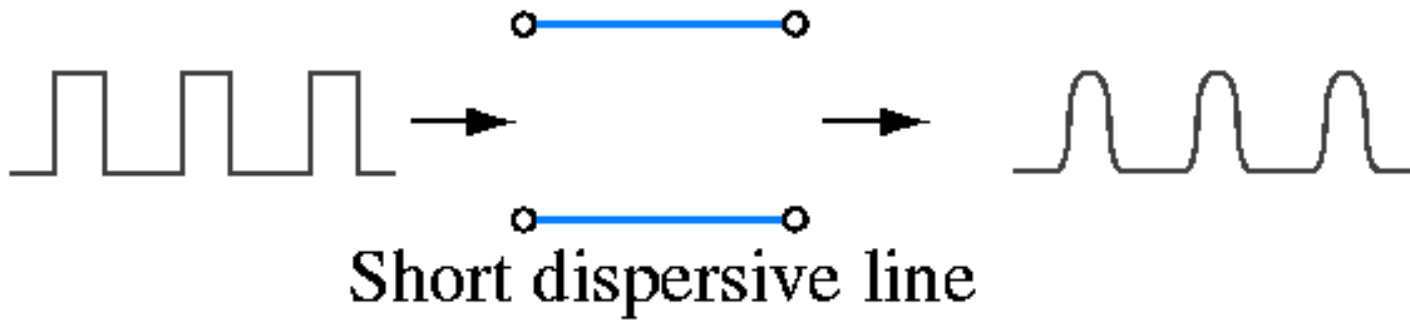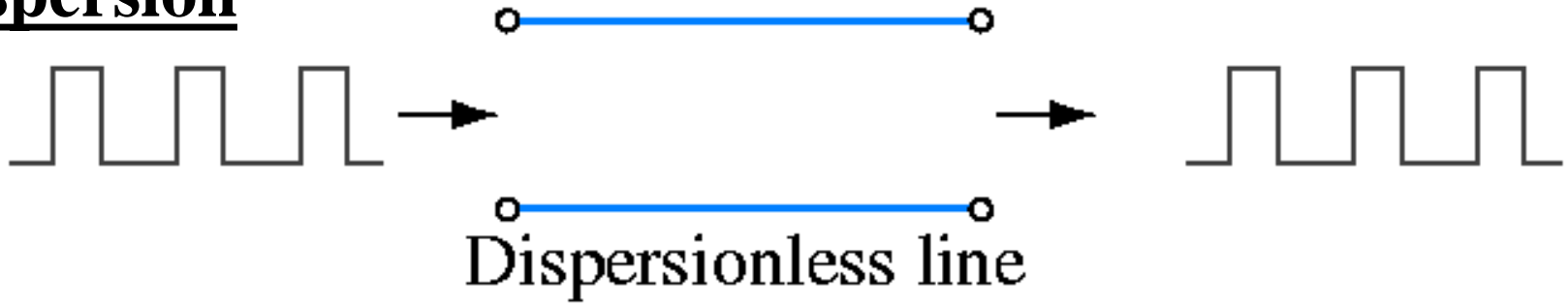


* Different frequency components of a signal travel at different speeds and undergo different attenuations as they travel down the line

Hmmm... it's not AC, so how can we use phasors ???

Reflection

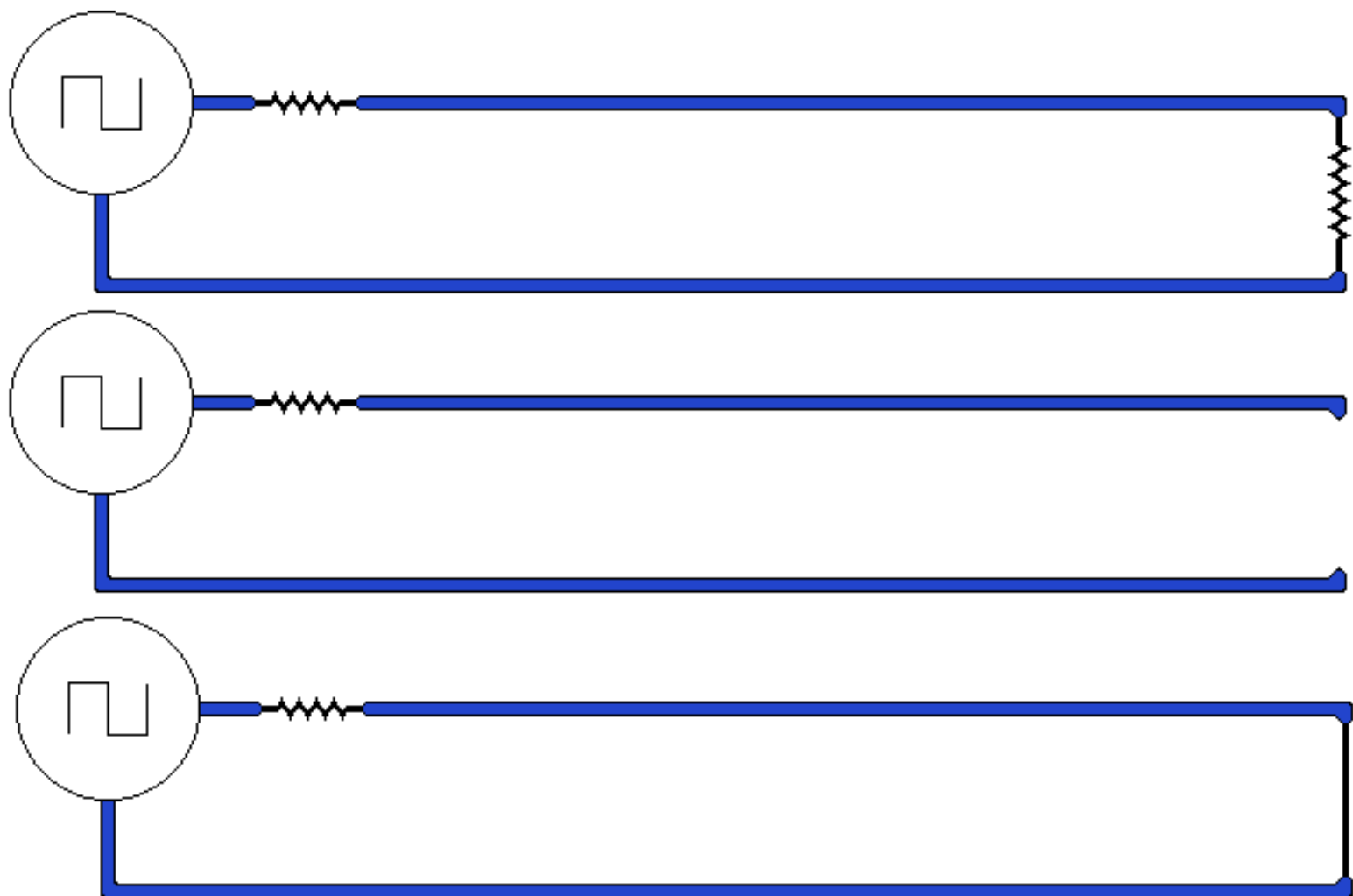

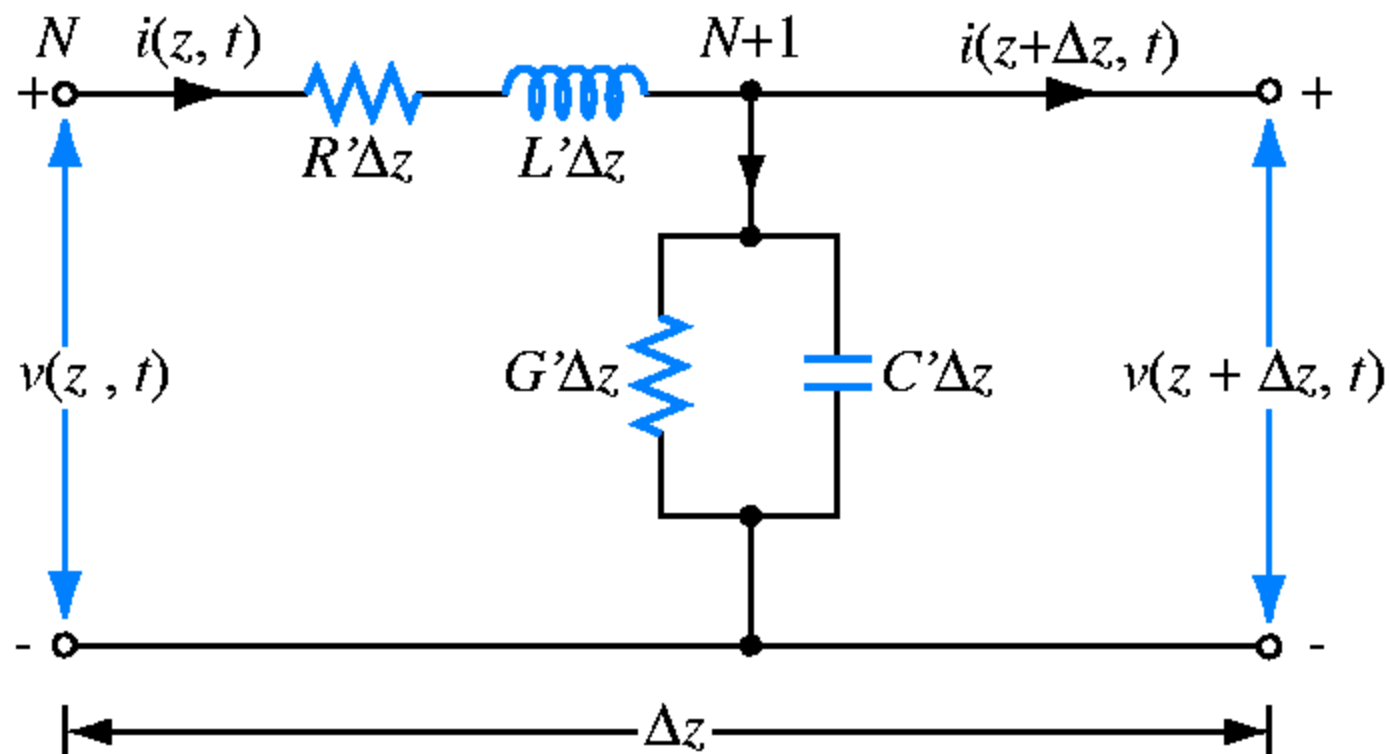


**Lloyd Espenschied and
Herman A. Affel*, [ca. 1949]**






* Filed 1st patent for coaxial cable [1929]




- Transmission lines transmit energy and signals from a source (generator) to a load
- Distinguishing characteristics of a transmission line:
 - the devices to be connected are separated by distances comparable to or larger than the signal wavelength
 - the parameters of the circuit are distributed and are evaluated on a per-unit length basis:
 - R' – resistance per unit length, Ω/m
 - L' – inductance per unit length, H/m
 - G' – conductance per unit length, S/m
 - C' – capacitance per unit length, F/m
 - transmission lines are circuit elements that have complex impedances, which are functions of line length and signal frequency

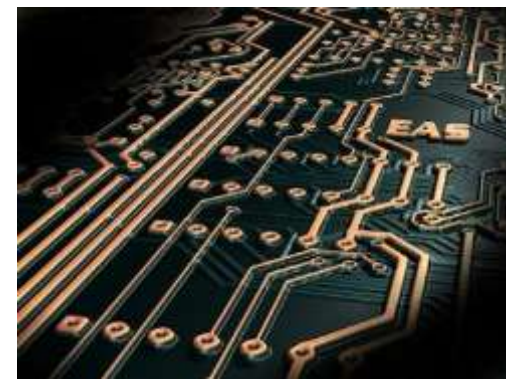

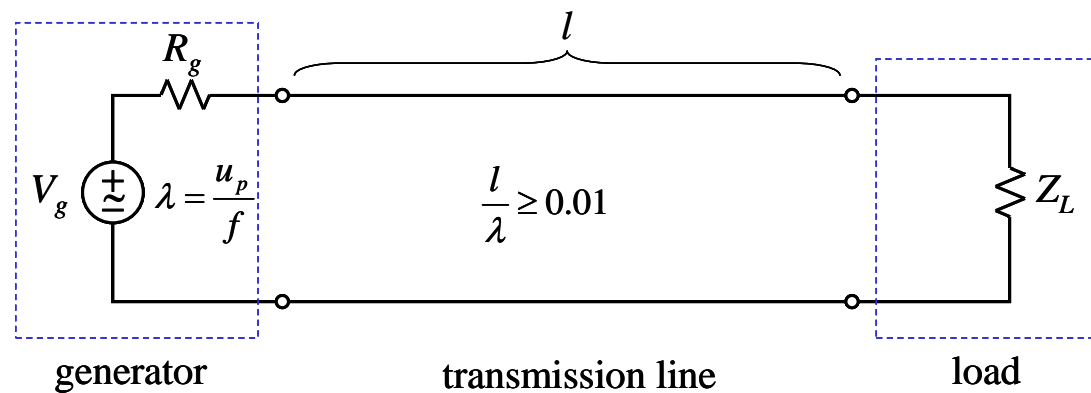- TEM transmission lines
 - two-wire line
 - coaxial cable
 - parallel-plate line




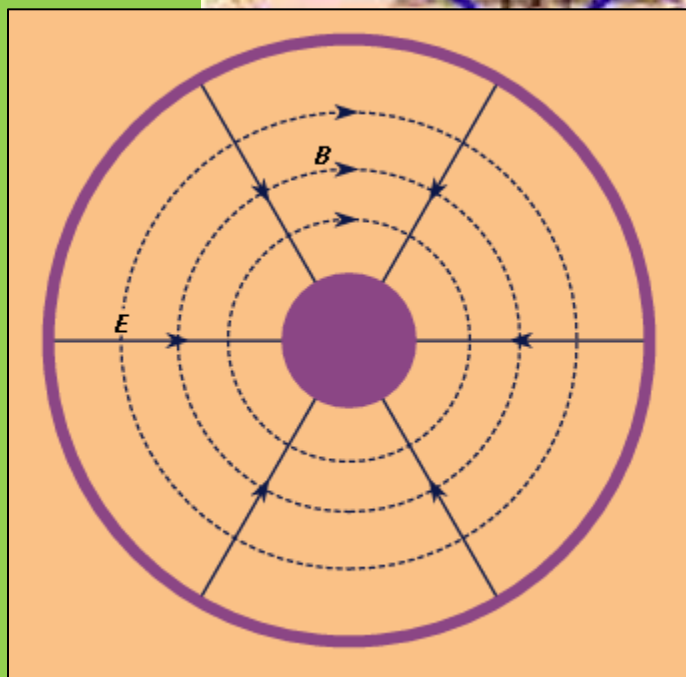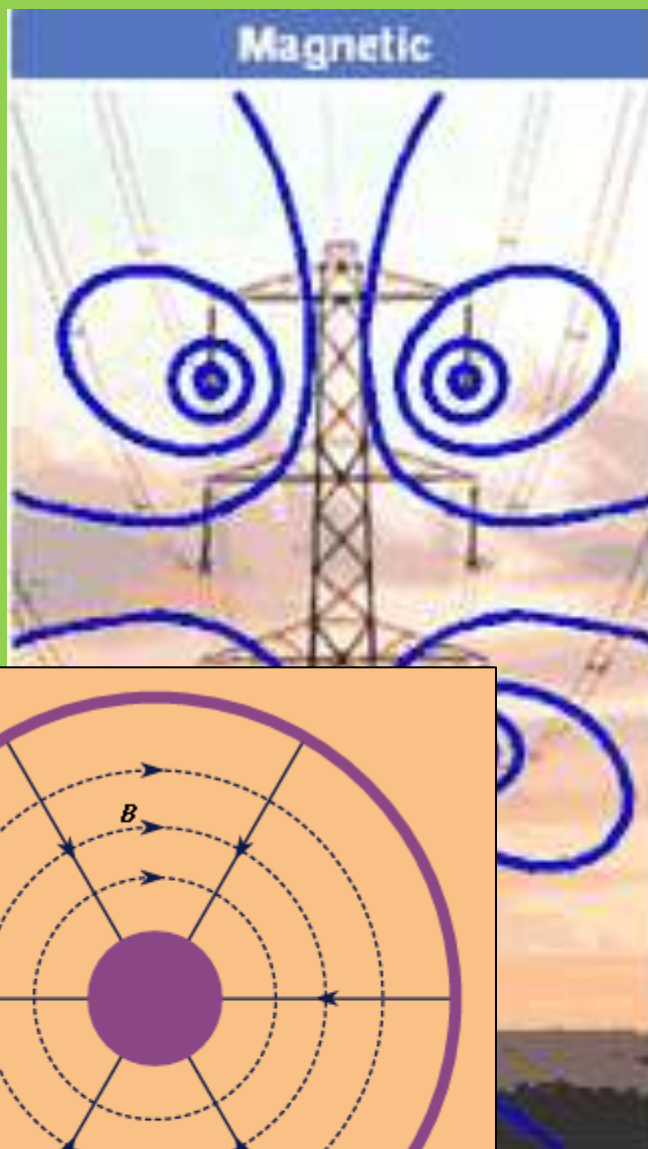

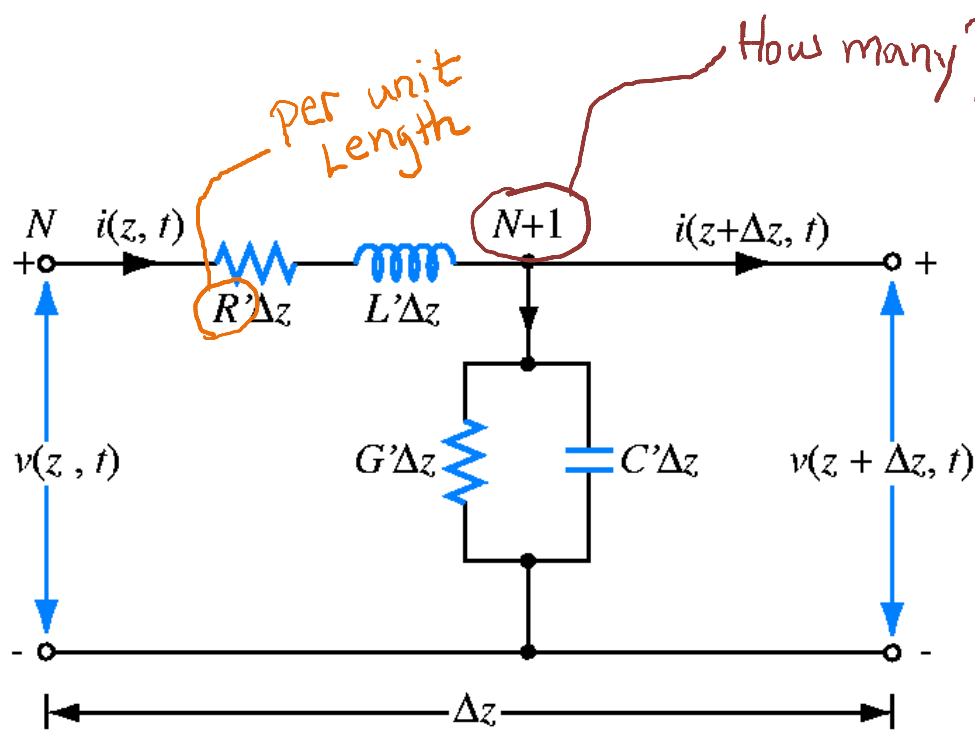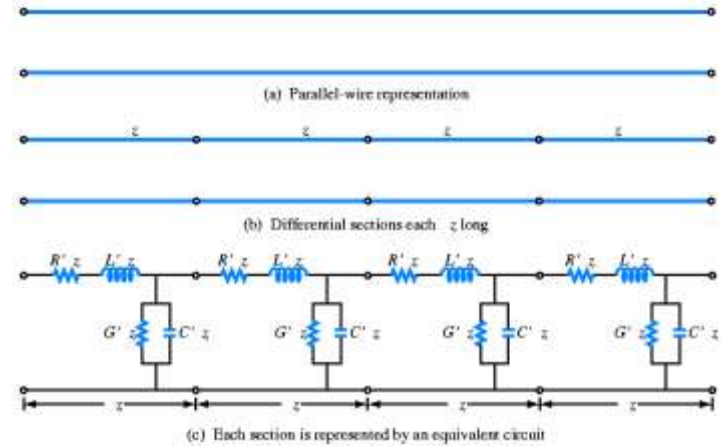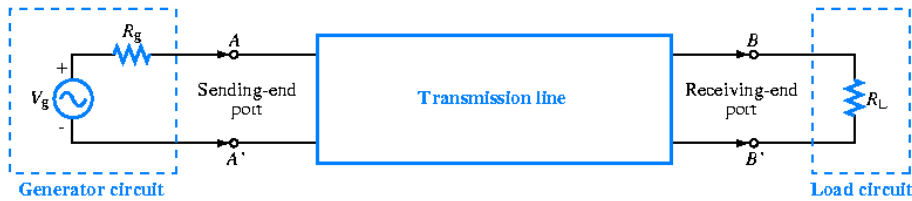


How many? What if T-Line is 1m Long?

Why NOT?

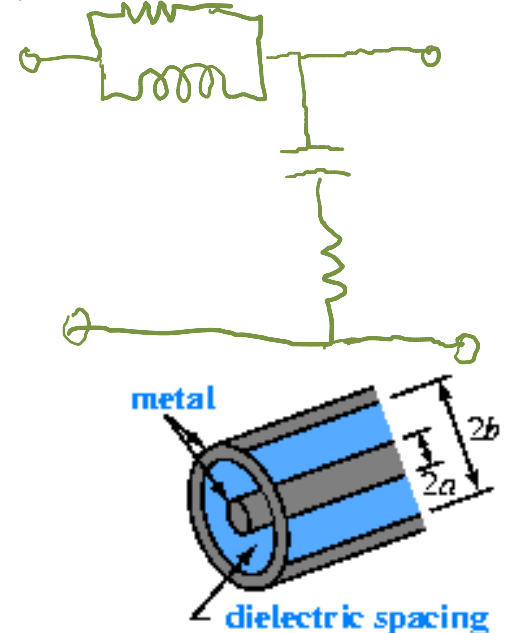


Kirchoff Time!

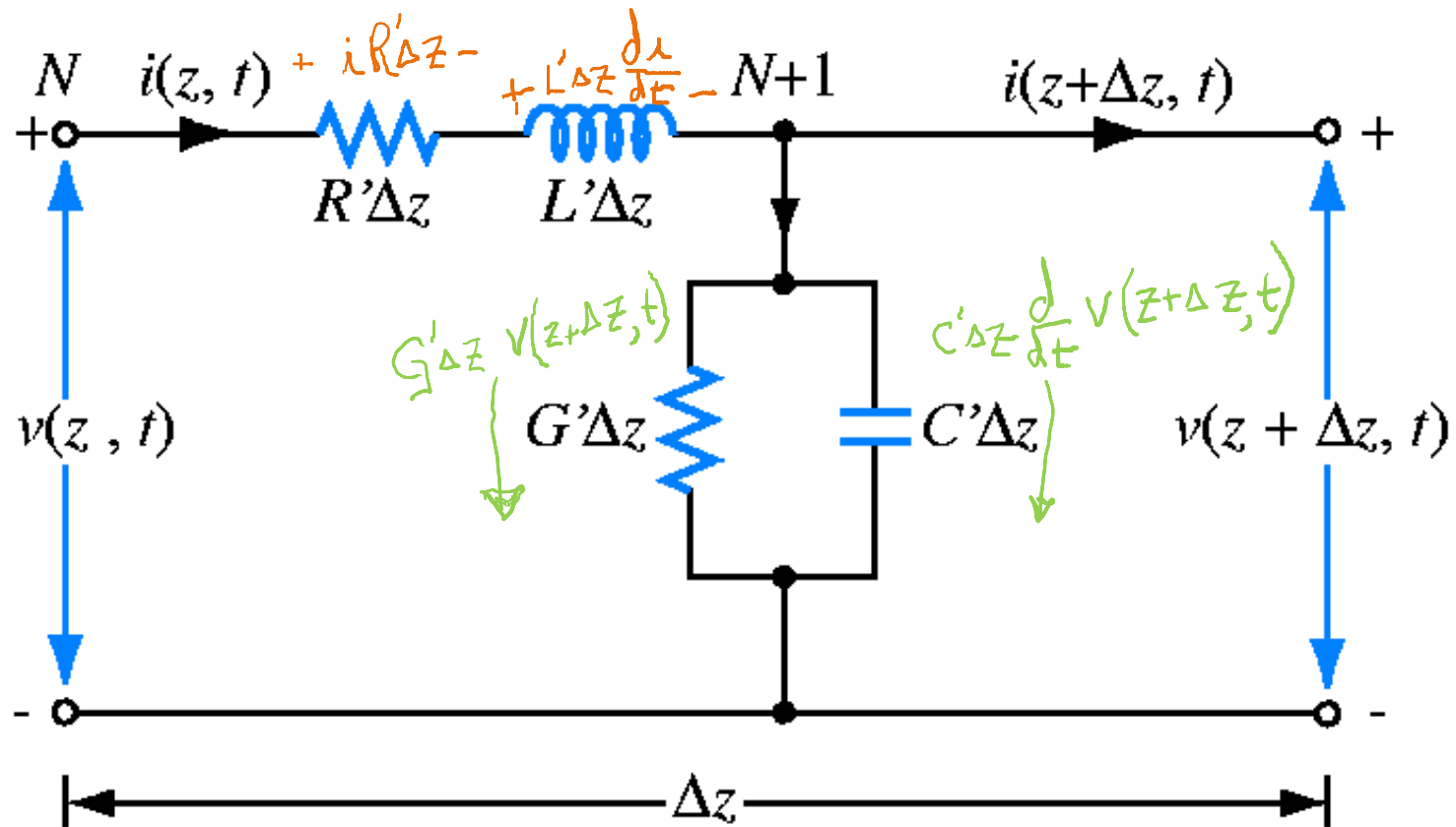

$$v(z, t) - i(z, t)R'\Delta z - L'\Delta z \frac{d}{dt} i(z, t) = v(z + \Delta z, t) \quad \text{KVL}$$
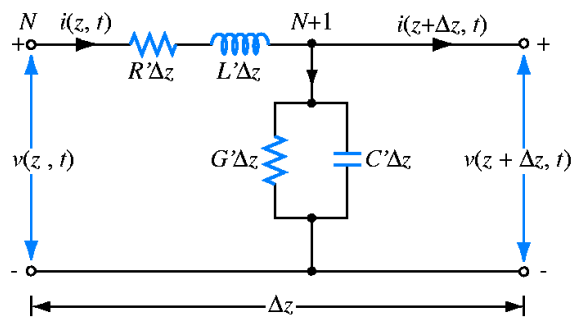
$$i(z, t) - G'\Delta z v(z + \Delta z, t) - C'\Delta z \frac{d}{dt} v(z + \Delta z, t) = i(z + \Delta z, t) \quad \text{KCL}$$



so, our
KVL & KCL
eqn. become



Now, $\frac{v(z+\Delta z, t) - v(z, t)}{\Delta z} \rightarrow \frac{d}{dz} v(z, t)$
as $\Delta z \rightarrow 0$

$$-\frac{dv(z, t)}{dz} = R' i(z, t) + L' \frac{di(z, t)}{dt}$$


$$-\frac{di(z, t)}{dz} = G' v(z, t) + C' \frac{dv(z, t)}{dt}$$

coupled equations...

Query: why **do** we do derivations?? ☺

Phasors*


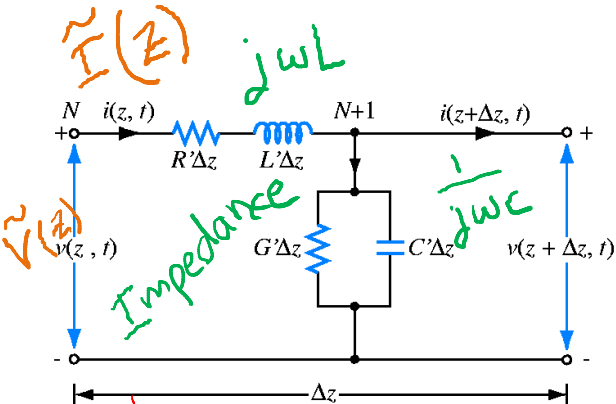
Transmission Line Equations
(a.k.a. Telegrapher's Equations)



* why? Is it practical?


$$-\frac{d\tilde{v}(z)}{dz} = (R' + j\omega L') \tilde{I}(z)$$
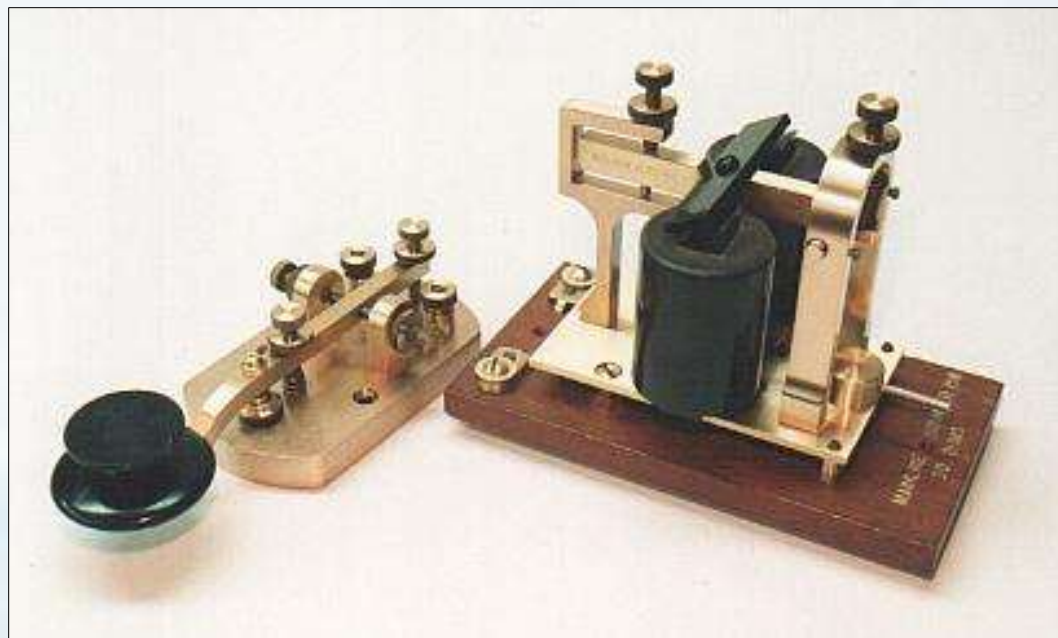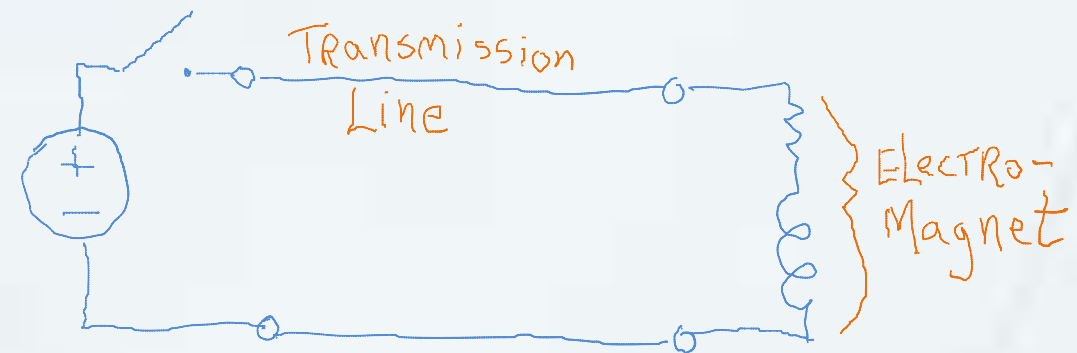
$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{v}(z)$$



$$\begin{aligned} -\frac{d\tilde{V}(z)}{dz} &= (R' + j\omega L') \tilde{I}(z) \\ -\frac{d\tilde{I}(z)}{dz} &= (G' + j\omega C') \tilde{V}(z) \end{aligned}$$

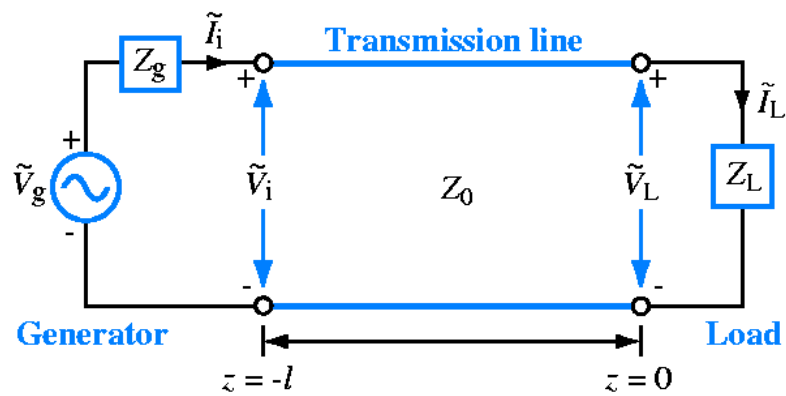The voltage and the current are inter-related!



$$\frac{-d^2 \tilde{V}(z)}{dz^2} = (R' + j\omega L') \frac{d \tilde{I}(z)}{dz}$$

what assumption?

$$\frac{-d^2 \tilde{I}(z)}{dz^2} = (G' + j\omega C') \tilde{V}(z)$$

\Rightarrow

$$\frac{d^2 \tilde{V}(z)}{dz^2} = \gamma^2 \tilde{V}(z)$$


Wave EQTN.

$$\text{with } \gamma \equiv \sqrt{(R' + j\omega L')(G' + j\omega C')} = \alpha + j\beta$$

\nwarrow propagation constant

\Rightarrow
can likewise
show
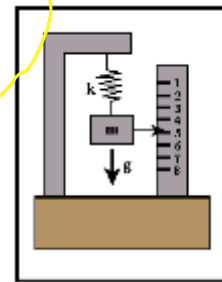
$$\frac{d^2 \tilde{I}(z)}{dz^2} = \gamma^2 \tilde{I}(z)$$



$$\frac{d^2 \tilde{V}(z)}{dz^2} = \gamma^2 \tilde{V}(z)$$

$$\frac{d^2 \tilde{I}(z)}{dz^2} = \gamma^2 \tilde{I}(z)$$

$$\gamma \equiv \sqrt{(R' + j\omega L')(G' + j\omega C')} = \alpha + j\beta = \gamma$$

solve



differential
equation



$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Plug 'em back in to verify!
(are there any other solvs?)


Hmmm...
Let's look at
the 1st term
of voltage

$$\tilde{V}(z) = V_0^+ e^{-\alpha z} e^{-j\beta z}$$

phasor


$$\Rightarrow v(z,t) = V_0^+ e^{-\alpha z} \cos(\omega t - \beta z)$$

time domain

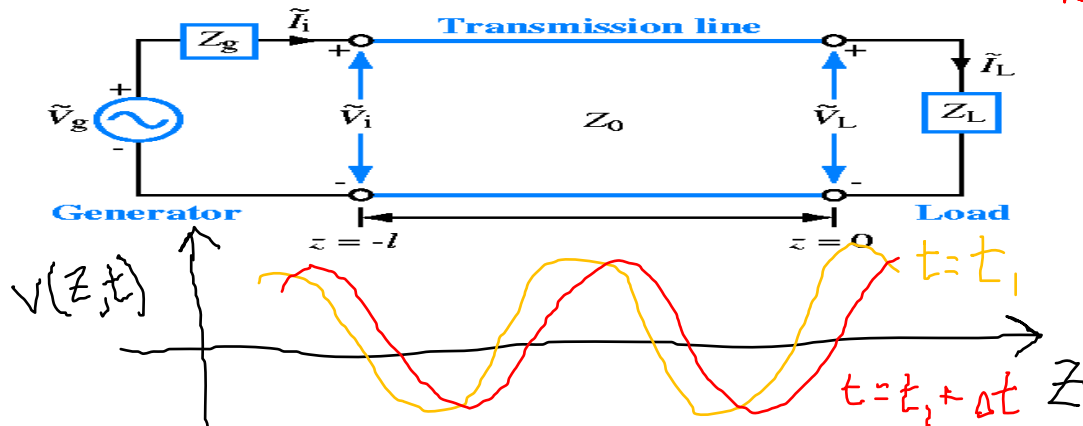

propagation
in $+z$ direction

V

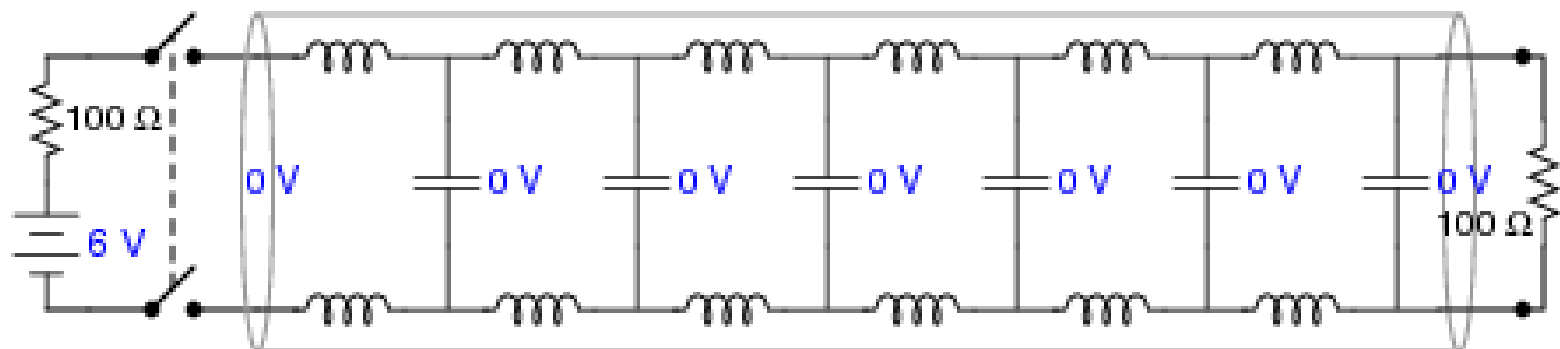

I

Wave Propagation on T-Lines

Wave in
+z direction

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Wave in -z
direction

can have both at
once ... they
add by superposition

$$\tilde{V}(z) = V_0^+ e^{-\alpha z} e^{-j\beta z} \Rightarrow v(z,t) = V_0^+ e^{-\alpha z} \cos(\omega t - \beta z)$$

attenuation

$$\alpha = \text{Re}\{\gamma\}$$

speed

$$\beta = \text{Im}\{\gamma\}$$

phase velocity

$$u_p = \frac{\omega}{\beta} = f\lambda$$

$$\text{so } \beta = \frac{2\pi}{\lambda}$$

It's a T-line if:

$$\frac{\lambda}{\lambda} \sim \frac{f\ell}{c} \gtrsim 1\% \Rightarrow \begin{matrix} 3\text{MHz} \sim \text{m's} \\ 3\text{GHz} \sim \text{mm's} \end{matrix}$$

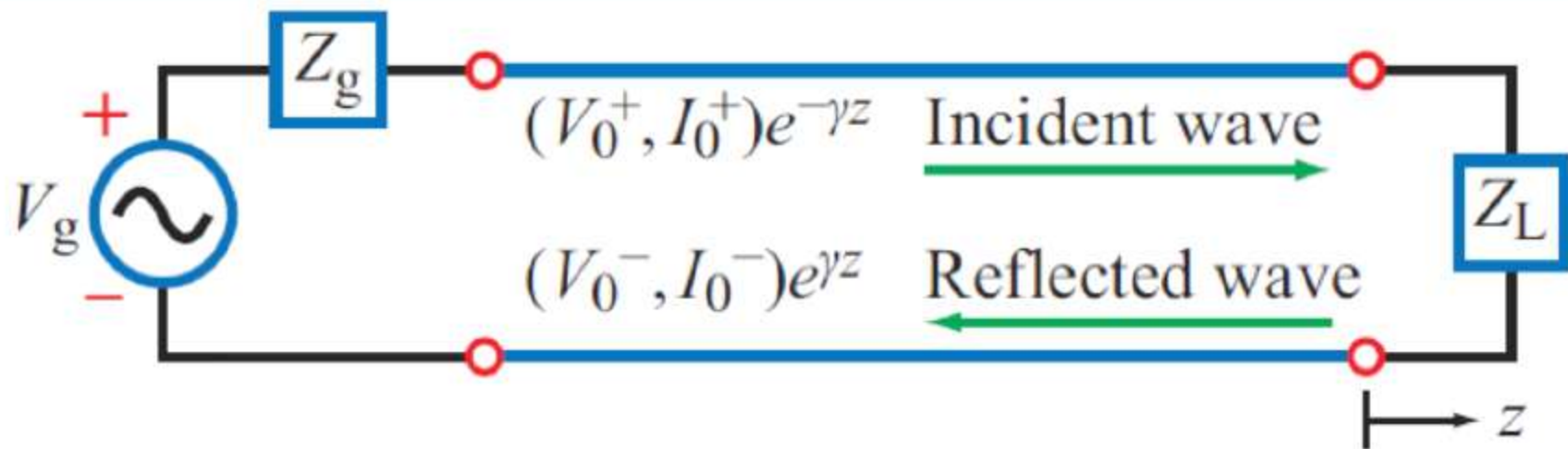


Figure 2-9: In general, a transmission line can support two traveling waves, an incident wave [with voltage and current amplitudes (V_0^+, I_0^+)] traveling along the $+z$ -direction (towards the load) and a reflected wave [with (V_0^-, I_0^-)] traveling along the $-z$ -direction (towards the source).





Characteristic Impedance

$$\frac{d\tilde{V}(z)}{dz} = -V_0^+ \frac{d}{dz} e^{-\gamma z} + -V_0^- \frac{d}{dz} e^{+\gamma z} = -\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z) = (R' + j\omega L') \cdot \tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

$$\Rightarrow \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \equiv Z_0$$

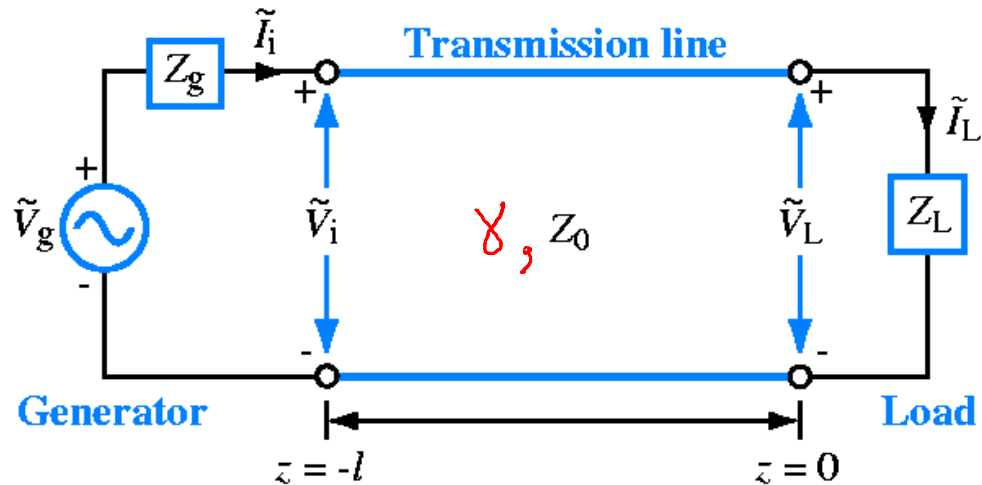Characteristic Impedance
of Transmission Line
(not a function of z or t)
(not equal to \tilde{V}/\tilde{I})



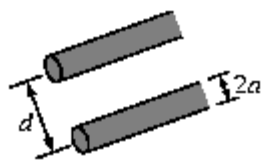

Exercise 2.4 A two-wire air line has the following line parameters: $R' = 0.404$ (mΩ/m), $L' = 2.0$ (μH/m), $G' = 0$, and $C' = 5.56$ (pF/m). For operation at 5 kHz, determine (a) the attenuation constant α , (b) the phase constant β , (c) the phase velocity u_p , and (d) the characteristic impedance Z_0 .

Solution: Given:

$$\begin{aligned} R' &= 0.404 \text{ (m}\Omega\text{/m)}, & G' &= 0, \\ L' &= 2.0 \text{ (}\mu\text{H/m)}, & C' &= 5.56 \text{ (pF/m)}. \end{aligned}$$

(a)

$$\begin{aligned} \alpha &= \Re \left\{ [(R' + j\omega L')(G' + j\omega C')]^{1/2} \right\} \\ &= \Re \left\{ [(0.404 \times 10^{-3} + j5 \times 10^3 \times 2 \times 10^{-6})(0 + j5 \times 10^3 \times 5.56 \times 10^{-12})]^{1/2} \right\} \\ &= \Re [3.37 \times 10^{-7} + j1.05 \times 10^{-4}] \\ \alpha &= 3.37 \times 10^{-7} \text{ (Np/m)}. \end{aligned}$$

Oops! Forgot the 2π ! ($\omega = 2\pi f$)

Note: final numerical answers are fine though ☺

(b) From part (a),

$$\begin{aligned} \beta &= \Im \left\{ [(R' + j\omega L')(G' + j\omega C')]^{1/2} \right\} \\ &= 1.05 \times 10^{-4} \text{ (rad/m)}. \end{aligned}$$

$$(c) \quad u_p = \frac{\omega}{\beta} = \frac{2\pi \times 5 \times 10^3}{1.05 \times 10^{-4}} = 3 \times 10^8 \text{ (m/s)}.$$

$$\begin{aligned} (d) \quad Z_0 &= \frac{R' + j\omega L'}{\alpha + j\beta} \\ &= \frac{0.404 \times 10^{-3} + j5 \times 10^3 \times 2 \times 10^{-6}}{3.37 \times 10^{-7} + j1.05 \times 10^{-4}} \\ &= (600 - j2) \Omega. \end{aligned}$$

an equiv. form for Z_0



For coaxial cables the characteristic impedance will be typically between 20 and 150 ohms (the ones you use in Lab are 50 ohms).

The length of the cable makes no difference whatsoever in regard to the characteristic impedance.

Table 3. Comparing $|Z_0|$ for a variety of transmission lines at 14 MHz.³

| Frequency (MHz) | | Z_0 (Ohms) |
|-----------------|----------|--------------|
| 24AWG | 2 twists | 45 |
| | 3 twists | 44 |
| | 4 twists | 43 |
| | 5 twists | 41 |
| 26AWG | 2 twists | 57 |
| | 3 twists | 54 |
| | 4 twists | 48 |
| | 5 twists | 47 |
| 28AWG | 3 twists | 51 |
| | 4 twists | 49 |
| | 5 twists | 47 |
| 30AWG | 3 twists | 49 |
| | 4 twists | 46 |
| | 5 twists | 47 |




Z_0

????



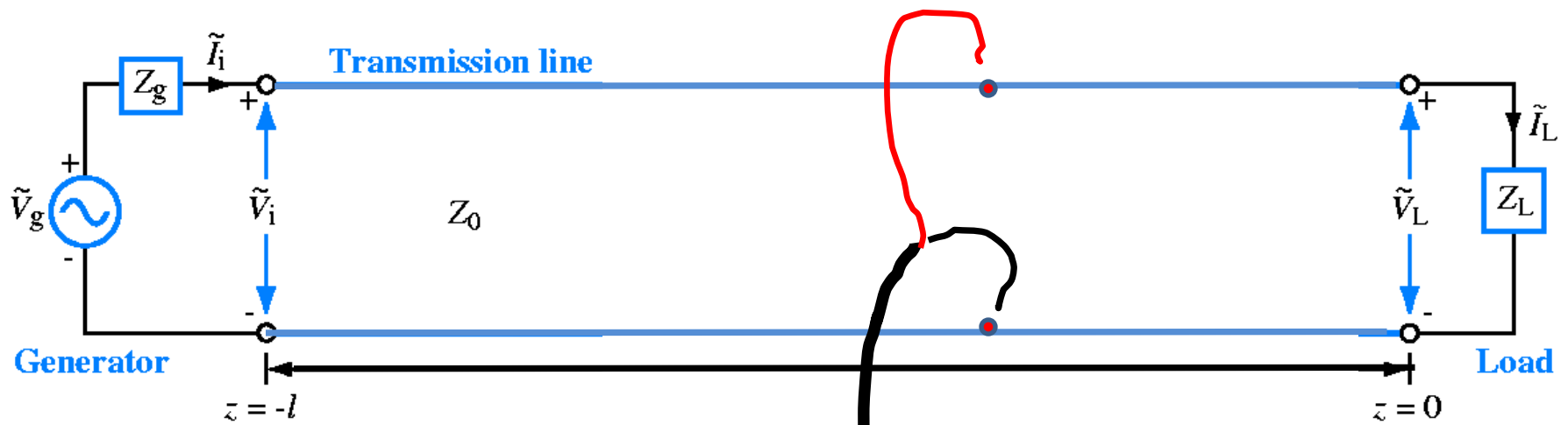**Example of acoustic
“transmission lines”**






$$\gamma \equiv \sqrt{(R' + j\omega L')(G' + j\omega C')} = \alpha + j\beta$$



$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$
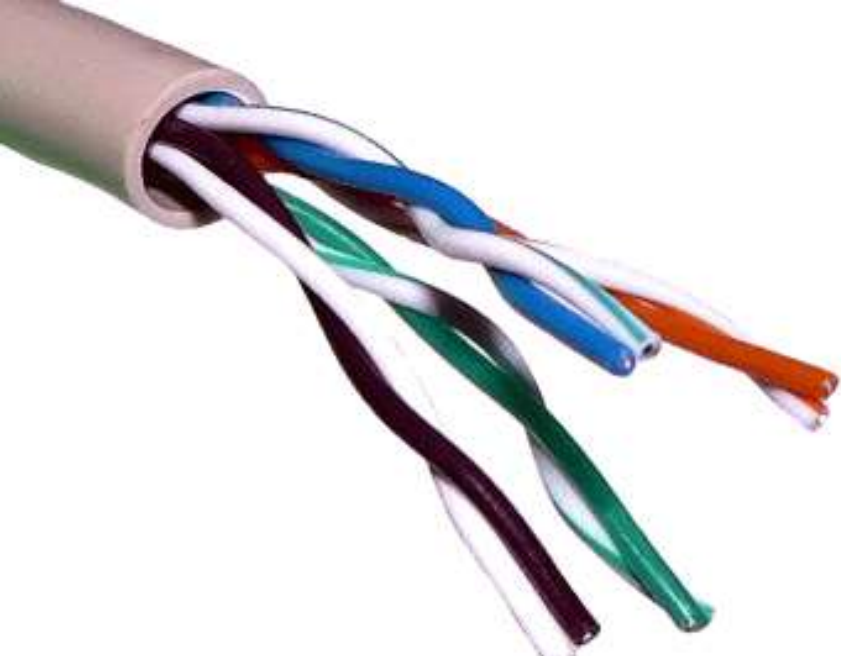
$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-}$$




(a)

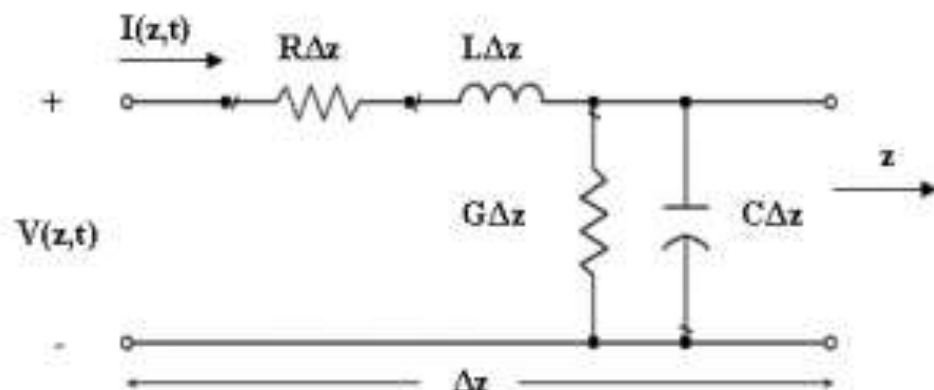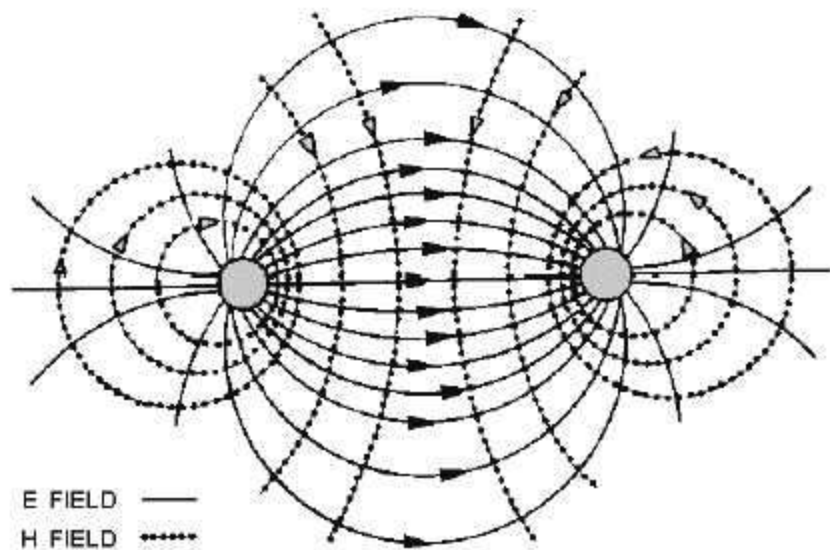

(b)

T-Lines (from Last Time)

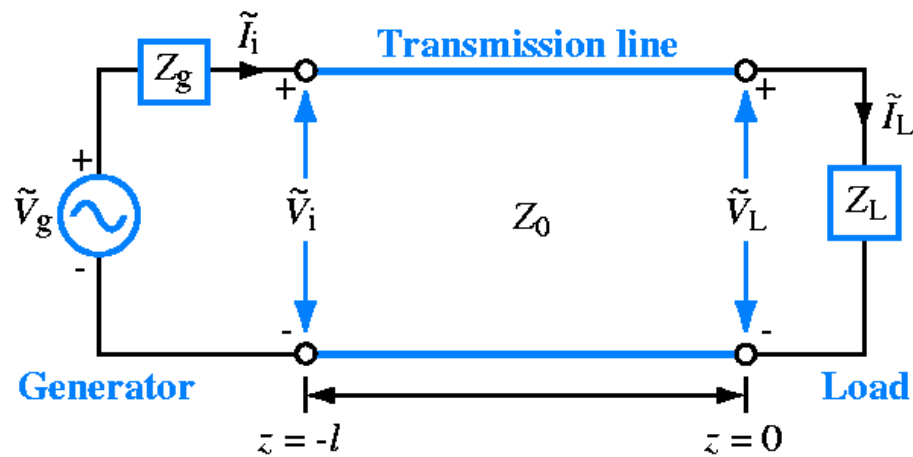


$$\gamma \equiv \sqrt{(R' + j\omega L')(G' + j\omega C')} = \alpha + j\beta$$

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$


$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-}$$


Lossless T-Line (special case)

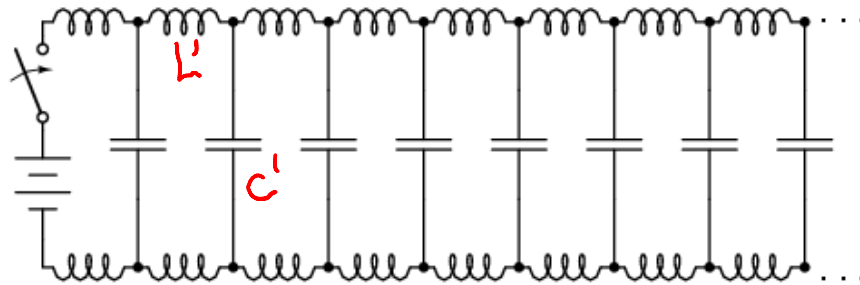


$$R' = G' = 0$$

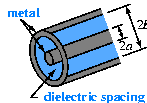

(a) Coaxial line

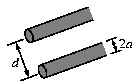

(b) Two-wire line

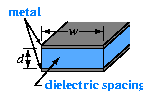

(c) Parallel-plate line

$$\gamma = \sqrt{j\omega L' \cdot j\omega C'} = j\omega \sqrt{L'C'}$$

$$\Rightarrow \alpha = 0 = \text{Lossless!}$$

$$\beta = \omega \sqrt{L'C'}$$

Remember
LC From
210? ☺

$$Z_0 = \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}} = \text{purely Real}$$

(when is this a good approx.?)

| | Propagation Constant $\gamma = \alpha + j\beta$ | Phase Velocity u_p | Characteristic Impedance Z_0 |
|---|--|-----------------------------|---|
| General case | $\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$ | $u_p = \omega/\beta$ | $Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$ |
| Lossless ($R' = G' = 0$) | $\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$ | $u_p = c/\sqrt{\epsilon_r}$ | $Z_0 = \sqrt{L'/C'}$ |
| Lossless coaxial | $\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$ | $u_p = c/\sqrt{\epsilon_r}$ | $Z_0 = (60/\sqrt{\epsilon_r}) \ln(b/a)$ |
| Lossless two wire | $\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$ | $u_p = c/\sqrt{\epsilon_r}$ | $Z_0 = (120/\sqrt{\epsilon_r}) \cdot \ln[(d/2a) + \sqrt{(d/2a)^2 - 1}]$ $Z_0 \simeq (120/\sqrt{\epsilon_r}) \ln(d/a),$ if $d \gg a$ |
| Lossless parallel plate | $\alpha = 0, \beta = \omega\sqrt{\epsilon_r}/c$ | $u_p = c/\sqrt{\epsilon_r}$ | $Z_0 = (120\pi/\sqrt{\epsilon_r}) (d/w)$ |
| Notes: (1) $\mu = \mu_0$, $\epsilon = \epsilon_r \epsilon_0$, $c = 1/\sqrt{\mu_0 \epsilon_0}$, and $\sqrt{\mu_0/\epsilon_0} \simeq (120\pi) \Omega$, where ϵ_r is the permittivity of insulating material. (2) For coaxial line, a and b are radii of inner and outer conductors. (3) For two-wire line, a = wire radius and d = separation between wire centers. (4) For parallel-plate line, w = width of plate and d = separation between the plates. | | | |

For Lossless T-Lines


$u_p = \text{phase velocity}$
 $= \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}$
 $= f\lambda$ with $\omega = 2\pi f$

Note: $\frac{1}{\sqrt{L'C'}}$ is not a function of frequency!


\Rightarrow Lossless T-Lines are non-dispersive

See HW for dispersionless line:
 $R'C' = L'G'$

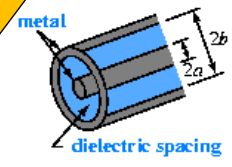
Note: we will get to all the μ & ϵ stuff later in the semester ... suffice it to say that L', C' , etc. depend on what the T-Line is made of!



(a) Coaxial line

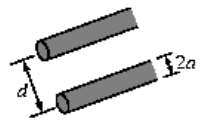


(b) Two-wire line

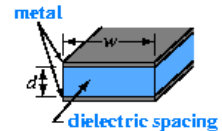

(c) Parallel-plate line

Where do those leftward propagating waves come from??

for Lossless

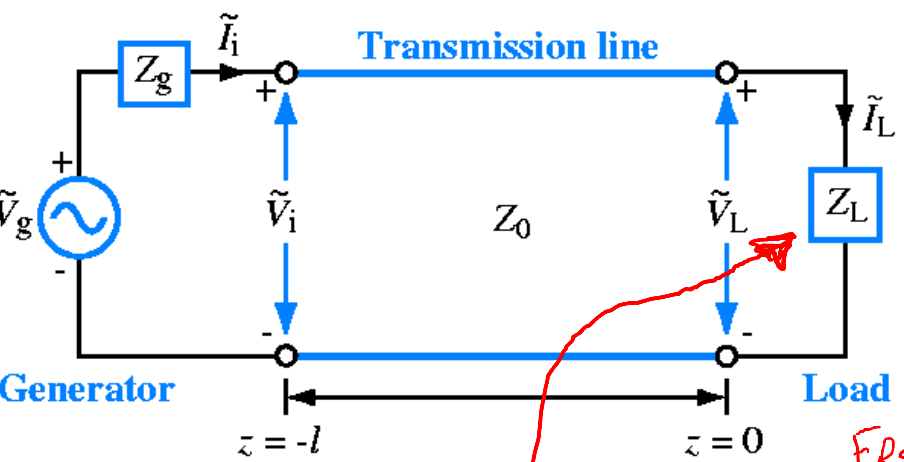

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \quad (1)$$

$$\begin{aligned} \tilde{I}(z) &= I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z} \quad (2) \end{aligned}$$

$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} \quad (3)$$

FROM Defn. Z_0




$$\frac{\text{EQTN (1) at } z=0}{\text{EQTN (2) at } z=0} = \frac{\tilde{V}_L}{\tilde{I}_L} = Z_L, \text{ from (3)}$$

$$\Rightarrow V_0^- = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) V_0^+$$

Reflected wave amplitude

Reflection Coefficient (Voltage), Γ

Source wave amplitude

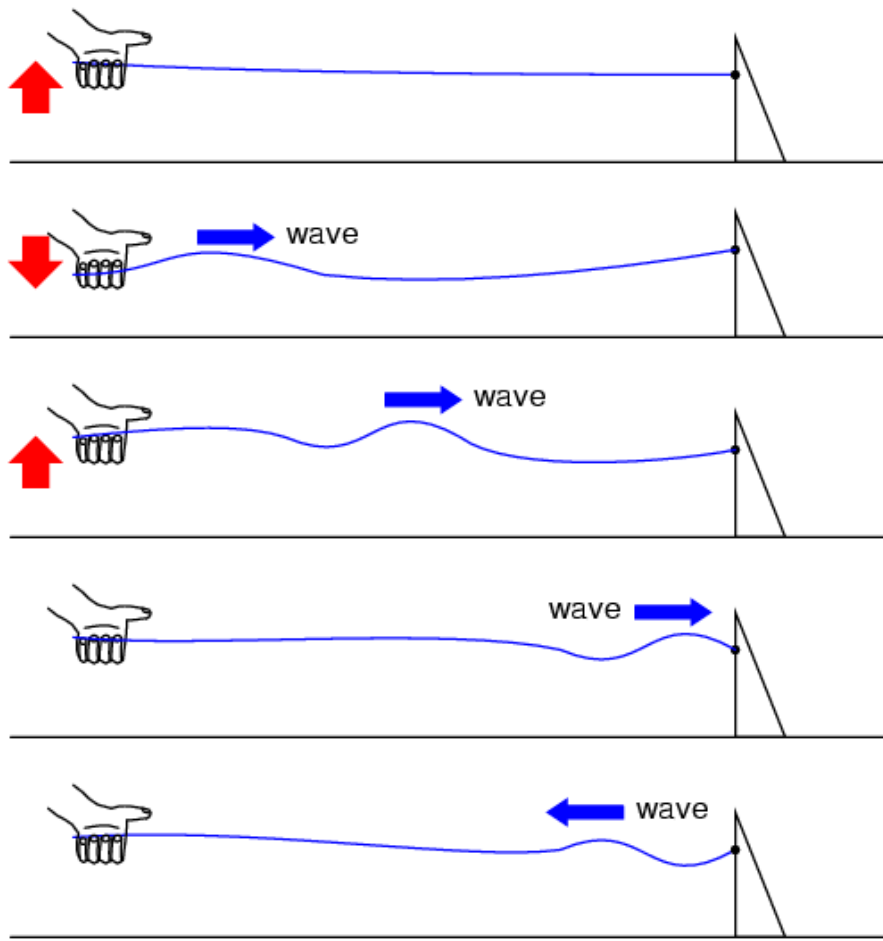

Reflection Coefficient

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1}$$

$$= |\Gamma| e^{j\theta_R}$$


in general,
complex
(even for Lossless
Lines)

$$\frac{V_0^-}{V_0^+} = \Gamma, \quad \frac{I_0^-}{I_0^+} = -\Gamma$$

Note: If $Z_L = Z_0$, $\Gamma = 0$
 \Rightarrow no Reflection!

Matched Load 😊

Example

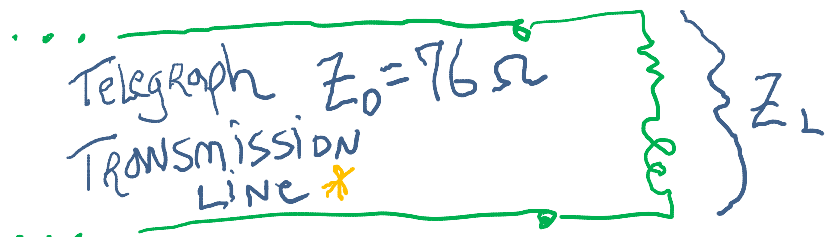

* Lossless!

$$R = 2 \Omega$$
$$L = 1 \text{ mH}$$



What is the Reflection Coefficient at the Load?

(oh yeah, assume 1 kHz)

$$Z_L = 2 + j(2\pi \times 1 \times 10^3 \times 1 \times 10^{-3})$$
$$= 2 + j6.28 \Omega$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.94 - j0.16 = 0.95 \angle -9.5^\circ$$

Yikes! it's mostly Reflected!

For a purely Reactive Load, can show that $|\Gamma| = 1$.

What's this all mean??

Example 2-3: Reflection Coefficient of a Series *RC* Load

A $100\text{-}\Omega$ transmission line is connected to a load consisting of a $50\text{-}\Omega$ resistor in series with a 10-pF capacitor. Find the reflection coefficient at the load for a 100-MHz signal.


Solution: The following quantities are given (Fig. 2-13):

$$R_L = 50\ \Omega, \quad C_L = 10\ \text{pF} = 10^{-11}\ \text{F},$$

$$Z_0 = 100\ \Omega, \quad f = 100\ \text{MHz} = 10^8\ \text{Hz}.$$

The **normalized** load impedance is
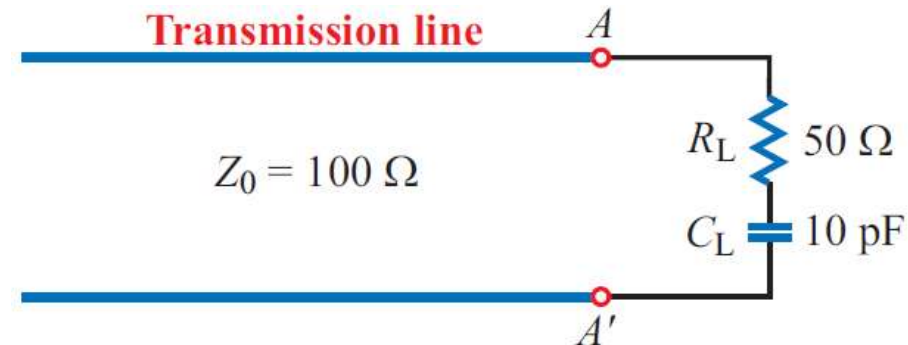
$$\begin{aligned} z_L &= \frac{Z_L}{Z_0} = \frac{R_L - j/(\omega C_L)}{Z_0} \\ &= \frac{1}{100} \left(50 - j \frac{1}{2\pi \times 10^8 \times 10^{-11}} \right) \\ &= (0.5 - j1.59)\ \Omega. \end{aligned}$$




$$\begin{aligned} \Gamma &= \frac{z_L - 1}{z_L + 1} \\ &= \frac{0.5 - j1.59 - 1}{0.5 - j1.59 + 1} \\ &= \frac{-0.5 - j1.59}{1.5 - j1.59} = \frac{-1.67e^{j72.6^\circ}}{2.19e^{-j46.7^\circ}} = -0.76e^{j119.3^\circ}. \end{aligned}$$

This result may be converted into the form of Eq. (2.62) by replacing the minus sign with e^{-j180° . Thus,

$$\Gamma = 0.76e^{j119.3^\circ} e^{-j180^\circ} = 0.76e^{-j60.7^\circ} = 0.76\angle -60.7^\circ,$$

or

$$|\Gamma| = 0.76, \quad \theta_r = -60.7^\circ.$$

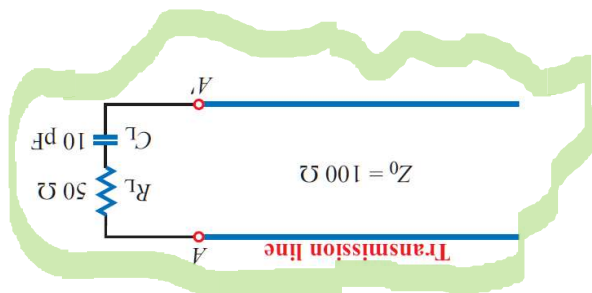

Transmitted wave and reflected wave *add* by superposition:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

In this animation:


Green wave moves to the right (+z)
Blue wave (the reflected one, although we do not see the load in this animation) moves to the left (-z)
Yellow waveform is the superposition of both (and therefore the **total** voltage on the line). It is a standing wave! 😊




Standing Wave animation (oscilloscope)

<http://www.youtube.com/watch?v=ic73oZogr70>



Standing wave on a string

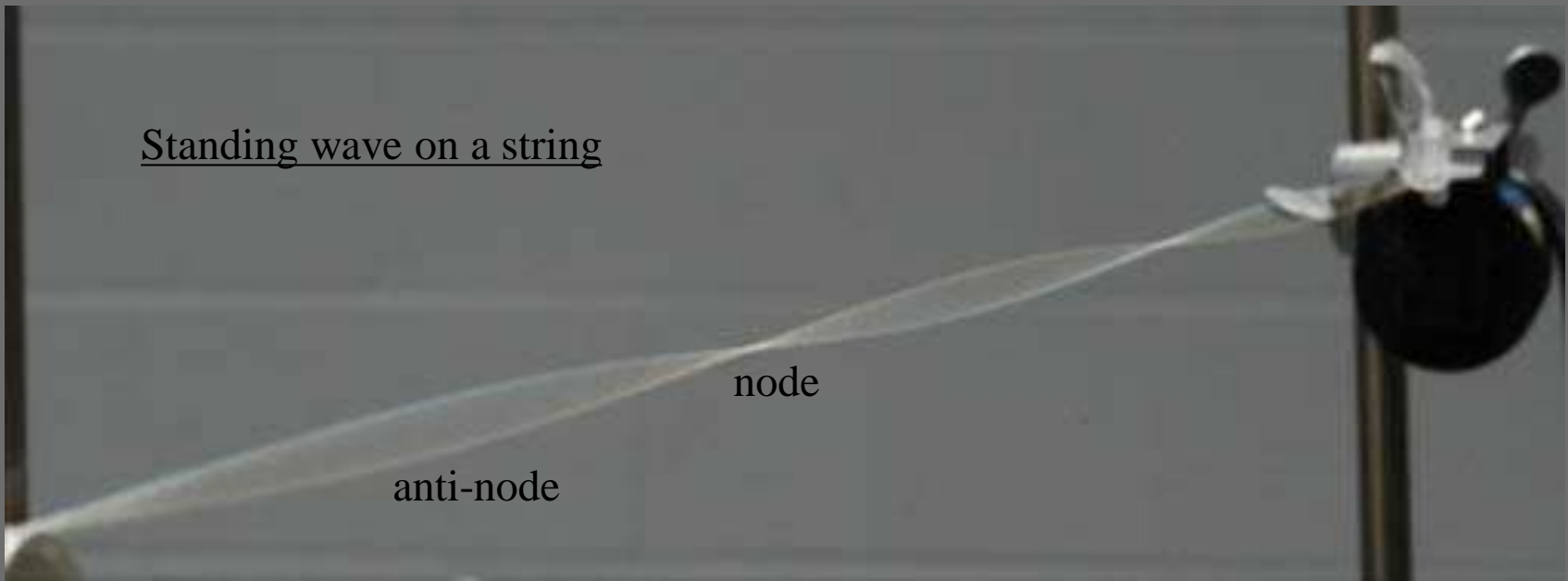

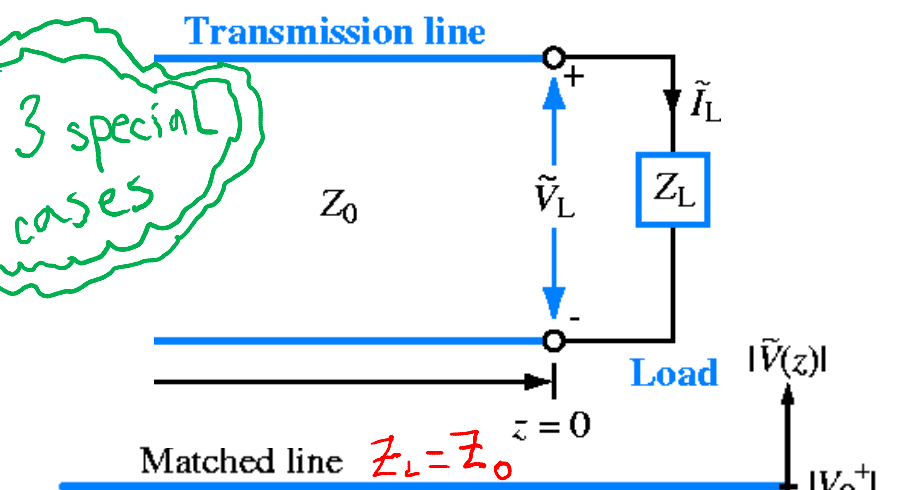


$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

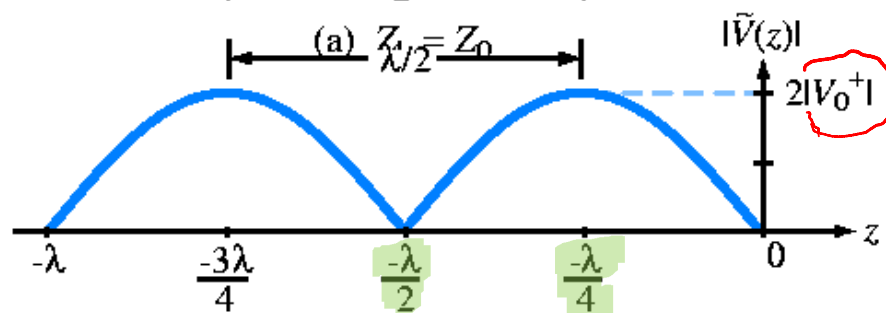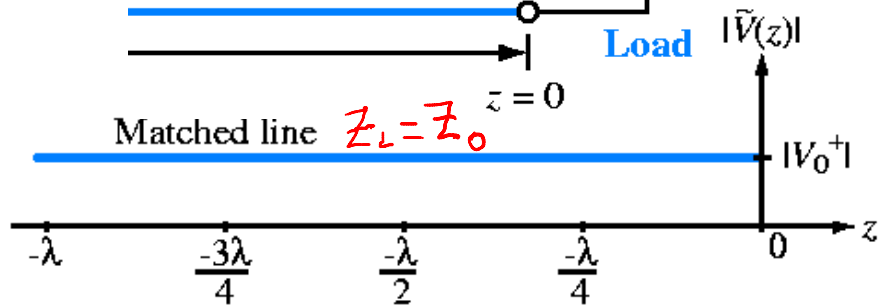The load represents a **boundary condition!**




Amplitude of wave
 $\Gamma = -1$

(b) $Z_L = 0$ (short circuit)

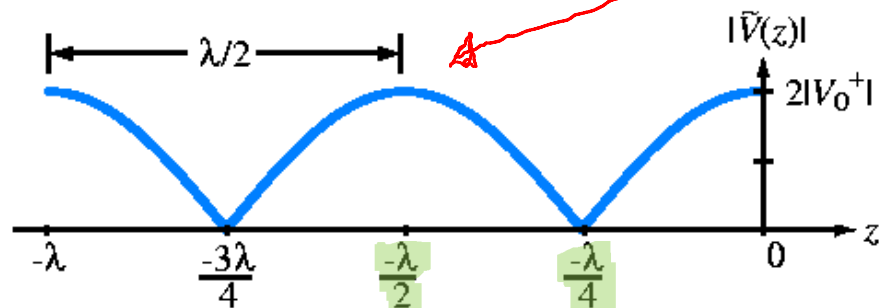


Point of max voltage is point of min current (and vice versa)

$\Gamma = 1$

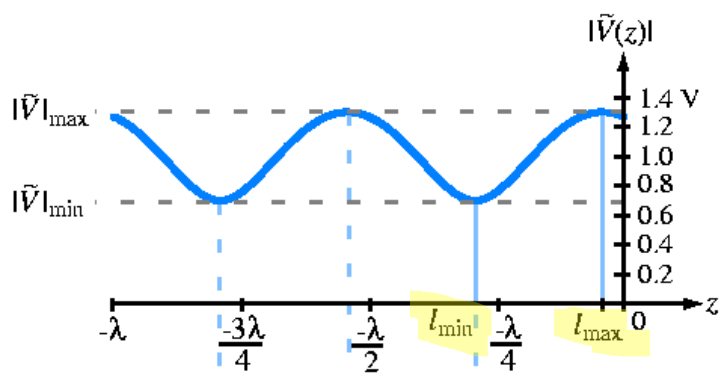

(a) $|\tilde{V}(z)|$ versus z

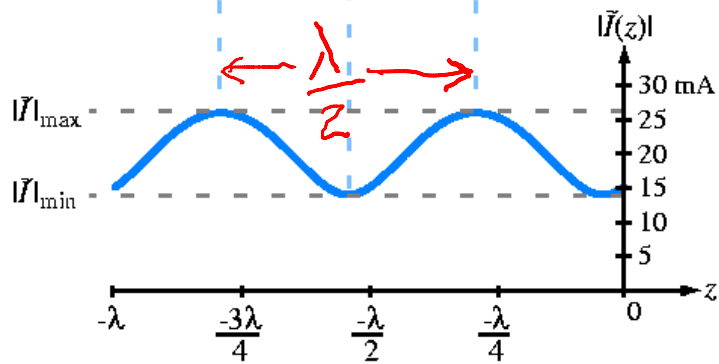

(b) $|\tilde{I}(z)|$ versus z


Note

- For a general Load, the max or min voltage is not necessarily at location $z=0$ (the Load)
- For a general Load, there don't need to be true nodes (e.g. $|\tilde{V}|=0$) anywhere.

(Voltage) Standing Wave Ratio*

$$S \equiv \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1+|\Gamma|}{1-|\Gamma|}$$

* VSWR OR SWR

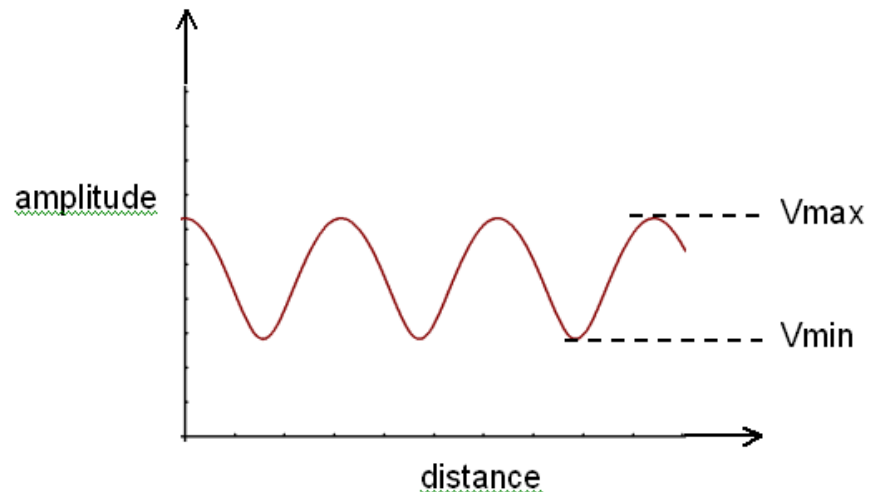

Exercise 2.10 A $140\text{-}\Omega$ lossless line is terminated in a load impedance $Z_L = (280 + j182)\text{ }\Omega$. If $\lambda = 72\text{ cm}$, find (a) the reflection coefficient Γ , (b) the voltage standing-wave ratio S , (c) the locations of voltage maxima, and (d) the locations of voltage minima.

Solution:

$$Z_0 = 140\text{ }\Omega, \quad Z_L = (280 + j182)\text{ }\Omega$$

(a)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{280 + j182 - 140}{280 + j182 + 140} = \frac{140 + j182}{420 + j182} = 0.5 \angle 29^\circ$$

$$= |\Gamma| \angle \theta_r$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.5}{1 - 0.5} = \frac{1.5}{0.5} = 3$$

(b) Note: if $|\Gamma| = 0$, then $S = 1$

(c)

$$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$$

$$= \frac{(29\pi/180) \times 0.72}{4\pi} + \frac{n \times 0.72}{2}$$

$$= (2.9 + 36n)\text{ (cm)}, \quad n = 0, 1, 2, \dots$$


what does $|\Gamma| = 0$ correspond to?

(d)

$$l_{\min} = l_{\max} + \frac{\lambda}{4}$$

$$= \left[(2.9 + 36n) + \frac{72}{4} \right] \text{ cm}$$

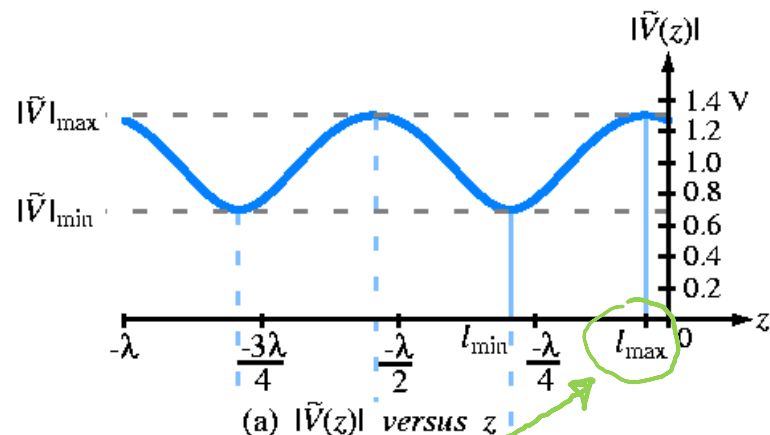
$$= (20.9 + 36n)\text{ cm}, \quad n = 0, 1, 2, \dots$$



the 1st max in the standing wave is located $l_{\max} = \frac{\theta_r \lambda}{4\pi}$ from the load.
(for Lossless Lines)

Q: what if $|\Gamma| = 1$?
what's that mean?
what is SWR?

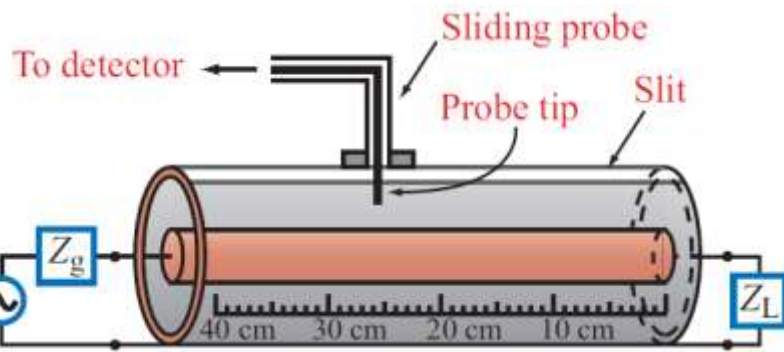Example 2-6: Measuring Z_L with a Slotted Line



Solution: The following quantities are given:

$$Z_0 = 50 \, \Omega,$$

$$S = 3,$$

$$d_{\min} = 12 \, \text{cm}.$$

Since the distance between successive voltage minima is $\lambda/2$,

$$\lambda = 2 \times 0.3 = 0.6 \, \text{m},$$

and

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.6} = \frac{10\pi}{3} \quad (\text{rad/m}).$$

From Eq. (2.73), solving for $|\Gamma|$ in terms of S gives

$$\begin{aligned} |\Gamma| &= \frac{S-1}{S+1} \\ &= \frac{3-1}{3+1} \\ &= 0.5. \end{aligned}$$

Next, we use the condition given by Eq. (2.71) to find θ_r :

$$2\beta d_{\min} - \theta_r = \pi, \quad \text{for } n = 0 \text{ (first minimum),}$$

which gives

$$\begin{aligned} \theta_r &= 2\beta d_{\min} - \pi \\ &= 2 \times \frac{10\pi}{3} \times 0.12 - \pi \\ &= -0.2\pi \text{ (rad)} \\ &= -36^\circ. \end{aligned}$$

Hence,

$$\begin{aligned} \Gamma &= |\Gamma|e^{j\theta_r} \\ &= 0.5e^{-j36^\circ} \\ &= 0.405 - j0.294. \end{aligned}$$

Solving Eq. (2.59) for Z_L , we have

$$\begin{aligned} Z_L &= Z_0 \left[\frac{1 + \Gamma}{1 - \Gamma} \right] \\ &= 50 \left[\frac{1 + 0.405 - j0.294}{1 - 0.405 + j0.294} \right] \\ &= (85 - j67) \, \Omega. \end{aligned}$$

EXAMPLE (S)

CIRCLE (T)RUE or (F)ALSE²



5) Z_o is only defined for lossless transmission lines. T F

6) You do **not** have to treat a 6 foot long power cord as a transmission line. T F

3) Given a lossless transmission line of known intrinsic impedance, phase speed and length, can you determine the load impedance from measurements of the input impedance? Explain.




Lecture 6

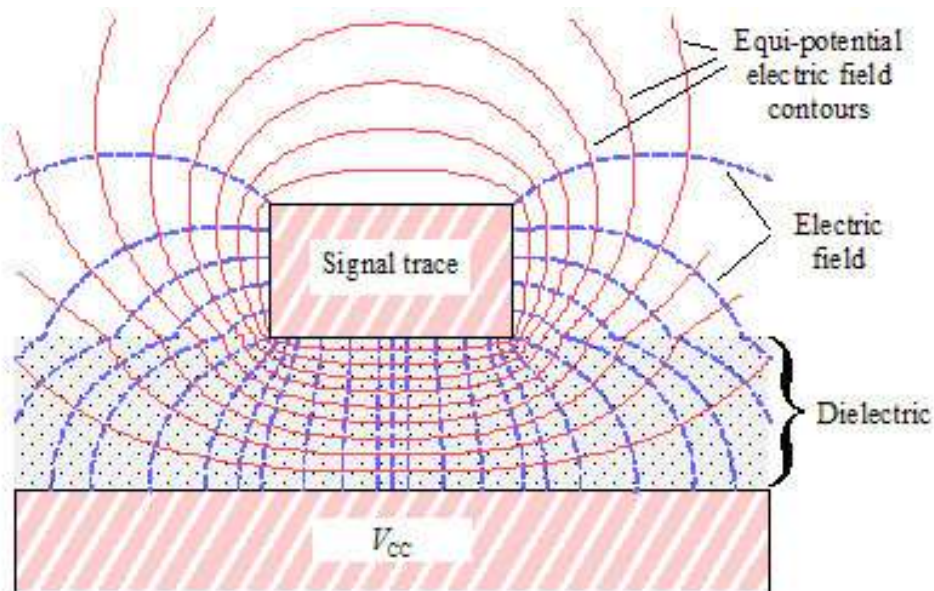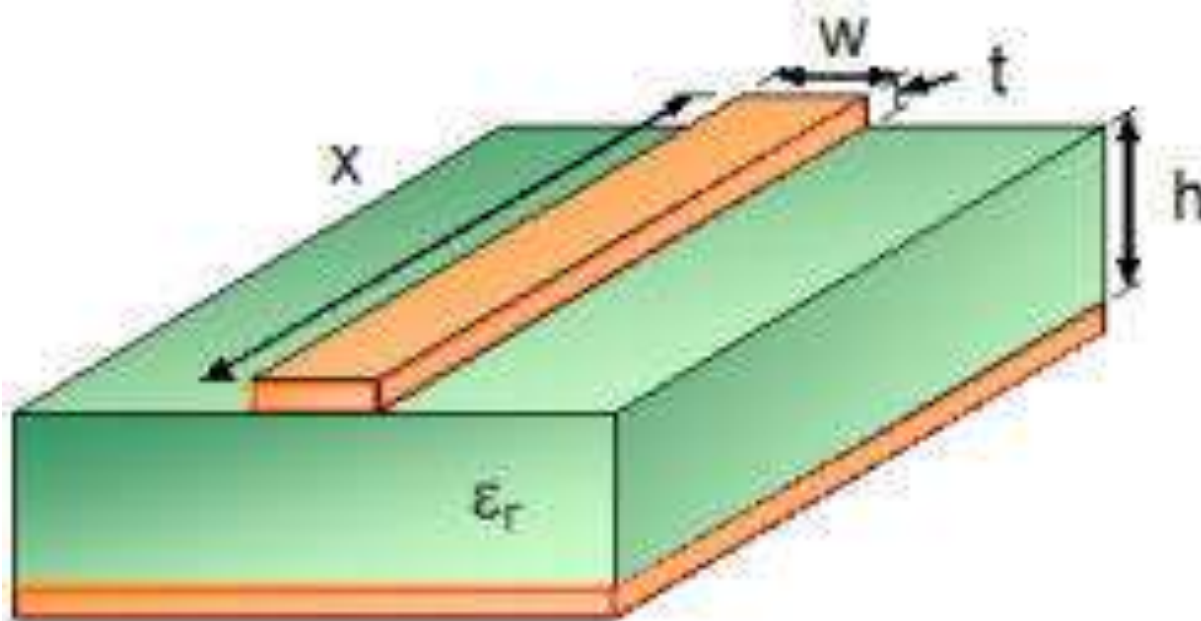

http://www.naic.edu/reu_program.html
<http://www.haystack.mit.edu/edu/reu/>
<http://www.csnr.usra.edu/>
<http://www.unl.edu/summerprogram/>
<http://www.vs.afrl.af.mil/SpaceScholars/>

PLUS lots more !!!! ☺

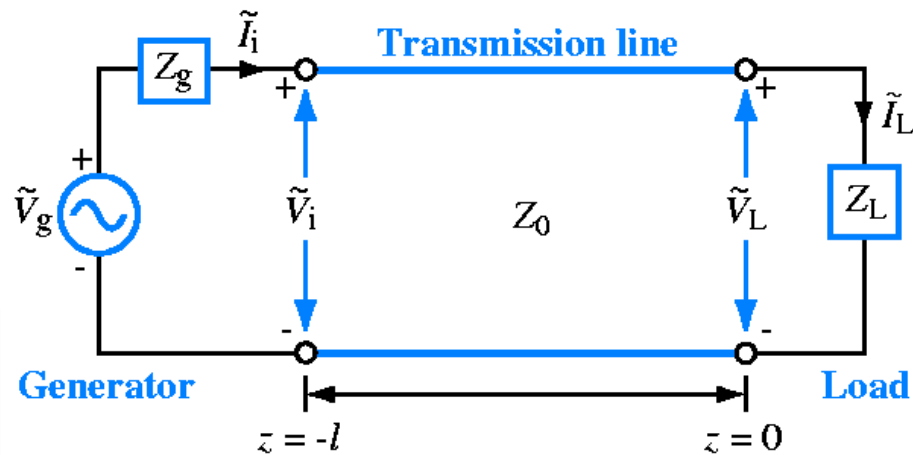

Reflection

$$\Gamma = \frac{V_o^-}{V_o^+} = \frac{-I_o^-}{I_o^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$



Note: Function of frequency!

Standing Waves



Standing Wave animation (oscilloscope)
<http://www.youtube.com/watch?v=ic73oZoqr70>

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

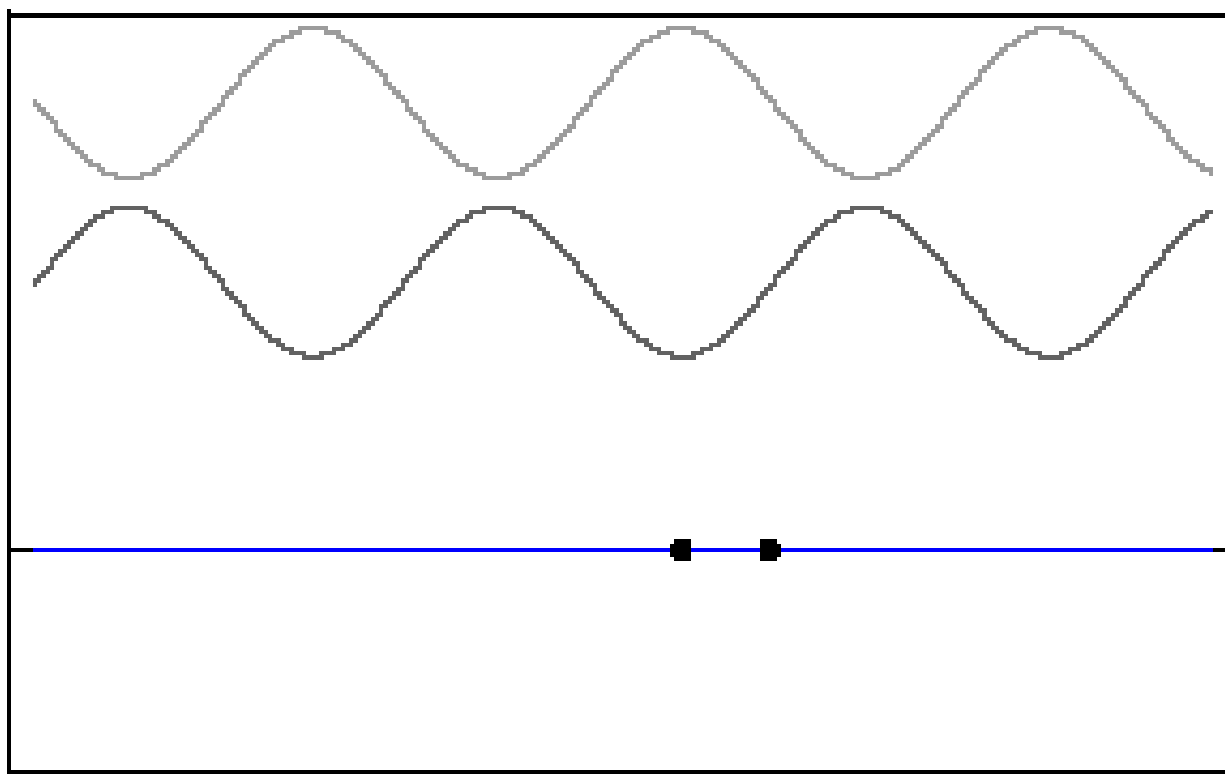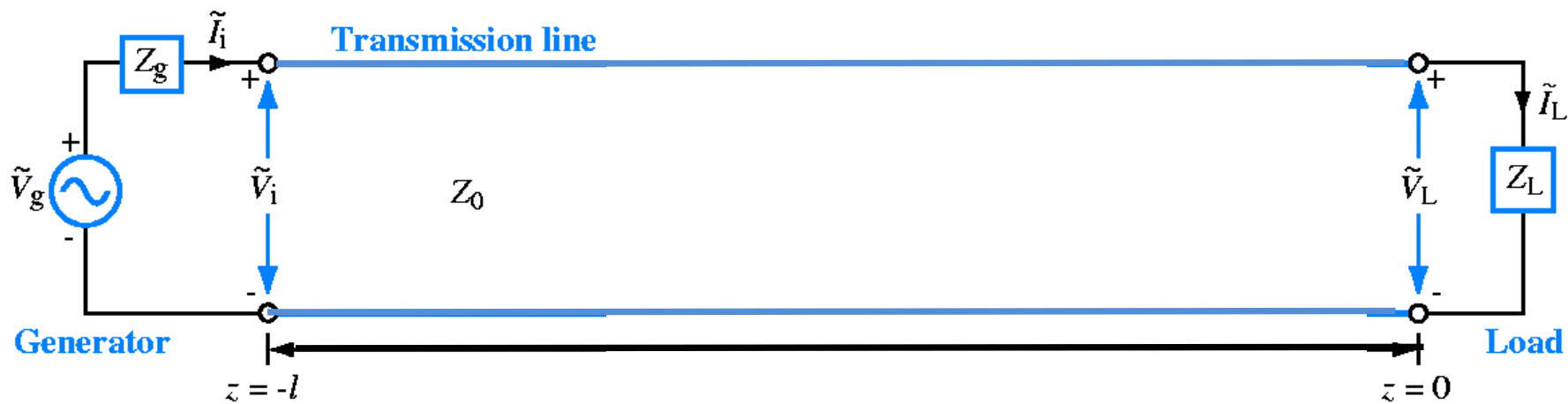Note: \tilde{V} & \tilde{I}
 are functions of position z
 (see slotted line ☺)



What is the load Z_L in this case?

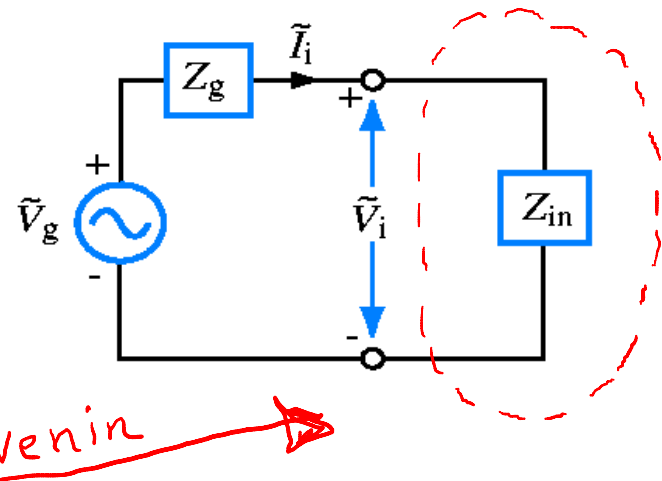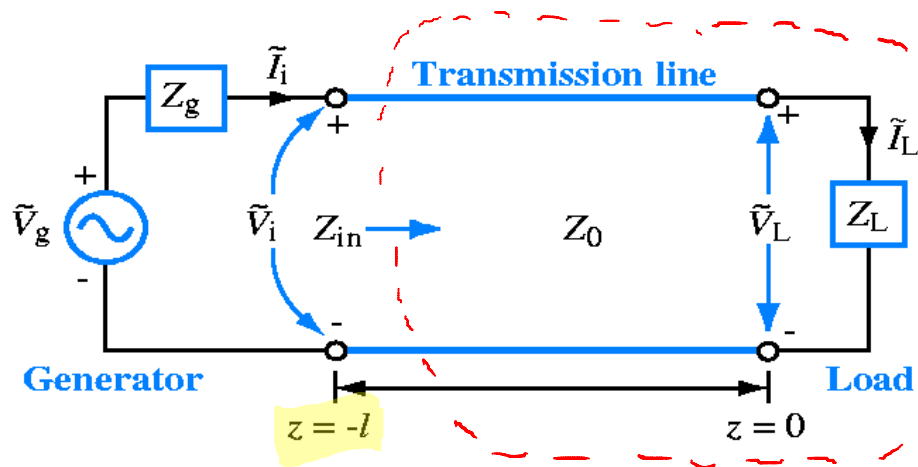

Input Impedance

Lossless \downarrow

$$Z_{in} = \frac{\tilde{V}(-l)}{\tilde{I}(-l)} = \frac{V_o^+ e^{-j\beta(-l)} + V_o^- e^{+j\beta(-l)}}{I_o^+ e^{-j\beta(-l)} + I_o^- e^{+j\beta(-l)}} = Z_0 \left[\frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right]$$

ΓV_o^+

V_o^+ / Z_0

$-\Gamma I_o^+$

Notes:

* Z_{in} is periodic in l

* $Z_{in} \neq Z_0$

* $\tilde{V}_i = \left(\frac{Z_{in}}{Z_{in} + Z_g} \right) \tilde{V}_g = V_o^+(-l) + V_o^-(-l)$

so can write in terms of trig, too

$$\beta = \text{Im}\{\gamma\} = \frac{2\pi}{\lambda}$$

or, equivalently:


$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$$

Example 2-7: Complete Solution for $v(z, t)$ and $i(z, t)$

A 1.05-GHz generator circuit with series impedance $Z_g = 10 \Omega$ and voltage source given by

$$v_g(t) = 10 \sin(\omega t + 30^\circ) \quad (\text{V})$$

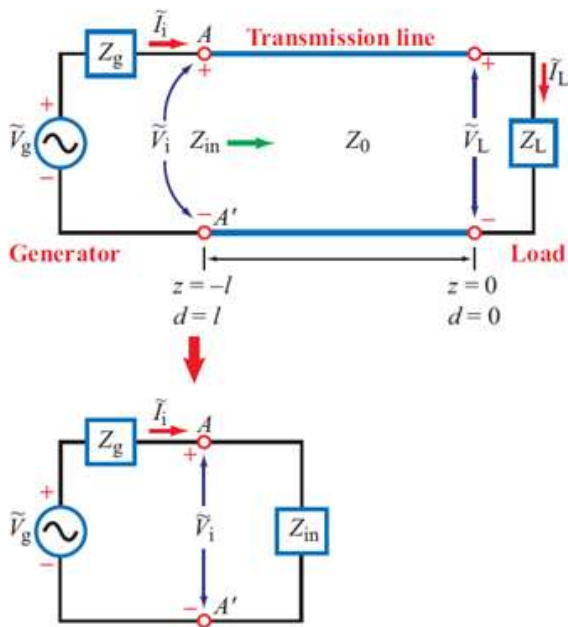is connected to a load $Z_L = (100 + j50) \Omega$ through a 50- Ω , 67-cm long lossless transmission line. The phase velocity of



the line is $0.7c$, where c is the velocity of light in a vacuum. Find $v(z, t)$ and $i(z, t)$ on the line.

Solution: From the relationship $u_p = \lambda f$, we find the wavelength

$$\begin{aligned} \lambda &= \frac{u_p}{f} \\ &= \frac{0.7 \times 3 \times 10^8}{1.05 \times 10^9} \\ &= 0.2 \text{ m,} \end{aligned}$$

and

$$\begin{aligned} \beta l &= \frac{2\pi}{\lambda} l \\ &= \frac{2\pi}{0.2} \times 0.67 \\ &= 6.7\pi = 0.7\pi = 126^\circ, \end{aligned}$$

where we have subtracted multiples of 2π . The voltage reflection coefficient at the load is

$$\begin{aligned} \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{(100 + j50) - 50}{(100 + j50) + 50} \\ &= 0.45e^{j26.6^\circ}. \end{aligned}$$

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{1 + \Gamma_l}{1 - \Gamma_l} \right) \\ &= Z_0 \left(\frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right) \\ &= 50 \left(\frac{1 + 0.45e^{j26.6^\circ} e^{-j252^\circ}}{1 - 0.45e^{j26.6^\circ} e^{-j252^\circ}} \right) = (21.9 + j17.4) \Omega. \end{aligned}$$

Rewriting the expression for the generator voltage with the cosine reference, we have

$$\begin{aligned} v_g(t) &= 10 \sin(\omega t + 30^\circ) \\ &= 10 \cos(90^\circ - \omega t - 30^\circ) \\ &= 10 \cos(\omega t - 60^\circ) \\ &= \Re[10e^{-j60^\circ} e^{j\omega t}] = \Re[\tilde{V}_g e^{j\omega t}] \quad (\text{V}). \end{aligned}$$

Hence, the phasor voltage \tilde{V}_g is given by

$$\begin{aligned} \tilde{V}_g &= 10 e^{-j60^\circ} \\ &= 10 \angle -60^\circ \quad (\text{V}). \end{aligned}$$

Application of Eq. (2.82) gives

$$\begin{aligned} V_0^+ &= \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right) \\ &= \left[\frac{10e^{-j60^\circ} (21.9 + j17.4)}{10 + 21.9 + j17.4} \right] \\ &\quad \cdot (e^{j126^\circ} + 0.45e^{j26.6^\circ} e^{-j126^\circ})^{-1} \\ &= 10.2e^{j159^\circ} \quad (\text{V}). \end{aligned}$$

Using Eq. (2.63a) with $z = -d$, the phasor voltage on the line is





$$\begin{aligned} \tilde{V}(d) &= V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d}) \\ &= 10.2e^{j159^\circ} (e^{j\beta d} + 0.45e^{j26.6^\circ} e^{-j\beta d}), \end{aligned}$$

and the corresponding instantaneous voltage $v(d, t)$ is






$$\begin{aligned} v(d, t) &= \Re[\tilde{V}(d) e^{j\omega t}] \\ &= 10.2 \cos(\omega t + \beta d + 159^\circ) \\ &\quad + 4.55 \cos(\omega t - \beta d + 185.6^\circ) \quad (\text{V}). \end{aligned}$$

Similarly, Eq. (2.63b) leads to
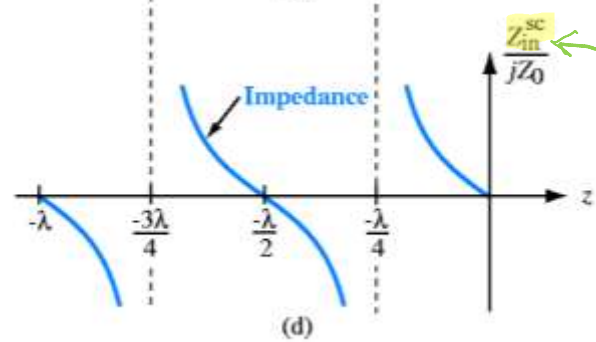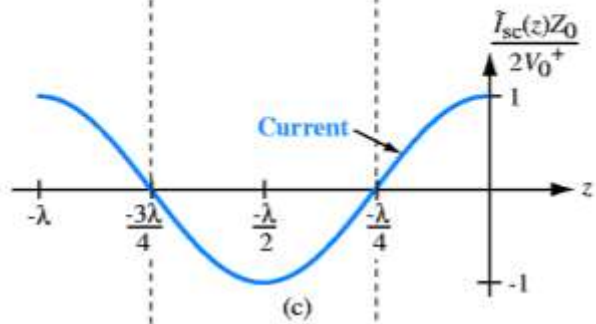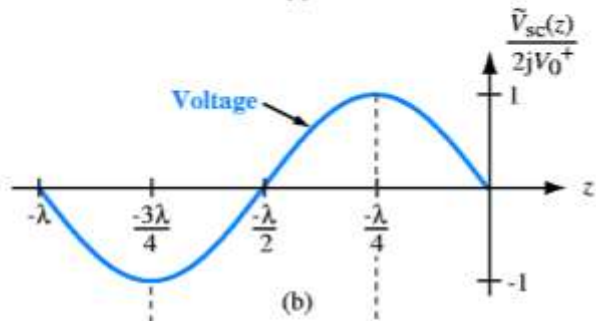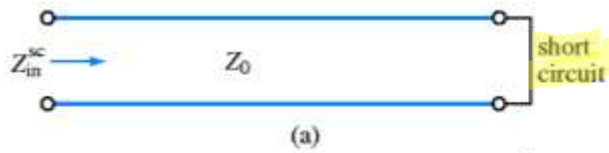
$$\begin{aligned} \tilde{I}(d) &= 0.20e^{j159^\circ} (e^{j\beta d} - 0.45e^{j26.6^\circ} e^{-j\beta d}), \\ i(d, t) &= 0.20 \cos(\omega t + \beta d + 159^\circ) \\ &\quad + 0.091 \cos(\omega t - \beta d + 185.6^\circ) \quad (\text{A}). \end{aligned}$$



Purely Reactive

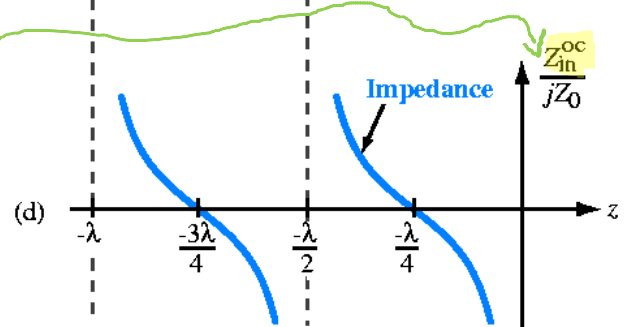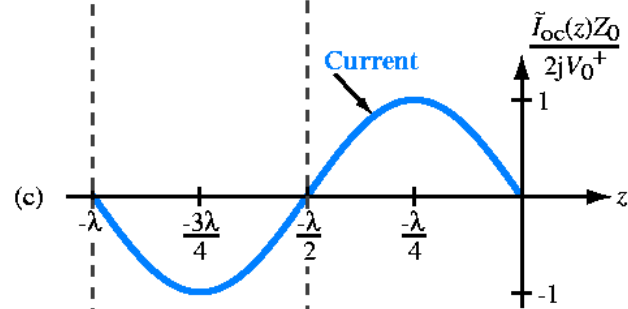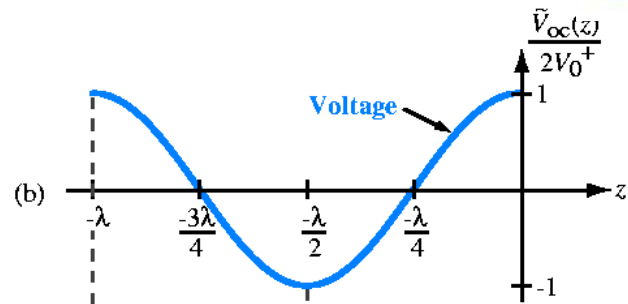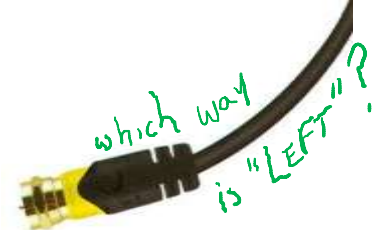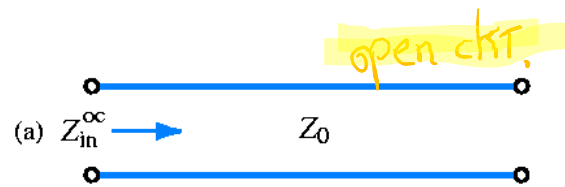

Special Cases

| | |
|--|--|
| Voltage maximum | $ \tilde{V} _{\max} = V_0^+ [1 + \Gamma]$ |
| Voltage minimum | $ \tilde{V} _{\min} = V_0^+ [1 - \Gamma]$ |
| Positions of voltage maxima (also positions of current minima) | $l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$ |
| Position of first maximum (also position of first current minimum) | $l_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$ |
| Positions of voltage minima (also positions of first current maxima) | $l_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$ |
| Position of first minimum (also position of first current maximum) | $l_{\min} = \frac{\lambda}{4} \left(1 + \frac{\theta_r}{\pi} \right)$ |
| Input impedance | $Z_{\text{in}} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) = Z_0 \frac{[1 + \Gamma e^{-j2\beta l}]}{[1 - \Gamma e^{-j2\beta l}]}$ |
| Positions at which Z_{in} is real | at voltage maxima and minima |
| Z_{in} at voltage maxima | $Z_{\text{in}} = Z_0 \left(\frac{1 + \Gamma }{1 - \Gamma } \right)$ |
| Z_{in} at voltage minima | $Z_{\text{in}} = Z_0 \left(\frac{1 - \Gamma }{1 + \Gamma } \right)$ |
| Z_{in} of short-circuited line | $Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$ |
| Z_{in} of open-circuited line | $Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot \beta l$ |
| Z_{in} of line of length $l = n\lambda/2$ | $Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$ |
| Z_{in} of line of length $l = \lambda/4 + n\lambda/2$ | $Z_{\text{in}} = Z_0^2 / Z_L, \quad n = 0, 1, 2, \dots$ |
| Z_{in} of matched line | $Z_{\text{in}} = Z_0 = Z_L$ |
| $ V_0^+ $ = amplitude of incident wave, $\Gamma = \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$; θ_r in radians. | |

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Always check out limiting cases, like $l=0$

Measuring β

$$\tan \beta l = \frac{-Z_{\text{in}}^{\text{sc}}}{Z_{\text{in}}^{\text{oc}}}$$

Beware phase wrap around ambiguity!

Frequency Dependence Matters!

Measuring Z_0

$$Z_0 = \sqrt{Z_{\text{in}}^{\text{sc}} Z_{\text{in}}^{\text{oc}}}$$

for lossless, NOT function of freq.!



=



or



??

Example:

Exercise 2.11 A $50\text{-}\Omega$ lossless transmission line uses an insulating material with $\epsilon_r = 2.25$. When terminated in an open circuit, how long should the line be for its input impedance to be equivalent to a 10-pF capacitor at 50 MHz ?

Solution: For a 10-pF capacitor at 50 MHz ,

Desired Equivalent Capacitance

$$Z_c = \frac{1}{j\omega C} = \frac{-j}{2\pi \times 50 \times 10^6 \times 10 \times 10^{-12}} = -j \frac{1000}{\pi} \Omega$$

$\left\{ \begin{array}{l} Z_L \rightarrow \infty \\ \Gamma = 1 \end{array} \right.$

$\beta = \frac{2\pi}{\lambda} = \frac{2\pi\sqrt{\epsilon_r}}{\lambda_0} = \frac{2\pi f\sqrt{\epsilon_r}}{c}$
 $\Delta m \{ \times \}$

$$= \frac{2\pi \times 5 \times 10^7 \sqrt{2.25}}{3 \times 10^8} = 1.57 \text{ (rad/m).}$$

$\lambda = 4\text{ m}$

For lossless lines with open-circuit termination,

$$Z_{in} = -jZ_0 \cot \beta l = -j50 \cot 1.57l =$$

$$Z_0 \left[\frac{1 + \Gamma e^{-2\beta l}}{1 - \Gamma e^{-2\beta l}} \right]$$

WORKS FOR ANY LOSSLESS LINE!

Hence,

$$-j \frac{1000}{\pi} = -j50 \cot 1.57l$$

$$l = 10 \text{ (cm).}$$

$\pm \sim 1\%$ of λ
 (a question of precision)

Q: Would you use an open or closed ckt. in practice?

or



Lines of Length $l = n\lambda/2$ and $l = n\frac{\lambda}{4}$

* $l = \frac{n\lambda}{2}$ for $n=0,1,2,\dots \Rightarrow Z_{in} = Z_L$, i.e. as if T-Line
HALF-wave Line

Note: For Lossless and single freq.

* $l = n\frac{\lambda}{4}$ for $n=1,3,5,\dots \Rightarrow Z_{in} = Z_0^2 / Z_L$
QUARTER wave Line

Example

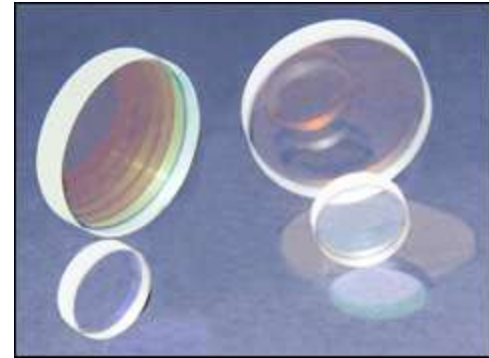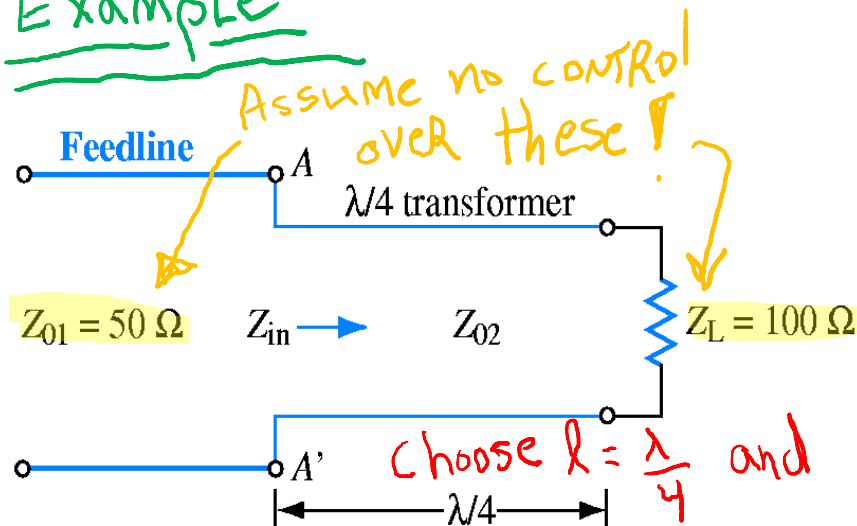


$$Z_{02} = \sqrt{100 \Omega \times 50 \Omega} = 70.7 \Omega$$


Why?

If length is *SHORT*, what is Z_{in} ??
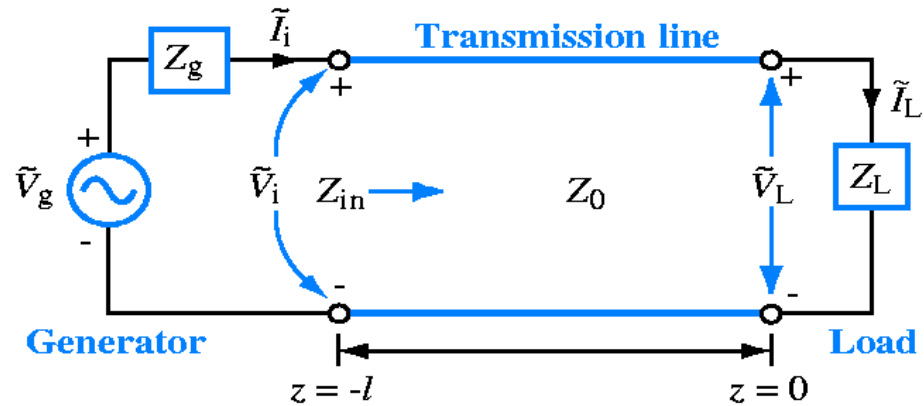
$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$$



$$\beta l \ll 1$$

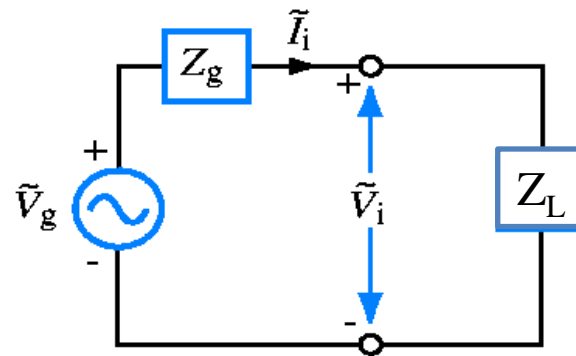

It's a T-line if:
 $\frac{l}{\lambda} \sim \frac{fl}{c} \gtrsim 1\% \Rightarrow 3\text{MHz} \sim \text{m's}$
 $3\text{GHz} \sim \text{mm's}$



Power


Instantaneous Power

$$\Leftrightarrow v_i(t) i_i(t)$$

Time Domain

$$= \frac{|V_o^+|^2}{Z_o} \cos^2(\omega t + \phi^+)$$

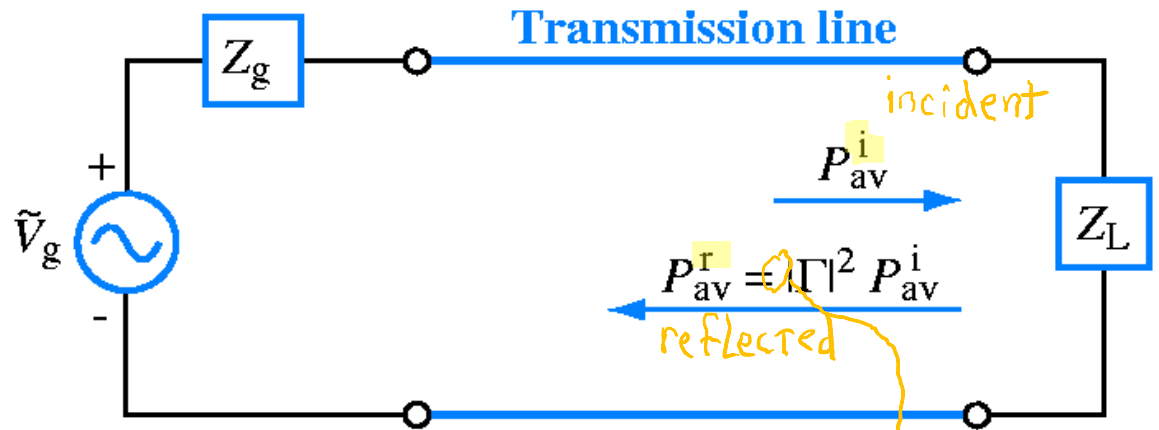using phasor #'s, but
still in time domain!



Time-Average Power

$$P_{av}^i = \frac{|V_o^+|^2}{2 Z_o} \text{ W, } P_{av}^r = -|\Gamma|^2 P_{av}^i$$

depends on
how you define
direction...


$$= \frac{1}{2} \text{Re}[\tilde{V} \cdot \tilde{I}^*]$$

phasor domain

Note: Power delivered to Load is $P_{AV}^i - P_{AV}^r$




Lecture 7

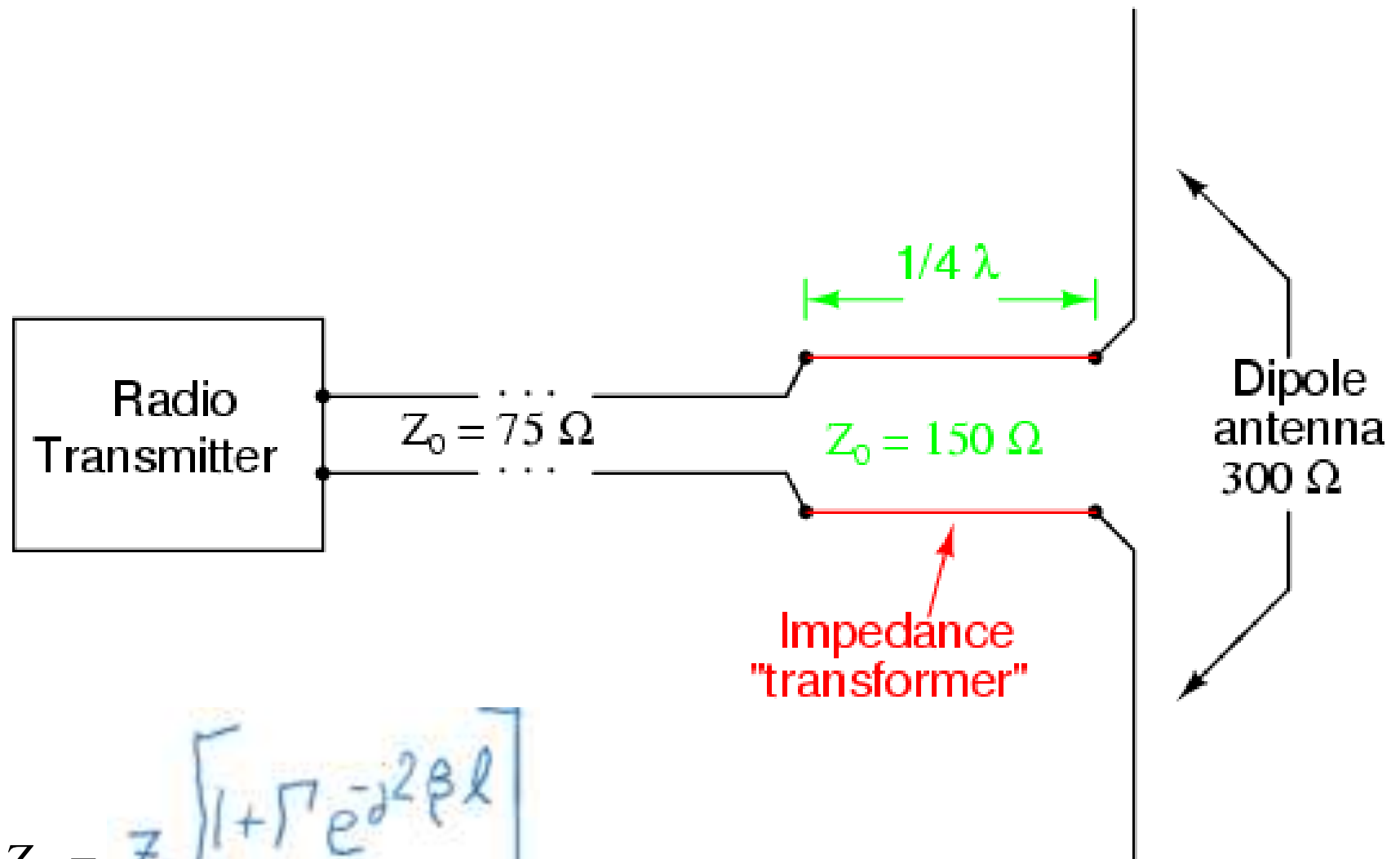

$$Z_{in} = Z_0 \left[\frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right]$$


or
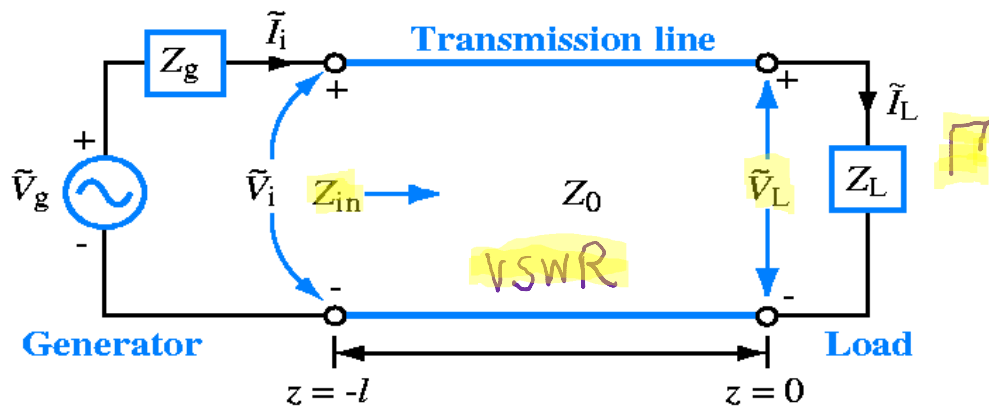
$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$$



Why?

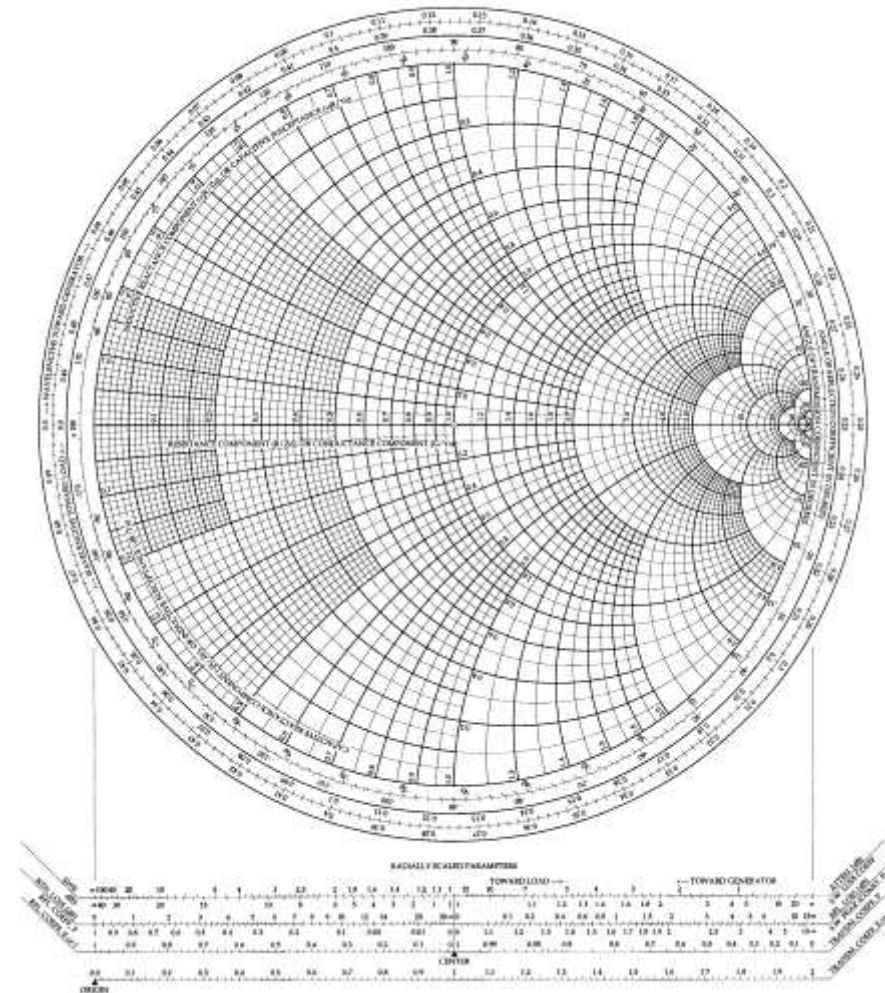The Complete Smith Chart
Black Magic Design



Smith's Chart

What is Smith's chart?

A graphical tool.

Purpose of introducing Smith's chart: To avoid heavy math and speed up the process of analyzing and designing transmission line circuits.

How is it constructed?

On the basis of the reflection coefficient plane.


$$\Gamma = |\Gamma| e^{j\theta_\Gamma} = \Gamma_r + j\Gamma_i, \quad \text{where } \Gamma_r = \text{Re}\{\Gamma\} \text{ and } \Gamma_i = \text{Im}\{\Gamma\}$$

Only a circle of radius 1 has a meaning since $|\Gamma| \leq 1$

Any point within the unit circle represents certain reflection coefficient.

Smith's chart works with normalized impedances and admittances:


$$z(z) = \frac{Z(z)}{Z_0}$$

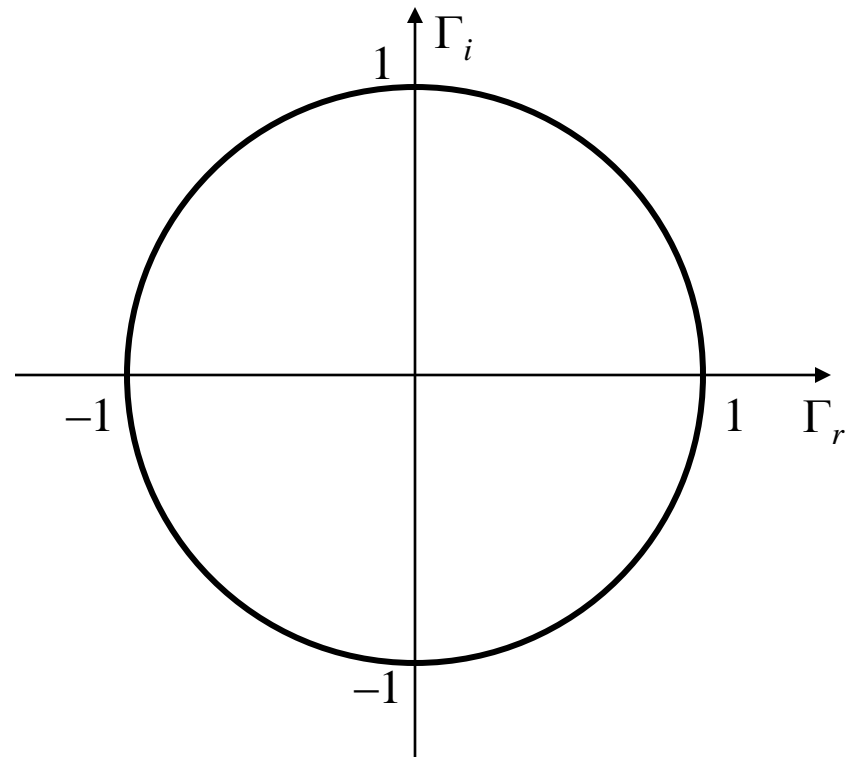

You CAN do it all with a computer of course...

$$\Gamma = \text{Reflection coeff.} = |\Gamma| e^{j\theta_R} = \Gamma_r + j\Gamma_i$$

≤ 1

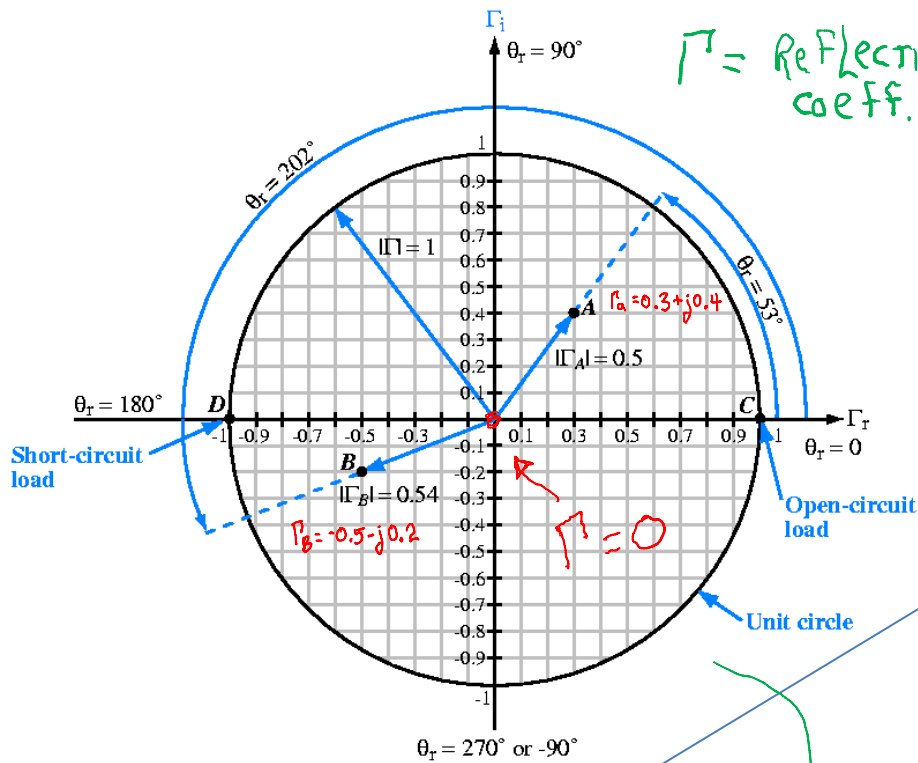

Normalized Impedance

Resistance
Reactance

$$z_L = \frac{Z_L}{Z_0} = \frac{R_L + jX_L}{Z_0} = r_L + jx_L$$

normalize to line impedance, Z_0

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \left(\frac{1/Z_0}{1/Z_0} \right) = \frac{z_L - 1}{z_L + 1}$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma}$$

conductance
susceptance

$$Y = \frac{1}{Z} = G + jB$$

Admittance


$$Z_L = r_L + jx_L = \frac{Z_L}{Z_0}$$

Inductance \uparrow
Capacitance \downarrow

$$\Gamma = \frac{Z_L - 1}{Z_L + 1}$$

$$\text{w/ } Z_L = 1 + j2$$

$$\Rightarrow \Gamma = \frac{1}{2} + \frac{j}{2} = 0.7 \angle 45^\circ$$

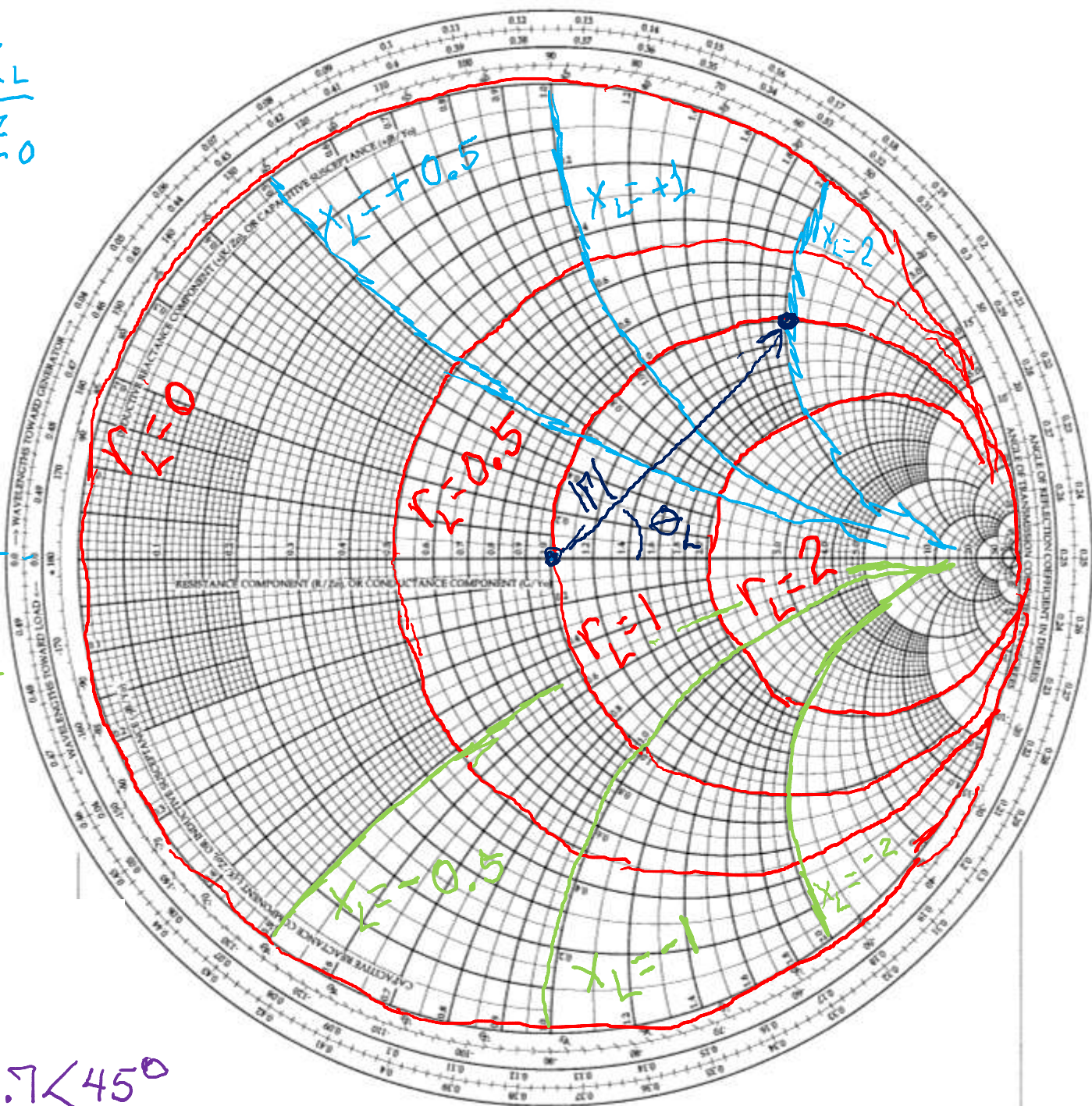


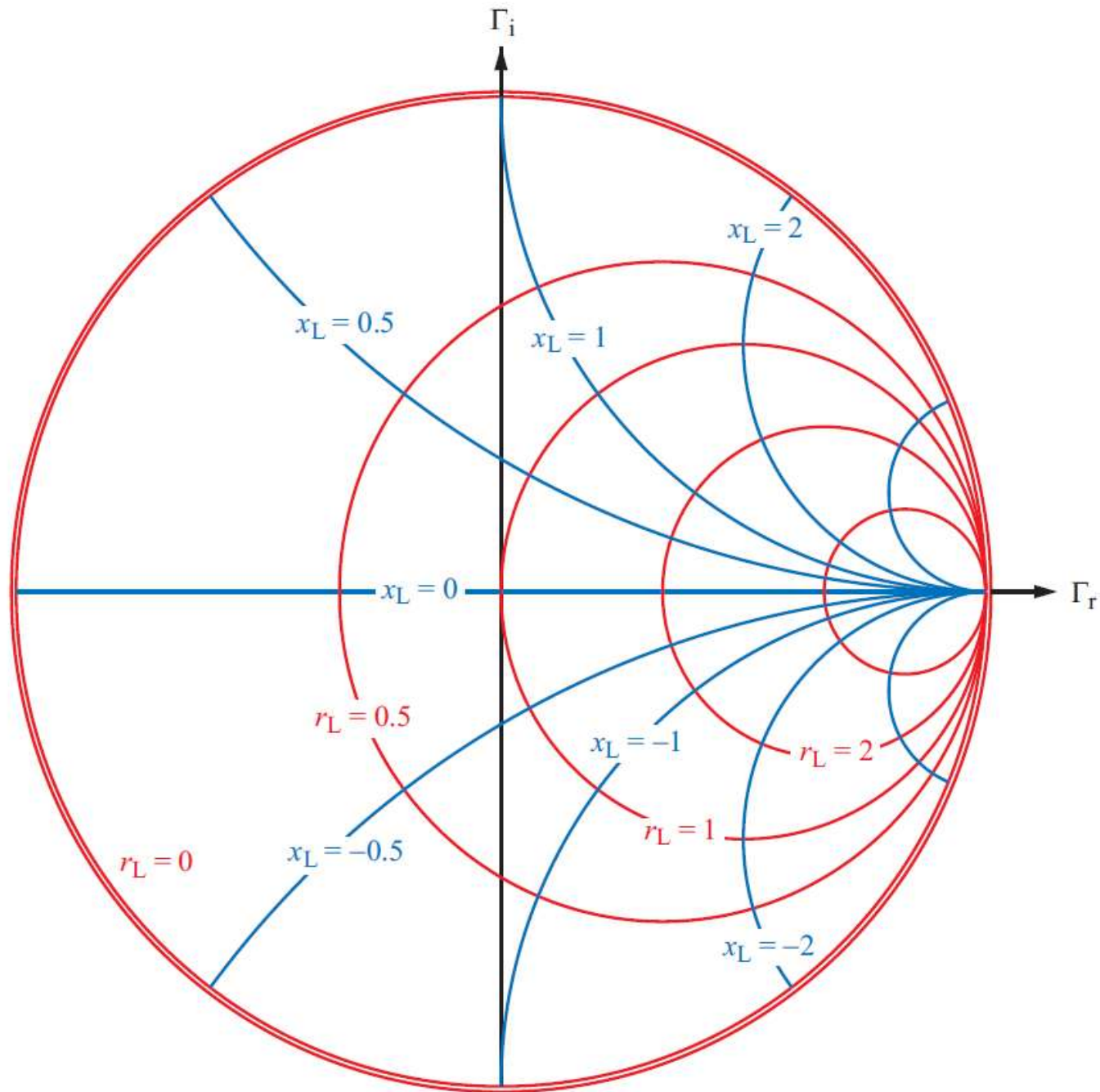


Figure 2-25: Families of r_L and x_L circles within the domain $|\Gamma| \leq 1$.

Load Impedance (with line impedance 50 Ohms)

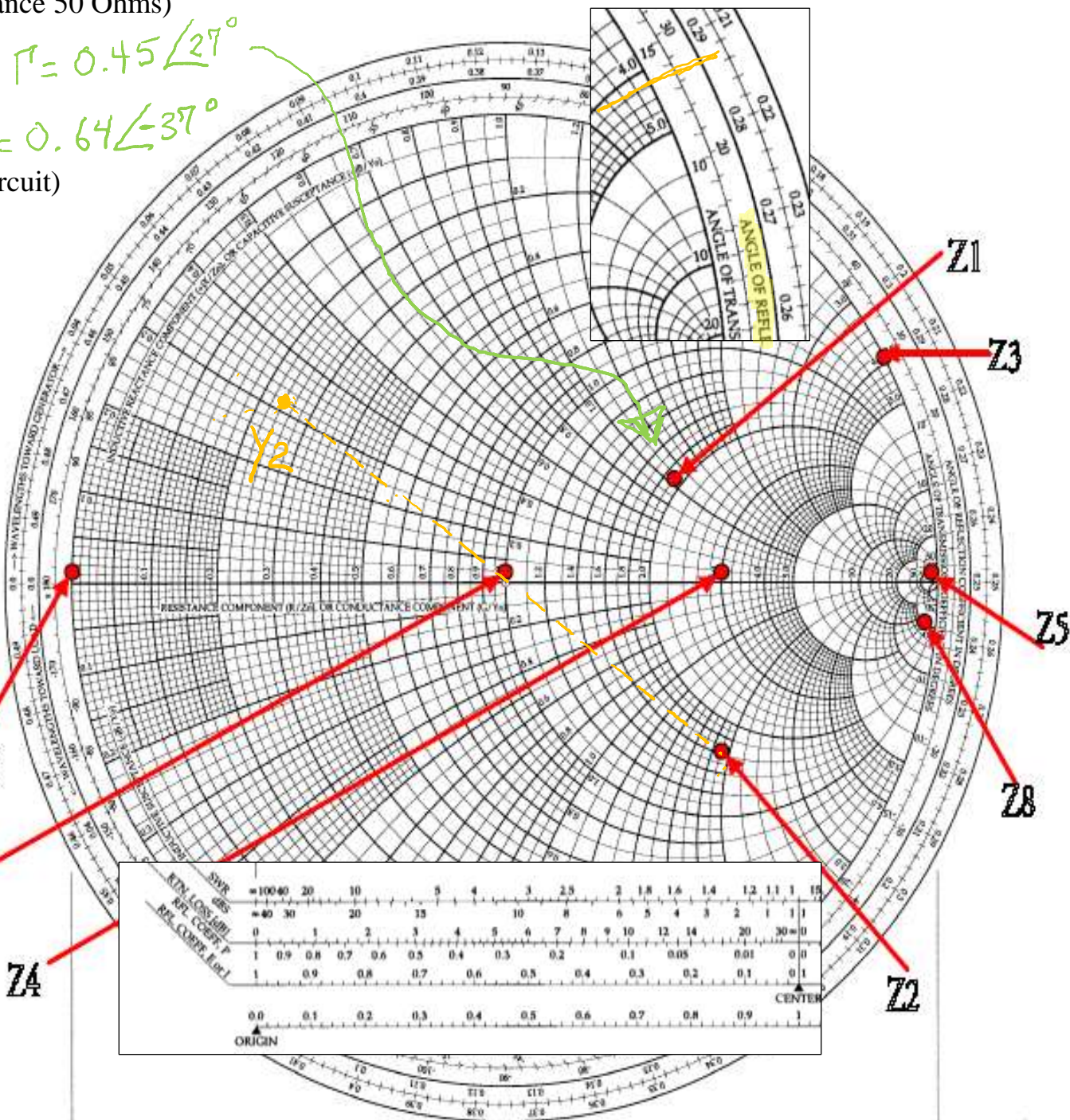- $Z1 = 100 + j50$
- $Z2 = 75 - j100$
- $Z3 = j200$
- $Z4 = 150$
- $Z5 = \text{infinity}$ (an open circuit)
- $Z6 = 0$ (a short circuit)
- $Z7 = 50$
- $Z8 = 184 - j900$



Admittance

$$Y = \frac{Y}{Y_0} = g + jb$$

rotate r_L around
"origin" by 180°
to get Y_L

Ex:

$$Y_2 = \frac{1}{Z_2} = 0.24 + j0.32$$


If a generalized reflection coefficient at an arbitrary point on the transmission line is defined as $\Gamma(z) = |\Gamma|e^{j(\theta_r + 2\beta z)}$, then the normalized impedance at that point can be expressed through the generalized reflection coefficient the same way the normalized load impedance is expressed in terms of the reflection coefficient at the load:


$$z(z) = \frac{Z(z)}{Z_0} = \frac{1 + \Gamma e^{-j2\beta z}}{1 - \Gamma e^{-j2\beta z}} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

This observation suggests that Smith's chart can be used to represent the impedance at any point on the line.

The reflection coefficient along a particular transmission line maintains its magnitude; only its phase changes. Therefore, the normalized impedance at any point on the transmission line must lie on a circle with radius $|\Gamma|$.

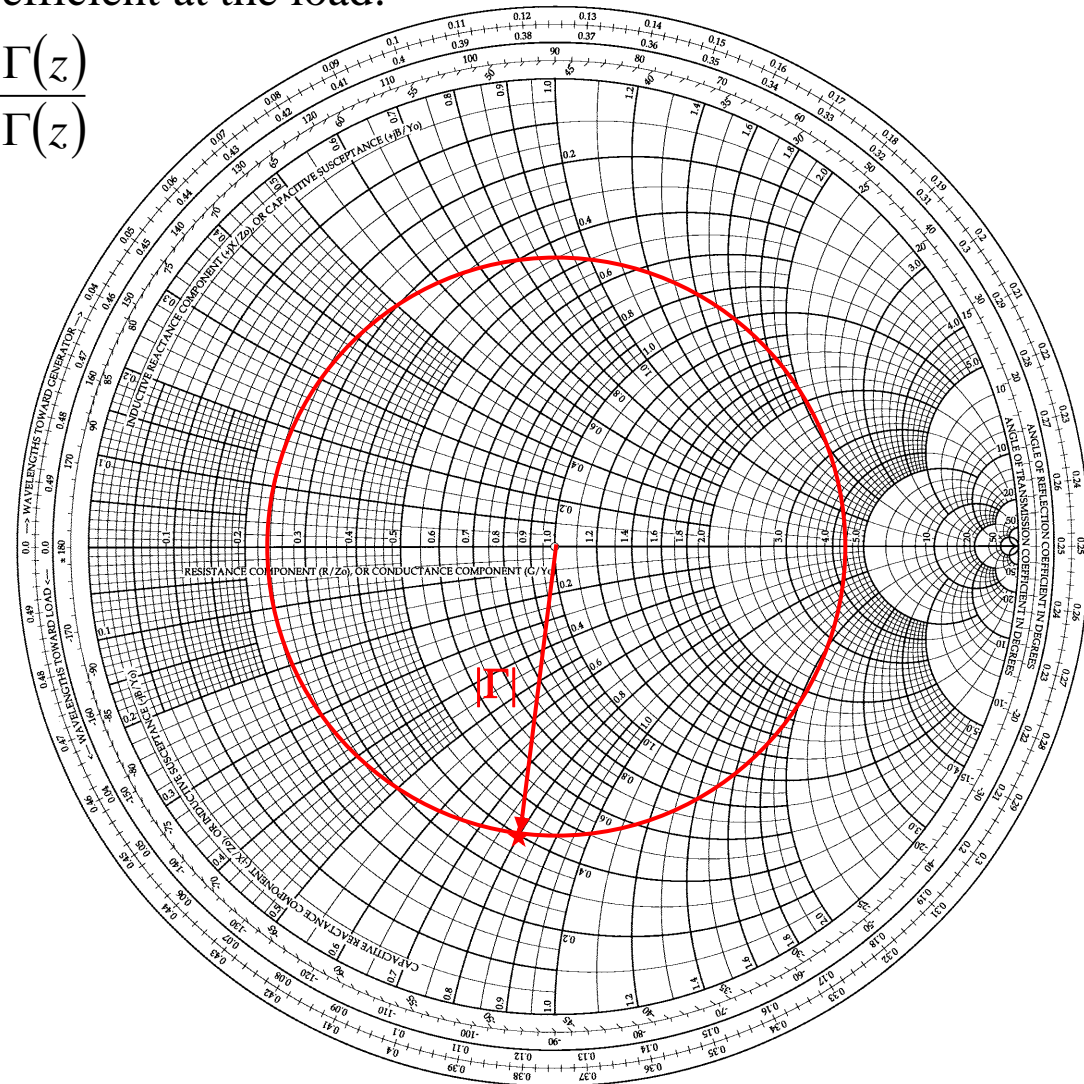Also, it is obvious that the impedance on the line repeats itself every $\lambda/2$ length of the line. Therefore, the Smith chart represents a $\lambda/2$ -long section of a transmission line.





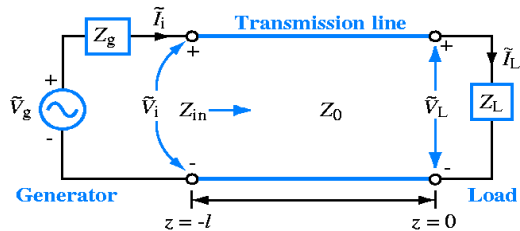

$$Z_{in} = \frac{Z_{in}}{Z_0} = \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{+j2\beta l}}, \quad \text{w/ } \beta = \frac{2\pi}{\lambda} \leftarrow \text{wavelength}$$

Map Z_L around
clockwise on
CONSTANT $|\Gamma|$
contour
by $\frac{l}{\lambda}$ to get

Z_L

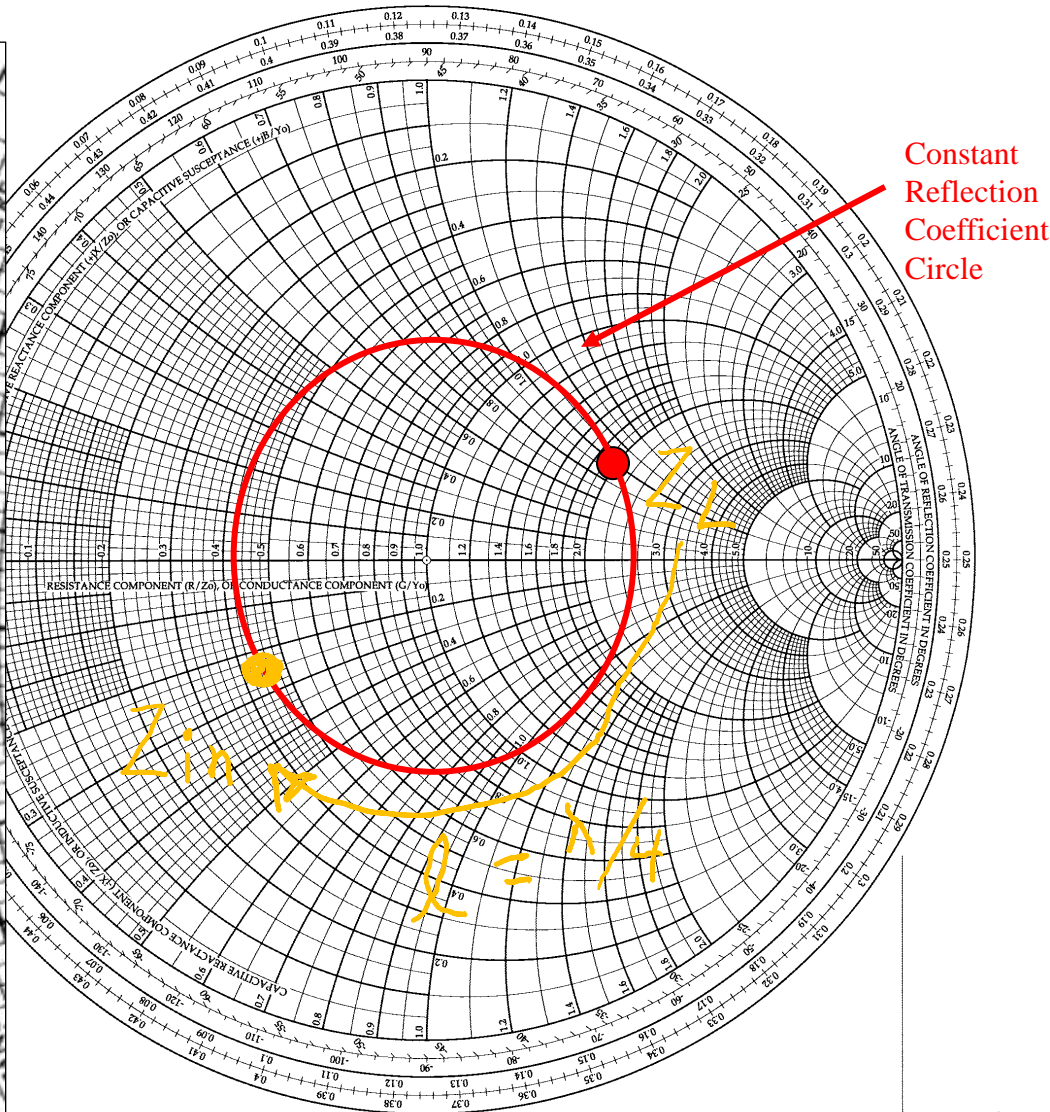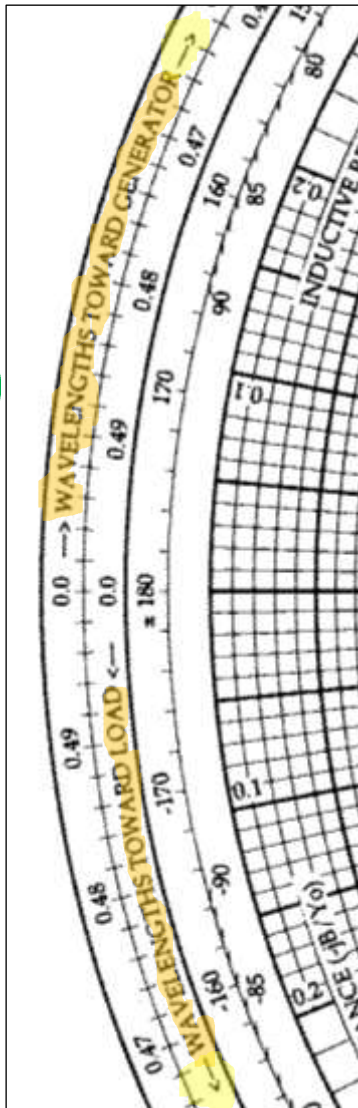

Full Circle is One Half Wavelength Since Everything Repeats

Standing Wave Ratio (SWR)



$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

SWR circle

P_{max} & P_{min} are points, not power


wavelengths to 1st minimum from Load #1

* Two independent examples

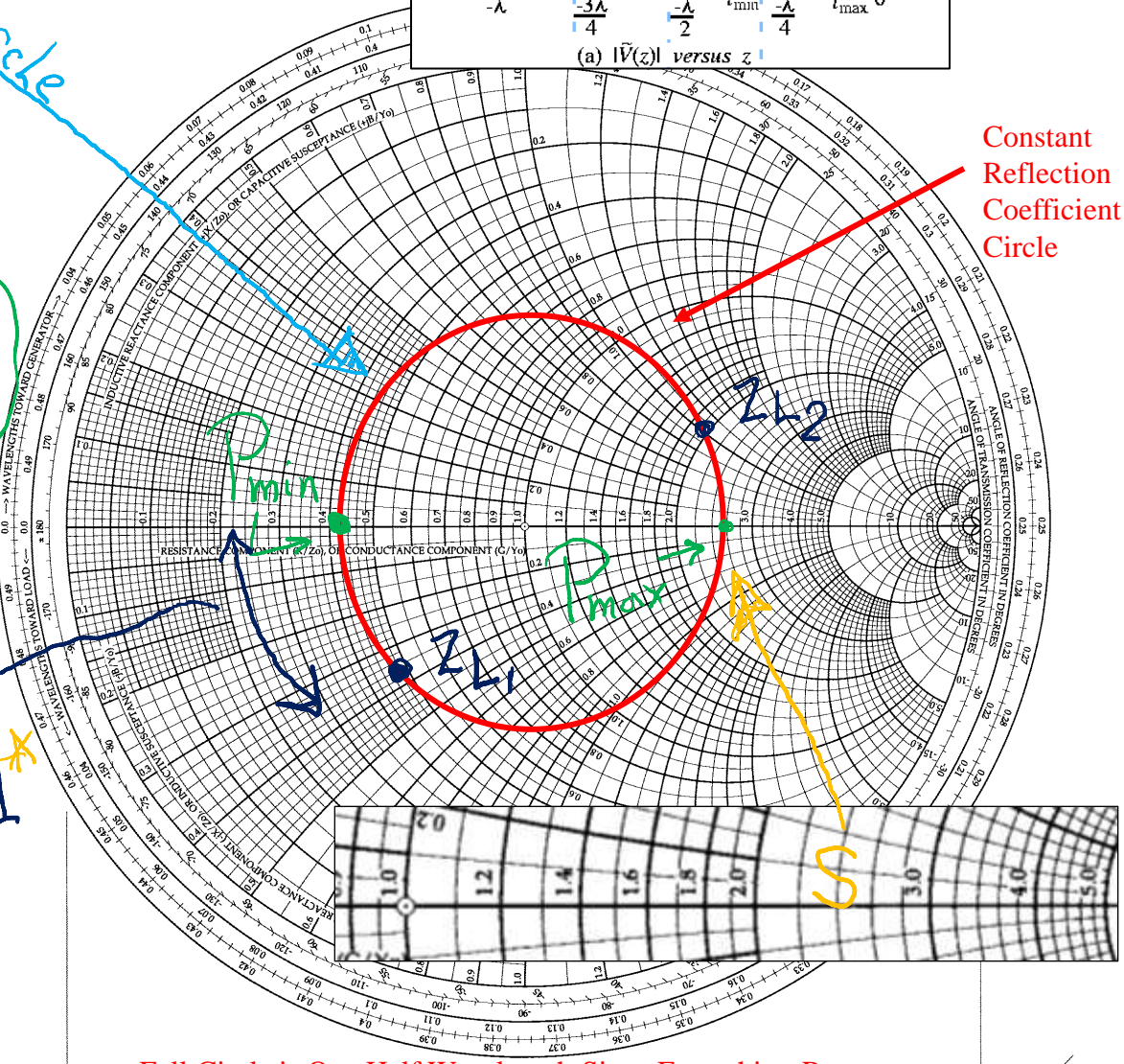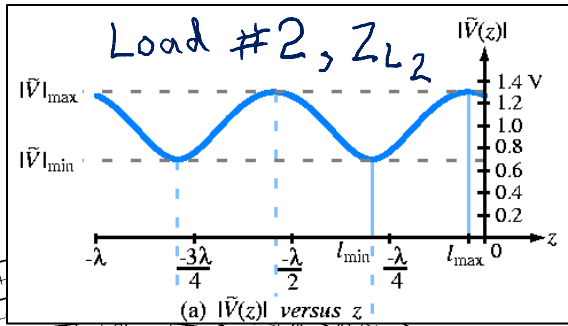

Full Circle is One Half Wavelength Since Everything Repeats

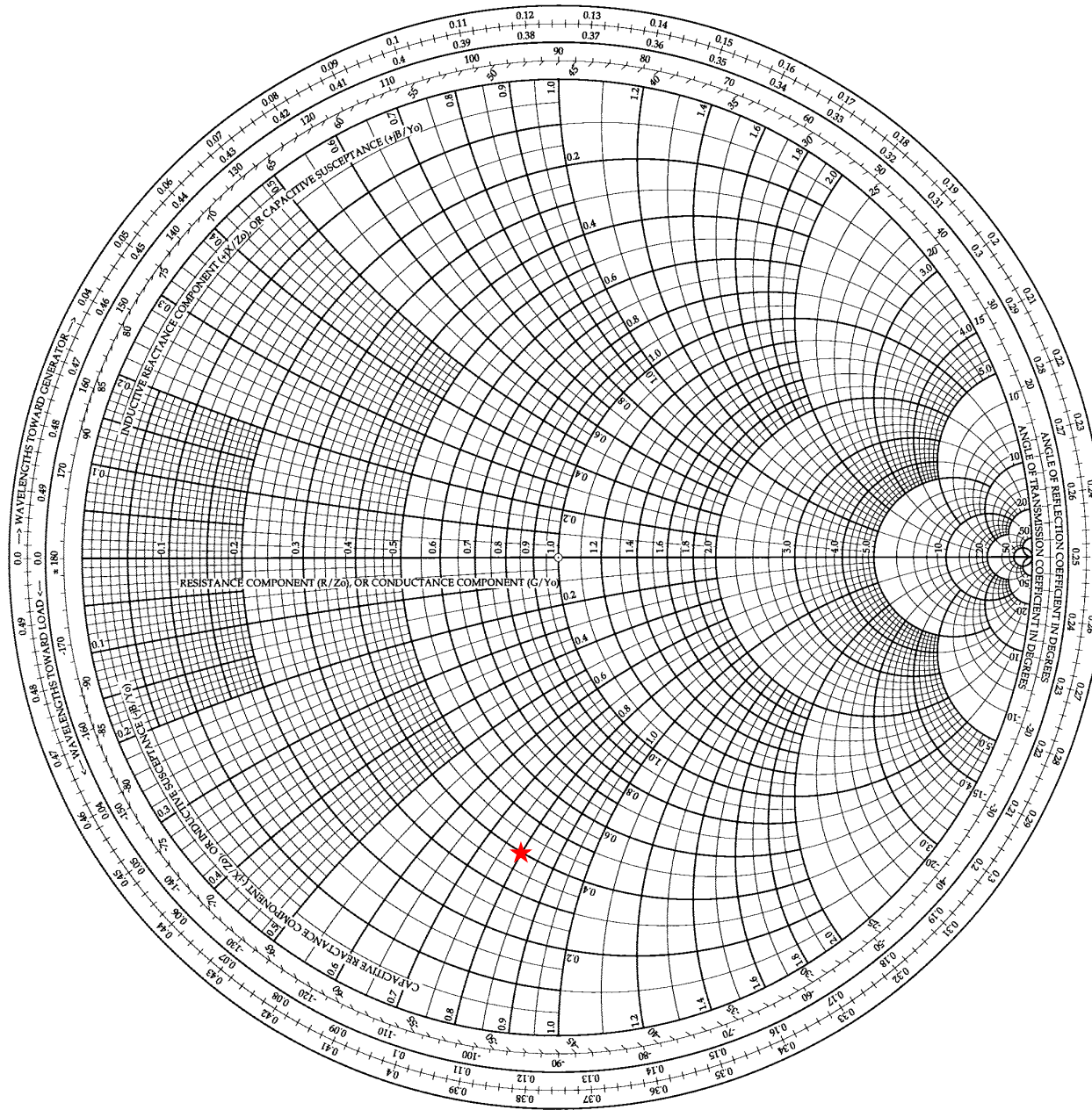Smith chart actually makes problems easier where you want a specific Z_{in} !!!!!



Examples:

Determine the load impedance denoted by the red star on the chart if this load terminates a 50- Ω transmission line.

The point represents

$$z_L = 0.4 - j0.8$$

Then

$$Z_L = z_L Z_0 = 20 - j40 \, \Omega$$

relative position of the point of interest

l_n

relative position of the load

Example:

Consider the load impedance from the previous example. Determine the impedance 20 cm away from the load if the signal wavelength on the line is 1 m.

$$z_L = 0.4 - j0.8$$


$$\text{Rel. pos. load} = 0.385$$

$$\Delta l = 20 \text{ cm} \Rightarrow l_n = \frac{\Delta l}{\lambda} = \frac{0.2}{1} = 0.2$$

$$\text{Rel. pos. } z = 0.385 + 0.2 = 0.585$$


$$z(-l_n) = 0.31 + j0.55$$
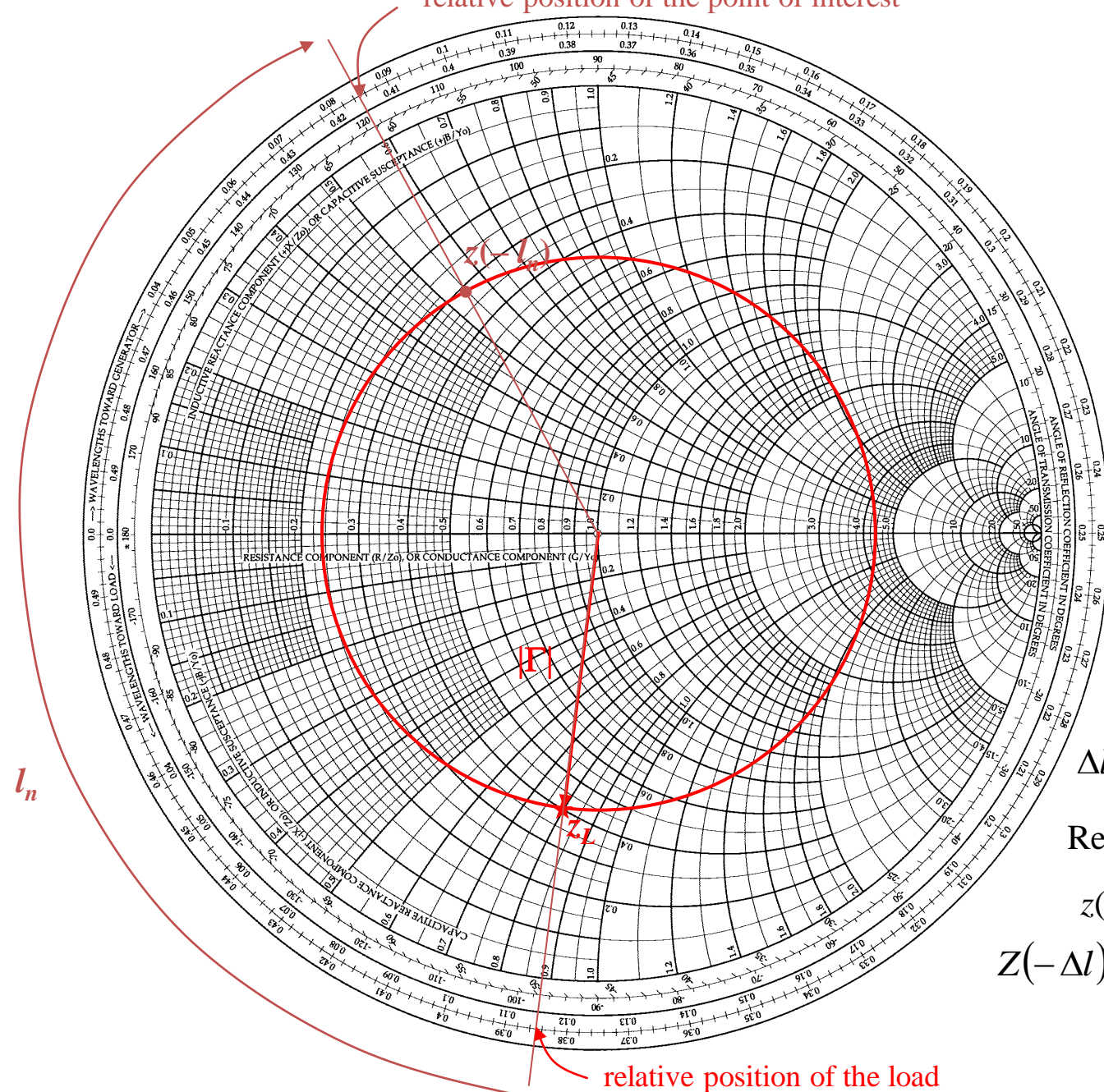
$$Z(-\Delta l) = Z_0 z(-l_n) = 15.5 + j27.5 \Omega$$



http://en.wikipedia.org/wiki/Smith_chart

<http://www.microwaves101.com/encyclopedia/smithchart.cfm>

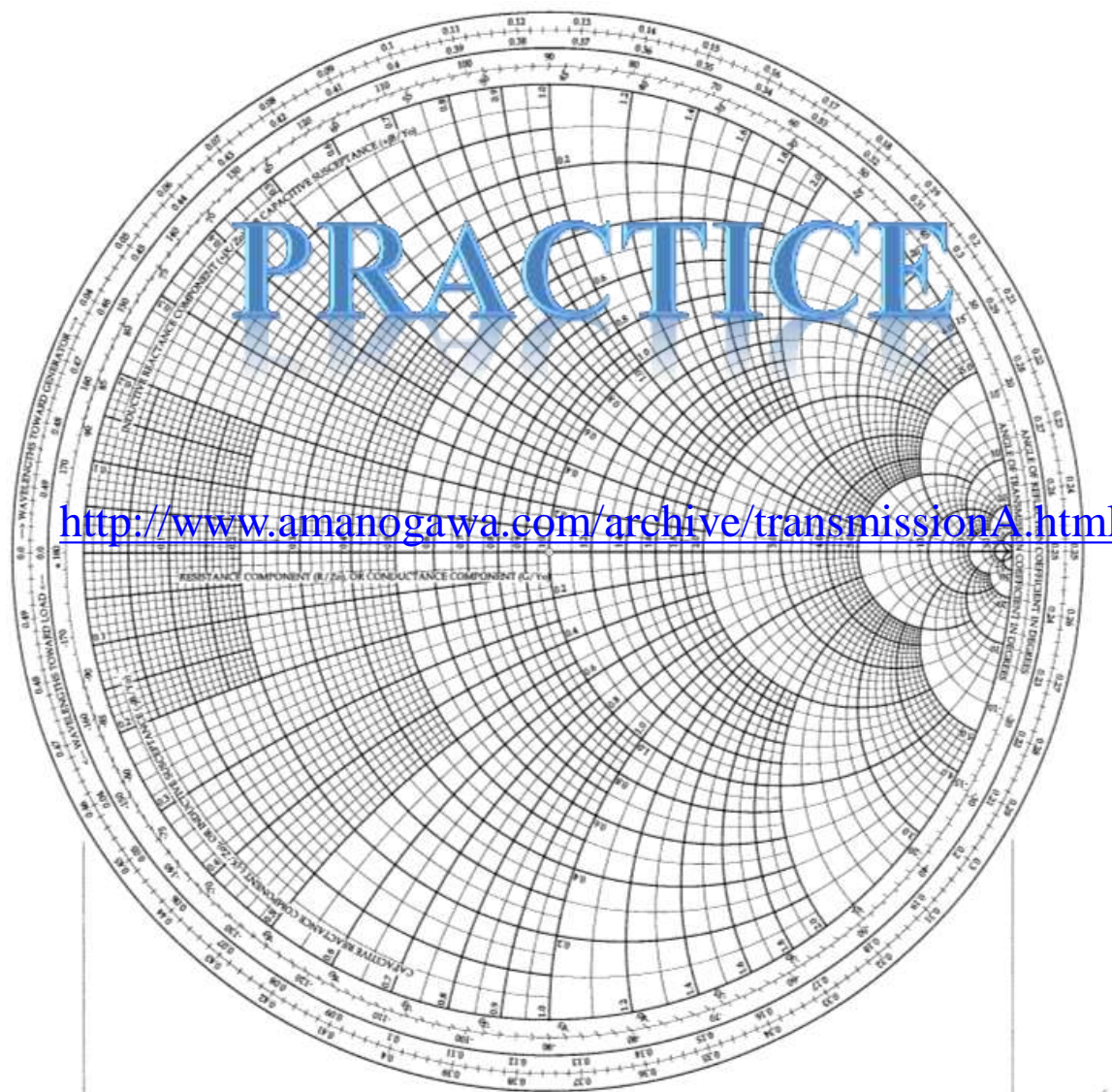

Example 2-11: Smith Chart Calculations

A $50\text{-}\Omega$ lossless transmission line of length 3.3λ is terminated by a load impedance $Z_L = (25 + j50)\text{ }\Omega$.

$$z_L = \frac{Z_L}{Z_0} = \frac{25 + j50}{50} = 0.5 + j1$$

(a)


$$d_{\max} = (0.25 - 0.135)\lambda = 0.115\lambda$$

$$d_{\min} = (0.5 - 0.135)\lambda = 0.365\lambda$$


(b)

$$z_{\text{in}} = 0.28 - j0.40$$

$$Z_{\text{in}} = z_{\text{in}} Z_0 = (0.28 - j0.40)50 = (14 - j20)\text{ }\Omega$$

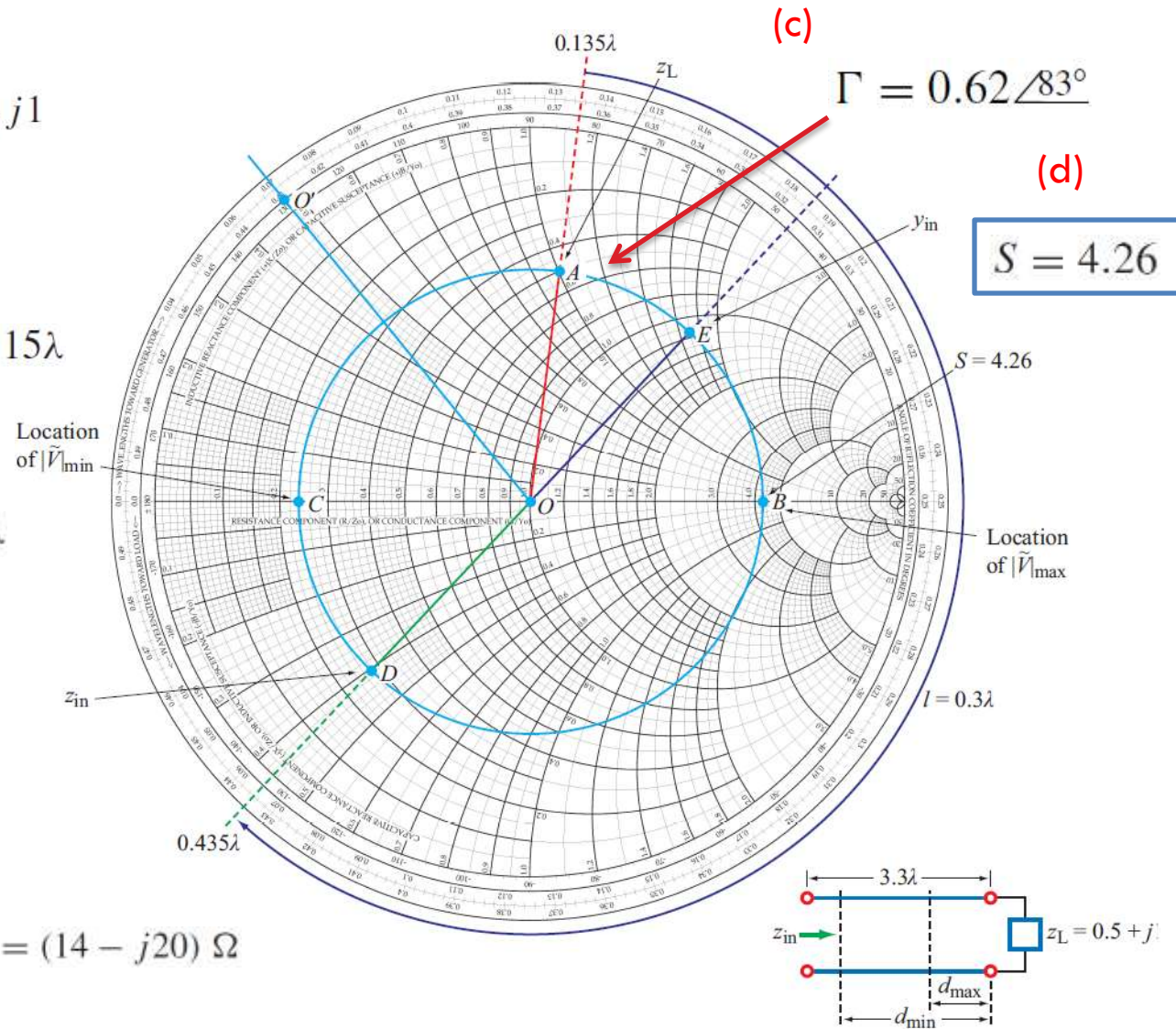


Lecture 8

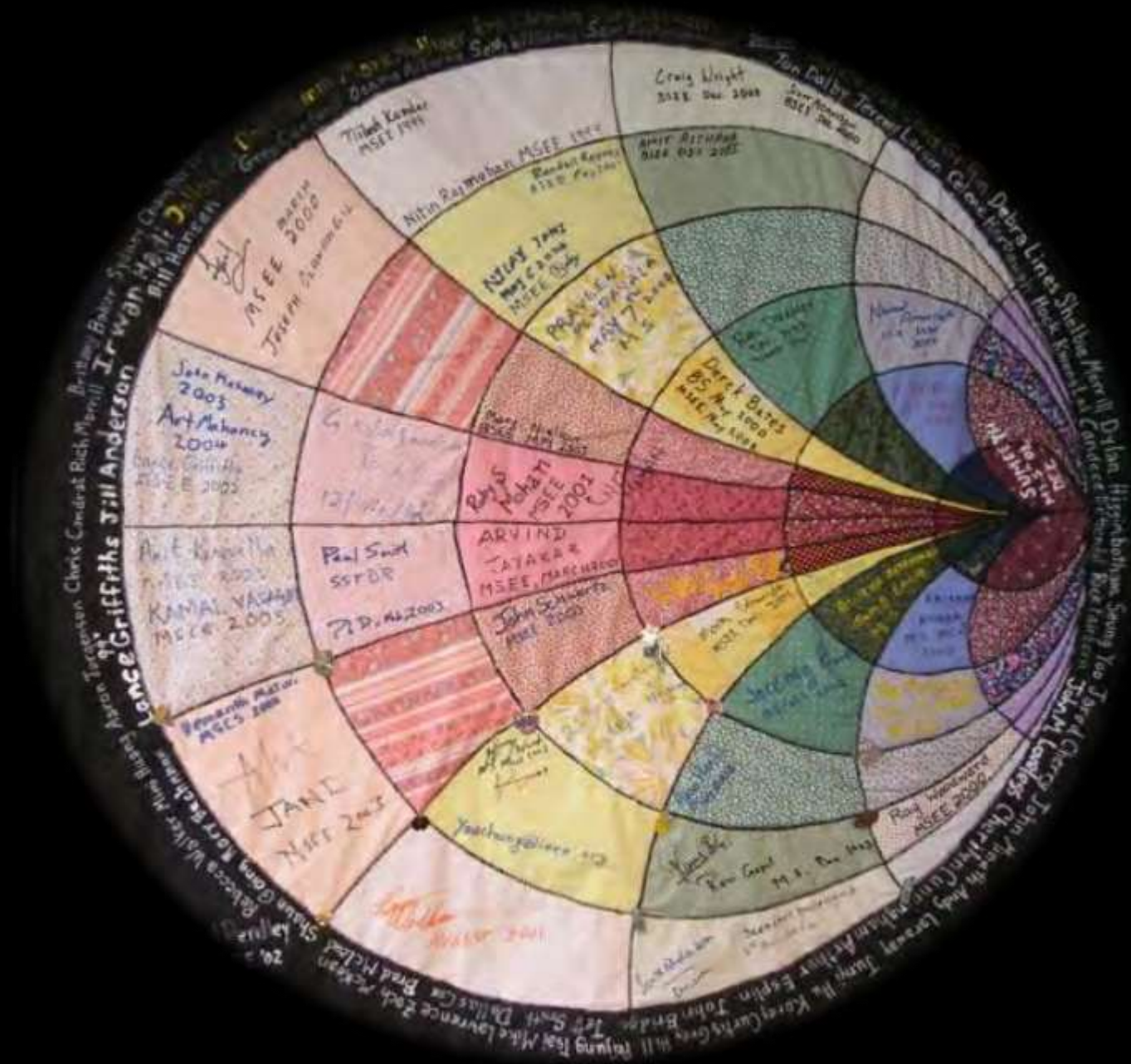

This quilt was made by Cynthia Furse, a Professor in the Department of Electrical and Computer Engineering at Utah State University. She has her students sign when they have finished their MS or BS design projects.

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu\varepsilon}} = \frac{c}{\sqrt{\varepsilon_r}} = f\lambda$$

$$\lambda = \frac{2\pi}{\beta}$$

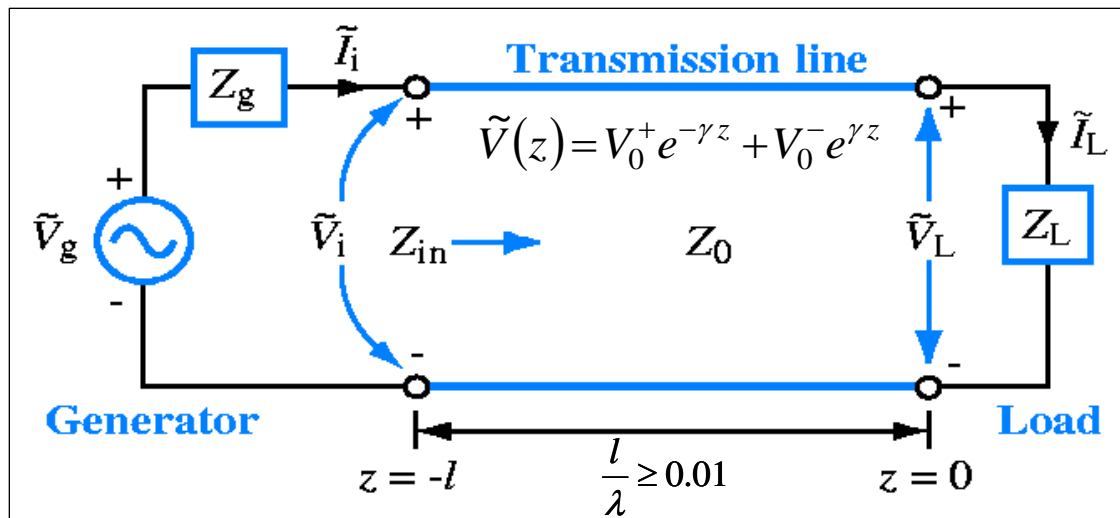

$$v(z, t) = |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_0^-| e^{\alpha z} \cos(\omega t + \beta z + \phi^-)$$

$$\gamma = \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$\frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} = Z_o = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$S = \frac{|\tilde{V}(z)|_{\max}}{|\tilde{V}(z)|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$Z_{in} = Z(-l) = \frac{\tilde{V}(-l)}{\tilde{I}(-l)} = Z_0 \left[\frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \right] = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$$

Given: $Z_L = (120 - j60) \Omega$, $Z_0 = 300 \Omega$
and $\ell = 0.8\lambda$

Find: Z_{in} , Γ , VSWR

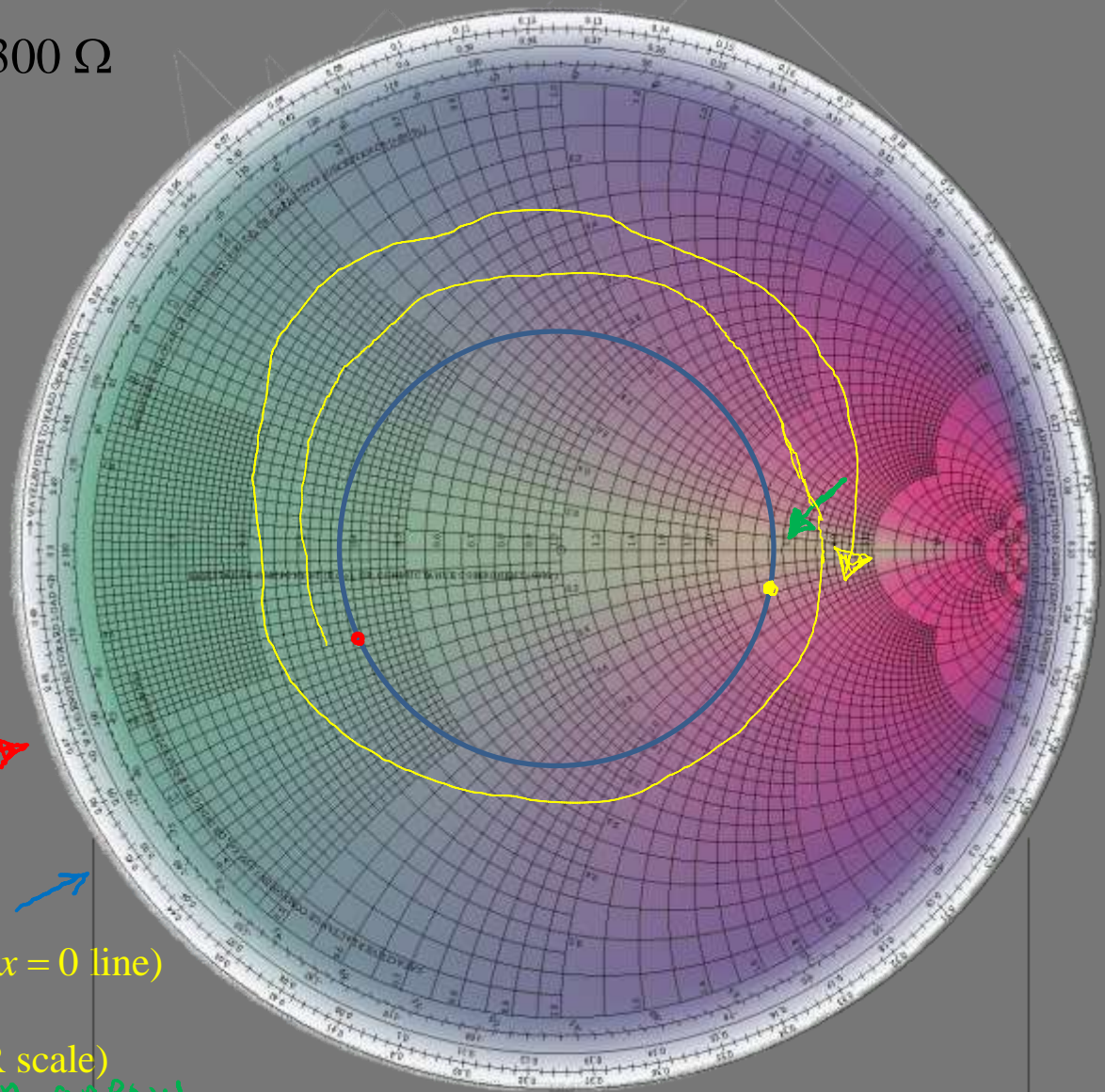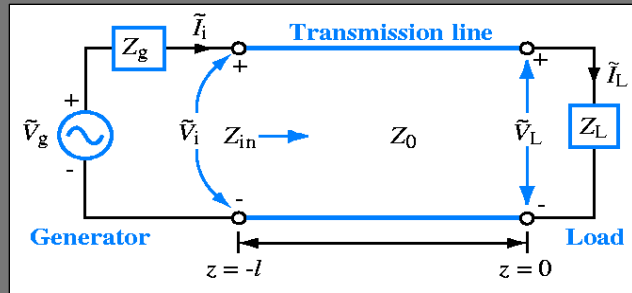

1) normalize: $z_L = \frac{120 - j60}{300} = 0.40 - j0.20$

2) locate point: (to lower left of center)
on $r_L = 0.40$ circle and $x_L = -0.20$ curve

3) $\Gamma = \frac{z_L - 1}{z_L + 1} = 0.45 \angle -153^\circ$

Radius of circle


(can verify $|\Gamma|$ on RFL COEFF scale or $x = 0$ line)

4) $VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1.45}{0.55} = 2.6$ (or by SWR scale)
see green arrow


5) rotate Γ_L $2\beta l = 2(288^\circ) = 576^\circ = (360^\circ + 216^\circ)$ ~~←~~ one time around Smith Chart is 0.5λ
to get $\Gamma_{in} = |\Gamma| e^{j(\phi - 2\beta l)} \Rightarrow z_{in} = 2.52 - j0.46$ (to lower right of center) → Yellow Dot

6) Un-normalize: $Z_{in} = (2.52 - j0.46)(300 \Omega) = (755 - j138) \Omega$

SUNDRIES

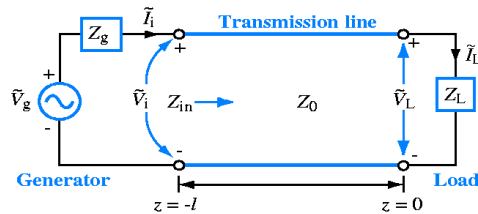

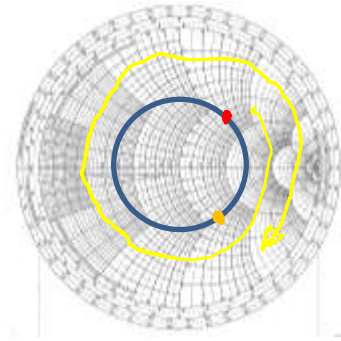
- What does a complex Γ actually mean?
- What does " Γ " changing as it moves toward the generator mean?



$$\cot^{-1}(x) = \tan^{-1}\left(\frac{1}{x}\right) \neq \frac{1}{\tan^{-1}(x)}$$

$$\cot(\beta l) \text{ in Radians}$$

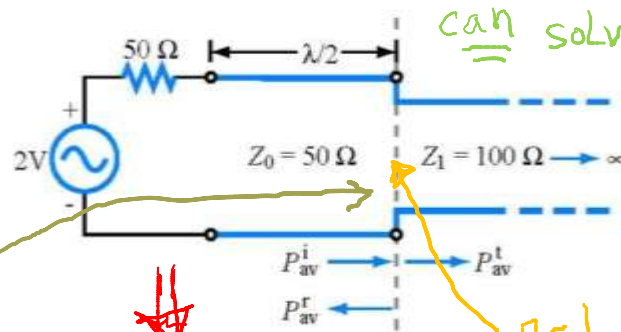There is often more than one way to solve these problems!



can solve using V_o^+ , etc.

$\Gamma = \frac{1}{3}$ why?

$Z_{in} = 100 \Omega$ why?



Power "absorbed" by Z_{in} equals P_{av}^t why?

(Note: this takes into account multiple bounces!)


$$\left. \begin{aligned} P_{AV}^i - P_{AV}^r &= P_{AV}^t \\ P_{AV}^r &= |\Gamma|^2 P_{AV}^i \end{aligned} \right\} \begin{matrix} W \\ h \\ Y? \end{matrix}$$

Q: Does this situation ever happen?


Impedance Matching

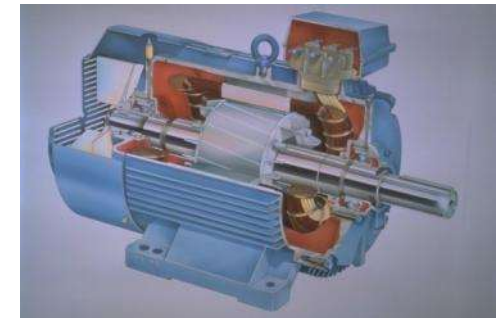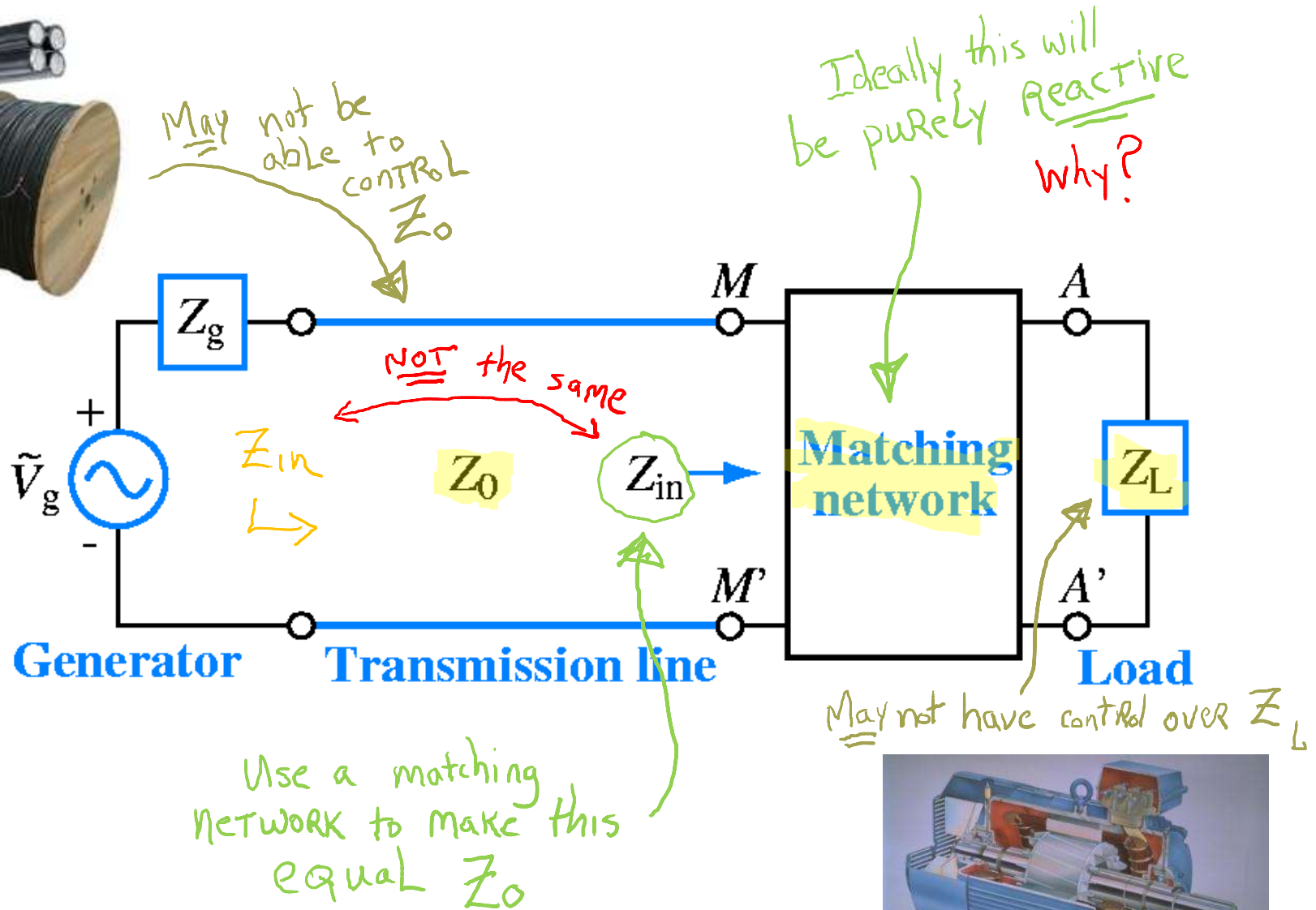


Examples of Matching Networks

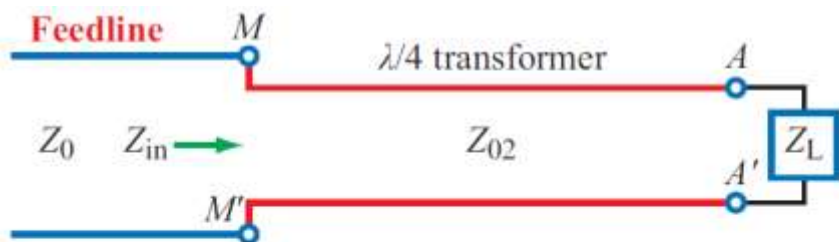

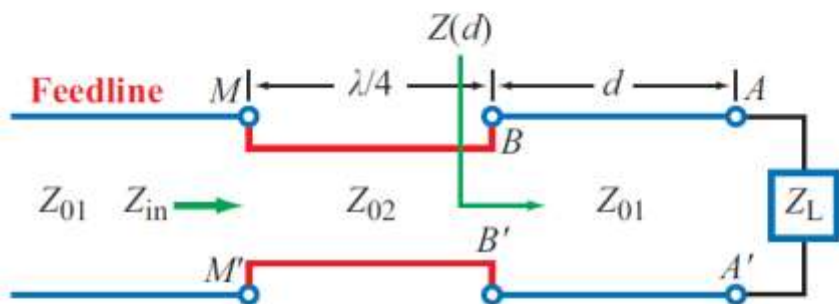
(a) In-series $\lambda/4$ transformer inserted at AA'



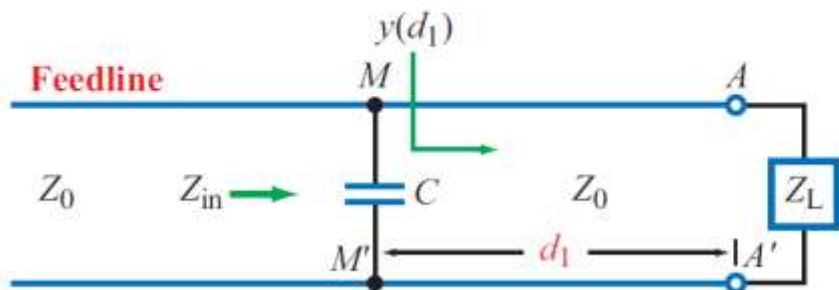
(b) In-series $\lambda/4$ transformer inserted at $d = d_{\max}$ or $d = d_{\min}$



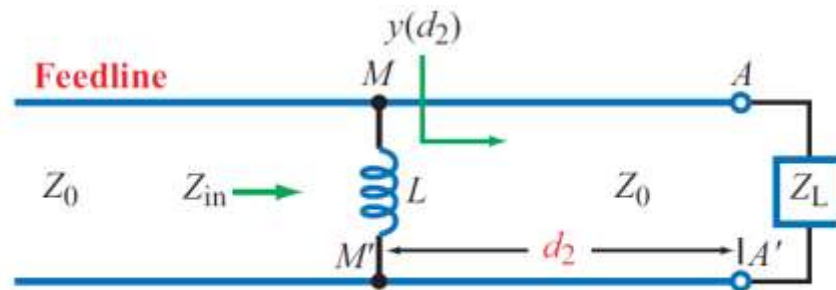(c) In-parallel insertion of capacitor at distance d_1



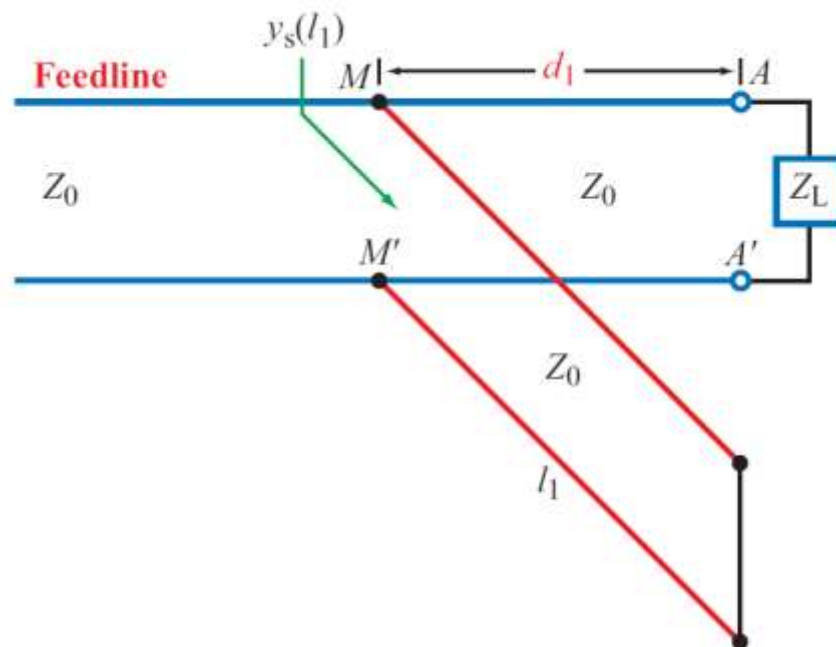(d) In-parallel insertion of inductor at distance d_2



(e) In-parallel insertion of a short-circuited stub

Single-Stub Impedance Matching

The power absorbed by the load is maximum (100% of the incident power) when the transmission line is matched, i.e., the load impedance equals the characteristic impedance, $Z_L = Z_0$.


Unfortunately, often $Z_L \neq Z_0$

Fortunately, there are means to match the load to the transmission line via impedance-matching network.

One of the possibilities is:

Single-stub matching using a short-circuited section of a transmission line.

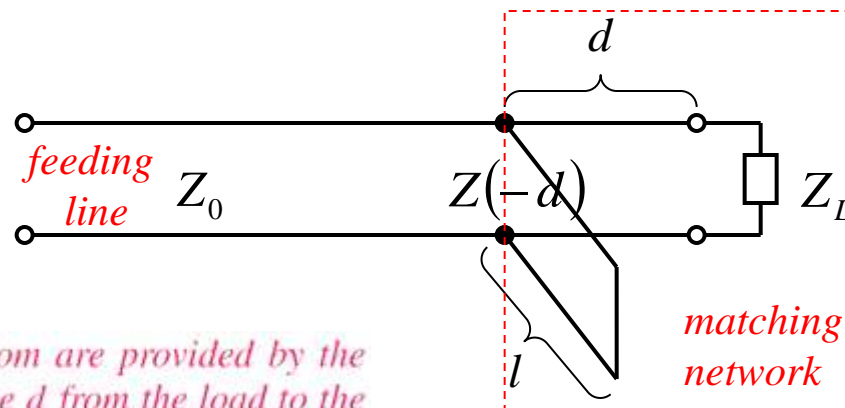
Essentially, a short-circuited section of the same type transmission line as the feeding (main) line is connected in parallel to the main line at a position that is relatively close to the load. The point of connection and the length of the short-circuited stub can be chosen in such a way so that to ensure an input impedance $Z(-d) = Z_0$ of the matching network that contains the load.




The required two degrees of freedom are provided by the length l of the stub and the distance d from the load to the stub position.

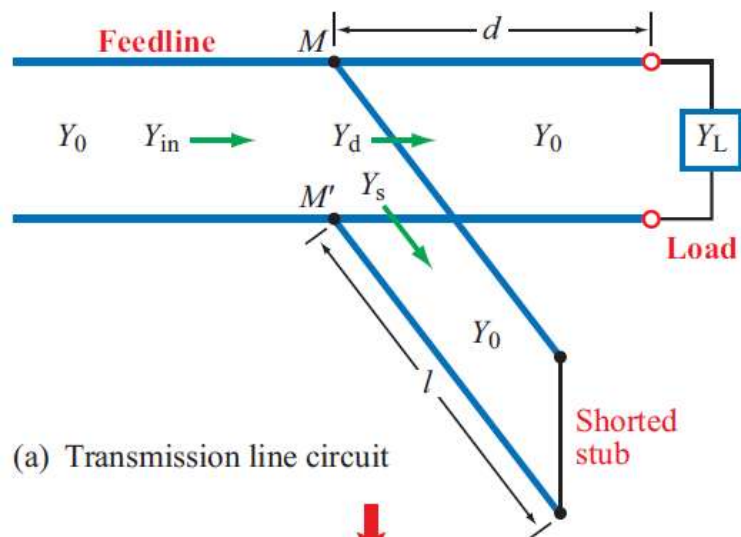Example 2-14: Single-Stub Matching

Repeat Example 2-13, but use a shorted stub (instead of a lumped element) to match the load impedance $Z_L = (25 - j50) \Omega$ to the $50\text{-}\Omega$ transmission line.



(a) Transmission line circuit

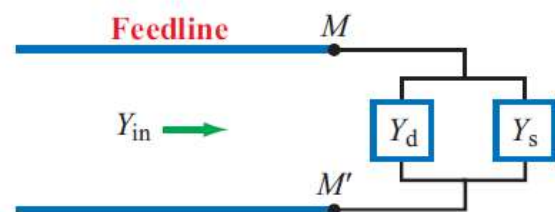


(b) Equivalent circuit





Solution: In Example 2-13, we demonstrated that the load can be matched to the line via either of two solutions:


(1) $d_1 = 0.063\lambda$, and $y_{s1} = jb_{s1} = -j1.58$,

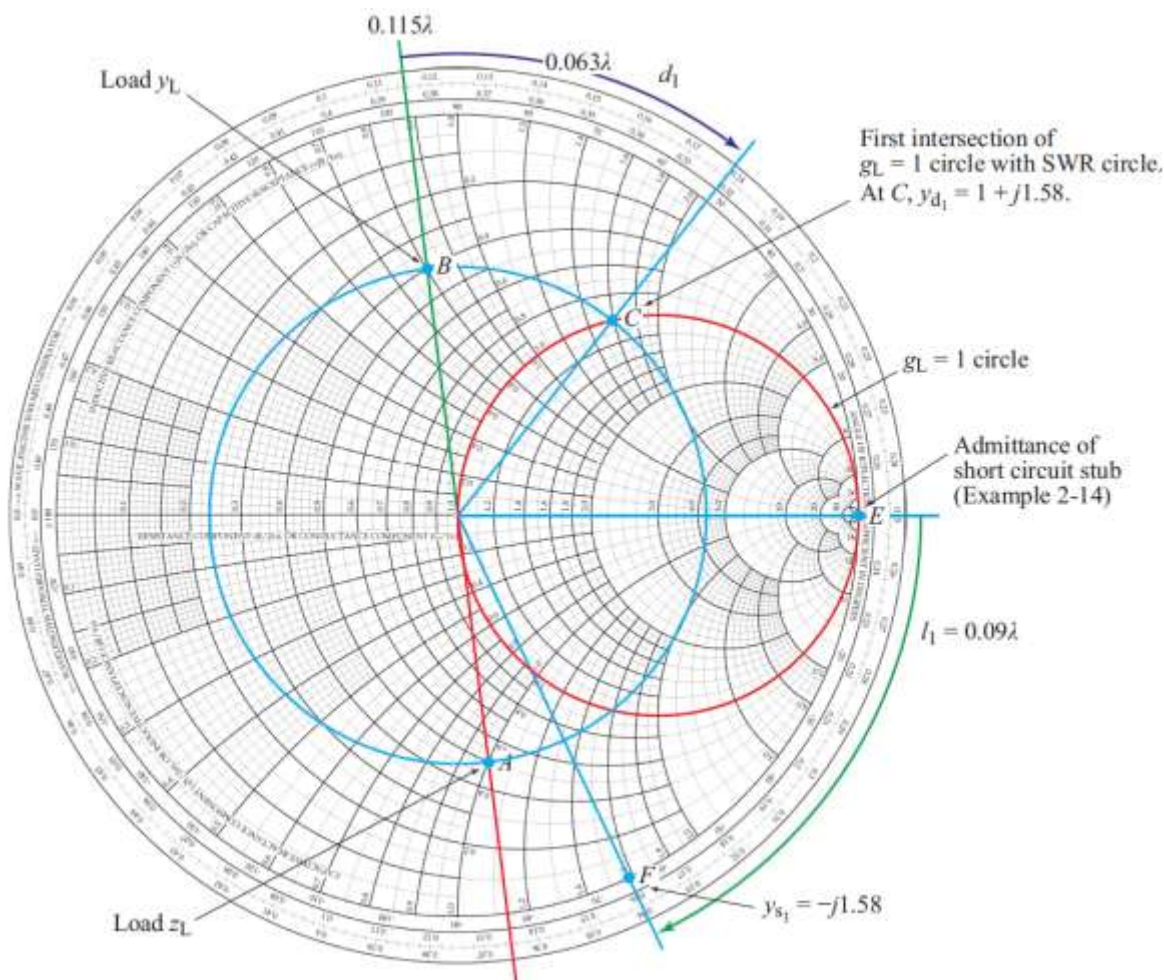(2) $d_2 = 0.207\lambda$, and $y_{s2} = jb_{s2} = j1.58$.



$l_1 = (0.34 - 0.25)\lambda = 0.09\lambda$



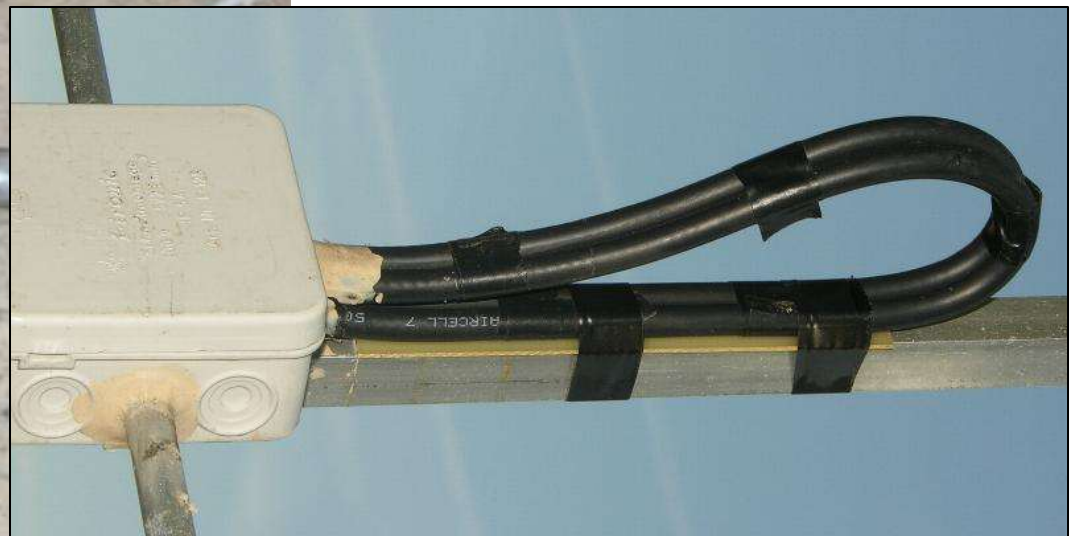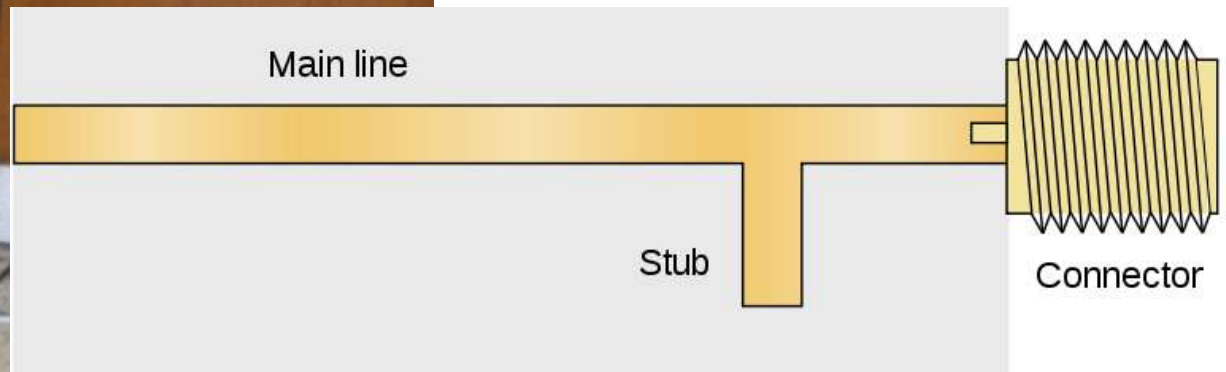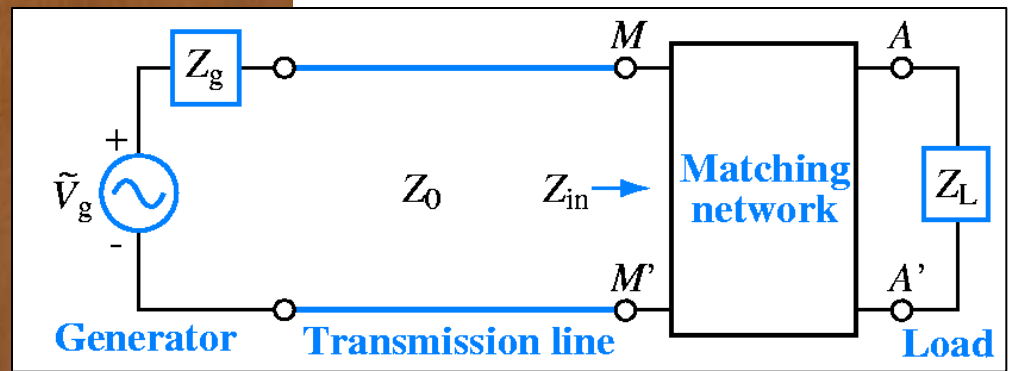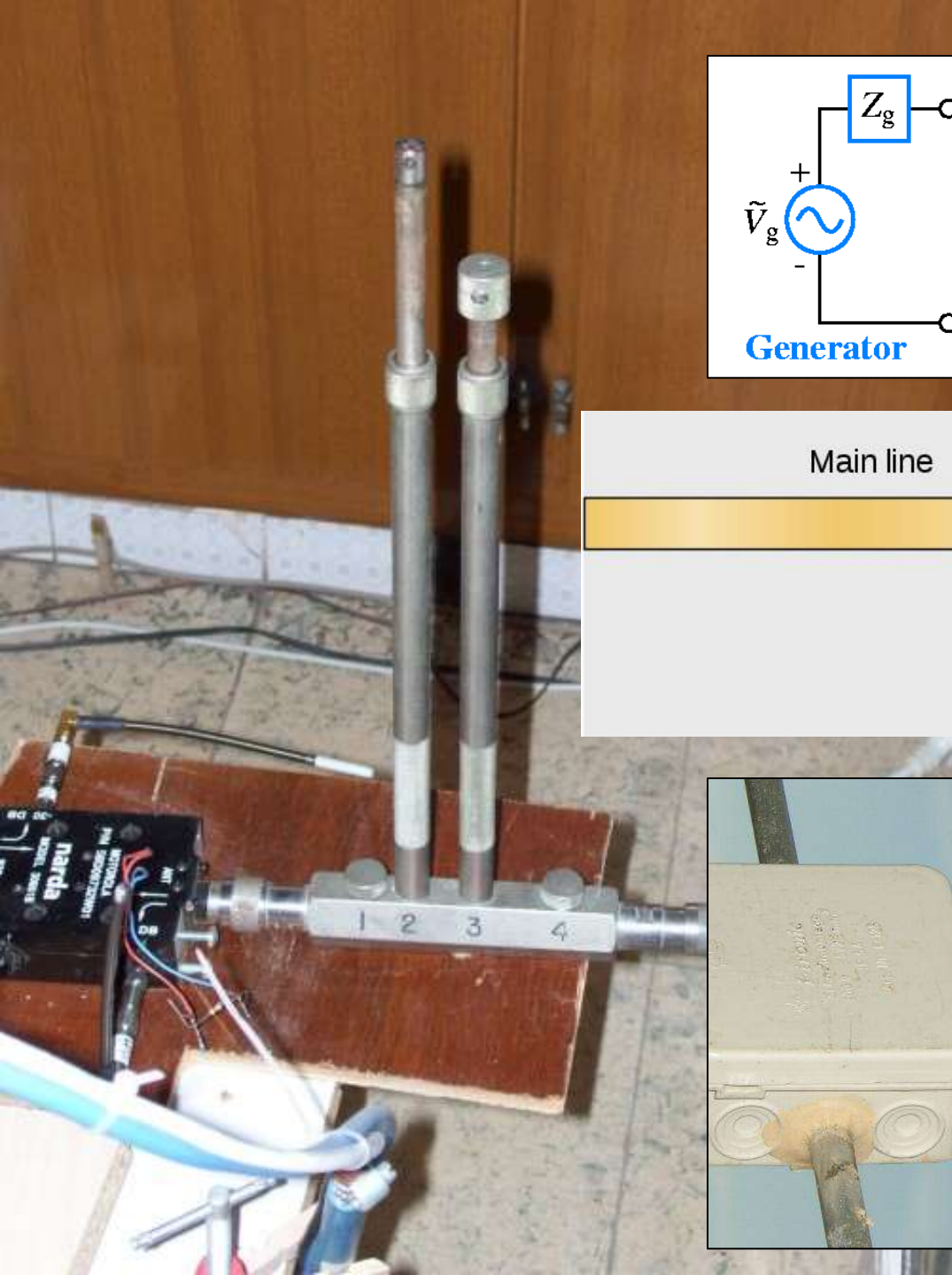


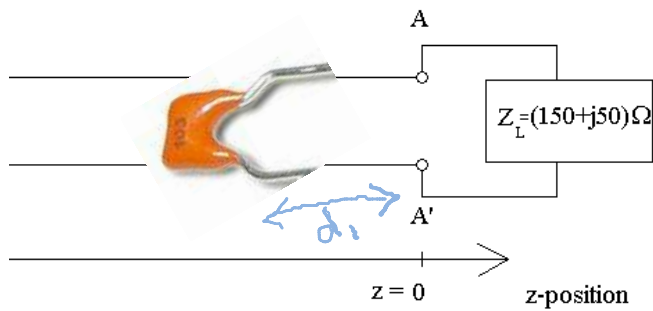


OR

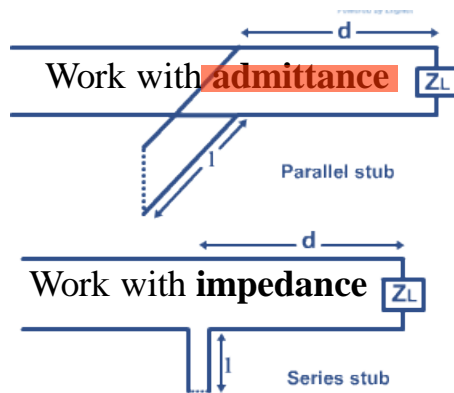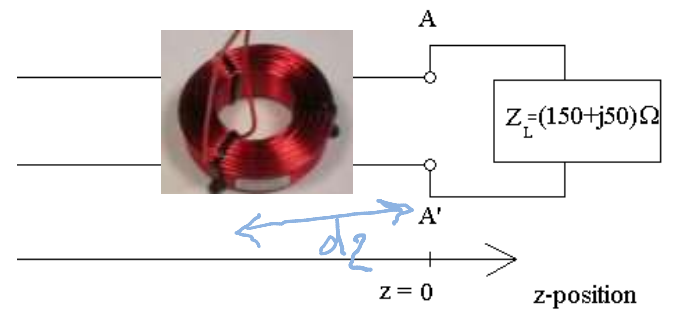


Why isn't this a short ckt.?



Schematic for Single Stub Match

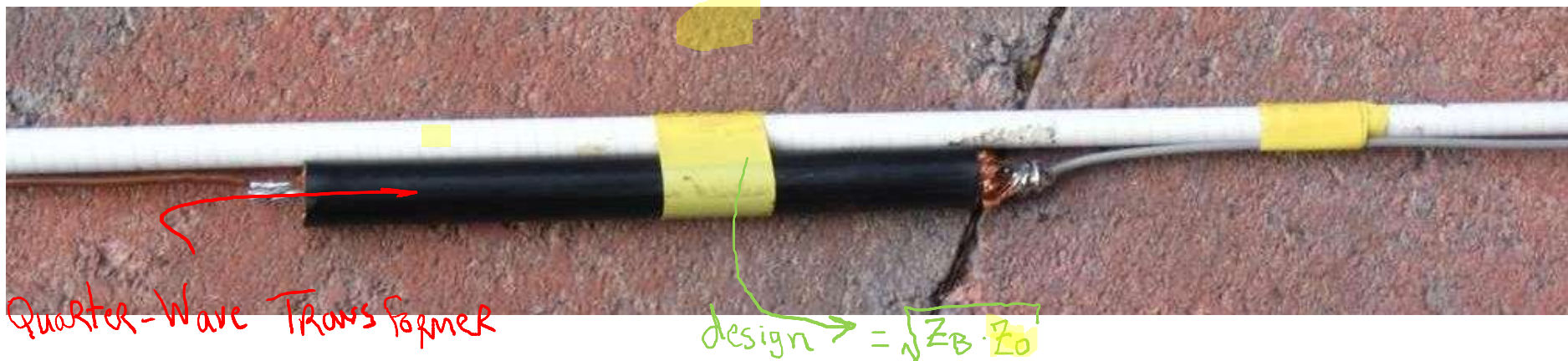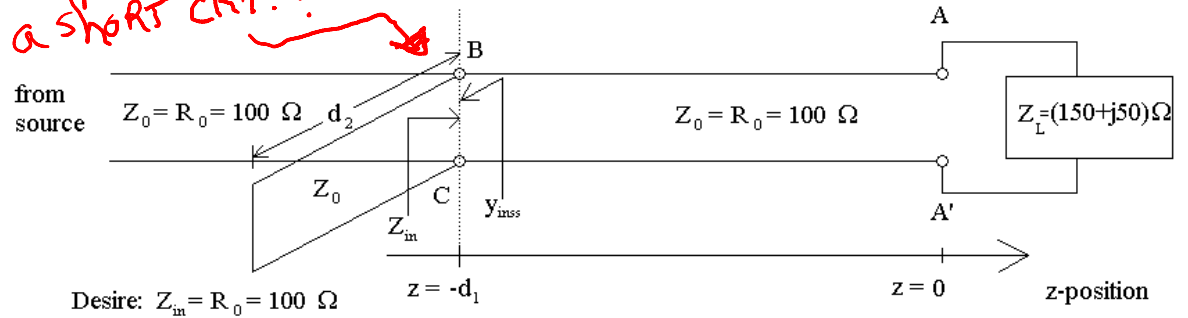

Quarter-Wave Transformer

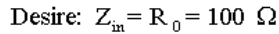from
source

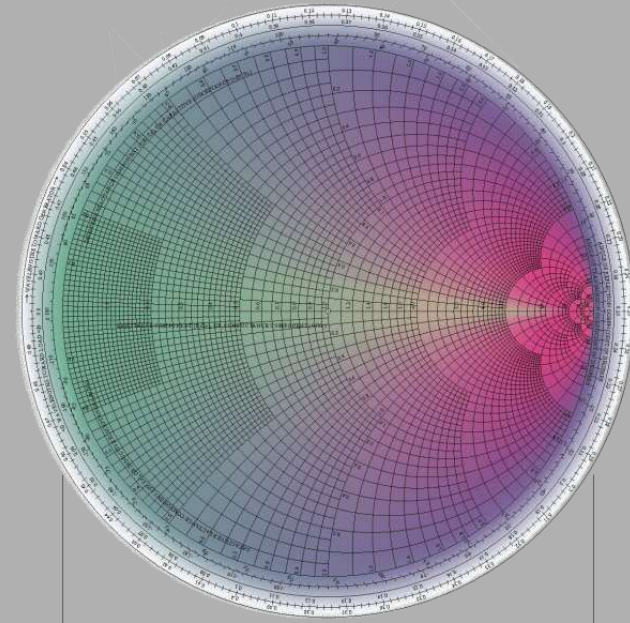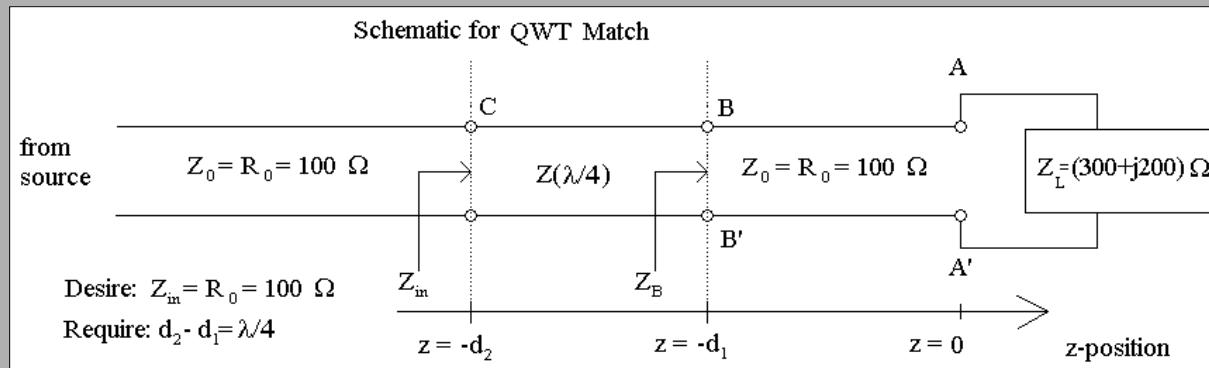- Go down to *narrow-band impedance matching*
- Pay attention to frequency ranges of operation
- Check out broad(er)-band, like tapered lines, etc.



- 1) Normalize load: $z_L = \frac{300 + j200}{100} = 3 + j2$
 - 2) Rotate CW on the $|\Gamma| = 0.63$ ($VSWR = 4.4$) circle to intersect with the horizontal ($x = 0$) midline where $z_B = 4.4 + j0 \Rightarrow z_B = (4.4)(100\Omega) = 440\Omega$
- Note: $z_B = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = VSWR = 4.4$ here!
- Find length: $d_1 = z_B - z_A = (0.250 - 0.224)\lambda = 0.026\lambda$

- 3) Find $Z(\lambda/4)$ for a match with 100Ω line:

$$Z(\lambda/4) = \sqrt{(440\Omega)(100\Omega)} = 210\Omega$$

then re-normalize on the QWT to get $z_B = \frac{z_B}{z(\lambda/4)} = \frac{440\Omega}{210\Omega} = 2.09$



- 4) Rotate CW on the $|\Gamma| = 0.36$ ($VSWR = 2.09$) circle halfway ($\lambda/4$) around the chart to input of the QWT where $z_C = 0.48 + j0$ and $Z_C = (0.48)(210\Omega) = 100.8\Omega$
- 5) Now re-normalize on the $Z_0 = R_0 = 100 \Omega$ line to get

$z_D = 1.0 = VSWR$ at D (we have arrived at HOME for a match!)


<http://www.amanogawa.com/archive/transmissionA.html>

- Go down to *narrow-band impedance matching*
- Pay attention to frequency ranges of operation
- Check out broad(er)-band, like tapered lines, etc.


Transients (on T-Lines)

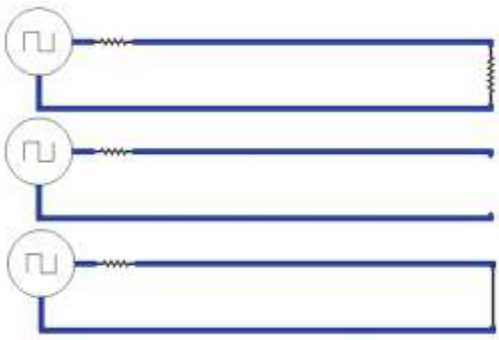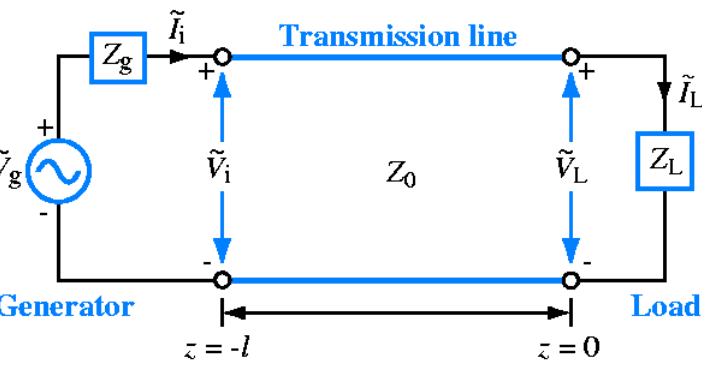

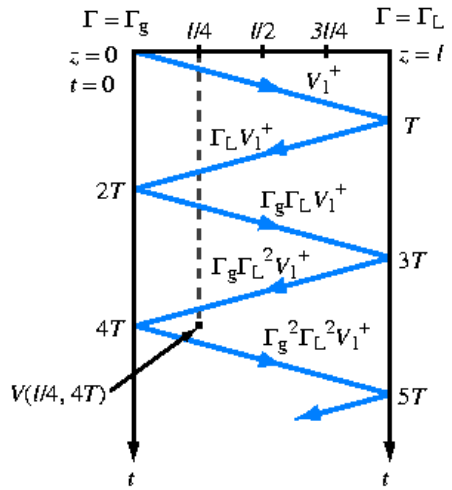
<http://www.amanogawa.com/archive/signalintegrityA.html>



(a) Voltage bounce diagram

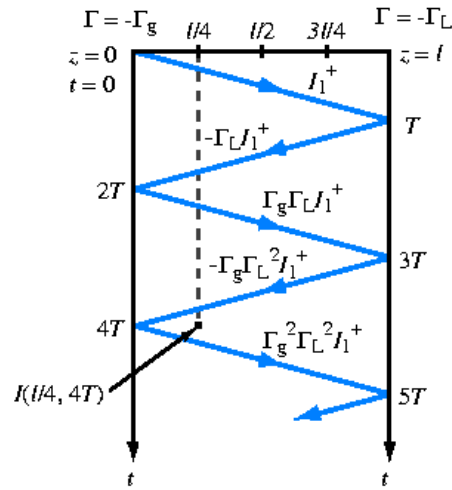


(b) Current bounce diagram

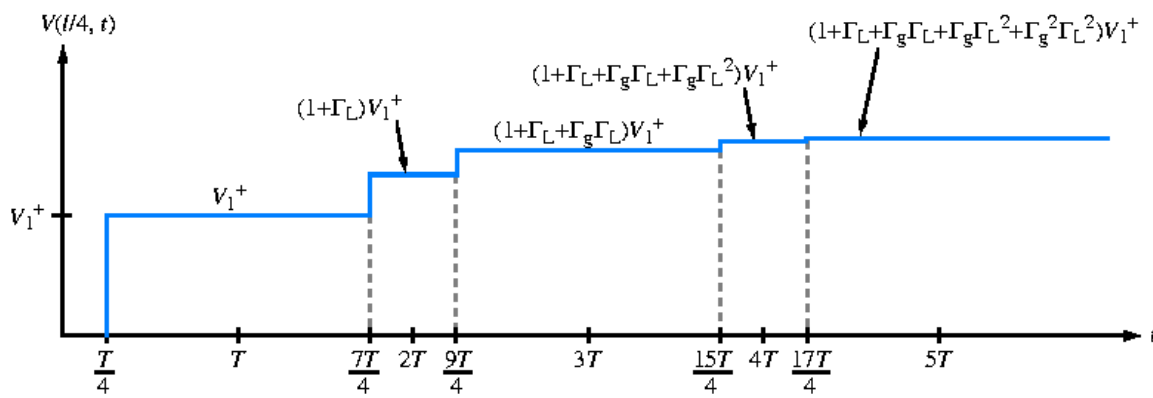

(c) Voltage versus time at $z = l/4$

Resonance

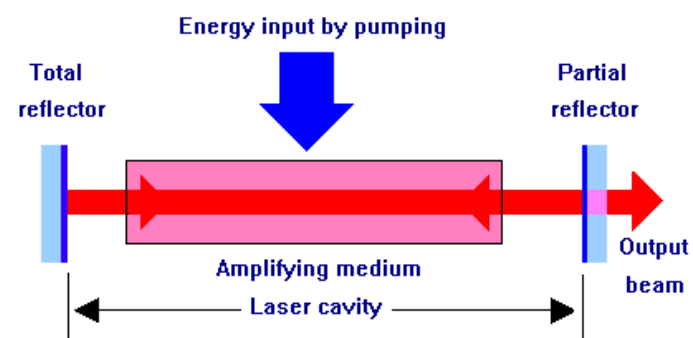

Example 2-15: Pulse Propagation

The transmission-line circuit of Fig. 2-43(a) is excited by a rectangular pulse of duration $\tau = 1$ ns that starts at $t = 0$. Establish the waveform of the voltage response at the load, given that the pulse amplitude is 5 V, the phase velocity is c , and the length of the line is 0.6 m.

Solution: The one-way propagation time is

$$T = \frac{l}{c} = \frac{0.6}{3 \times 10^8} = 2 \text{ ns.}$$




The reflection coefficients at the load and the sending end are

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{150 - 50}{150 + 50} = 0.5,$$


$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{12.5 - 50}{12.5 + 50} = -0.6.$$

By Eq. (2.147), the pulse is treated as the sum of two step functions, one that starts at $t = 0$ with an amplitude $V_{10} = 5$ V and a second one that starts at $t = 1$ ns with an amplitude $V_{20} = -5$ V. Except for the time delay of 1 ns and the sign reversal of all voltage values, the two step functions will generate identical bounce diagrams, as shown in Fig. 2-43(b). For the first step function, the initial voltage is given by
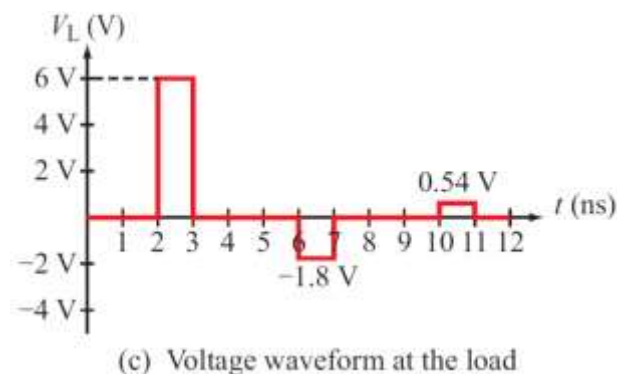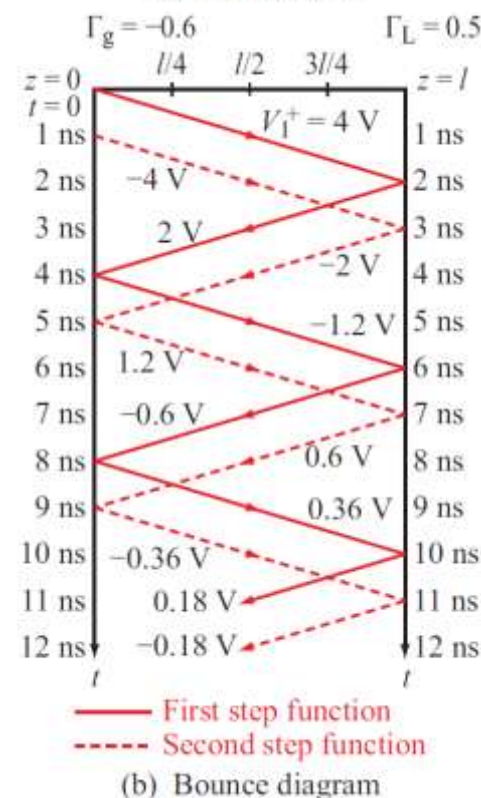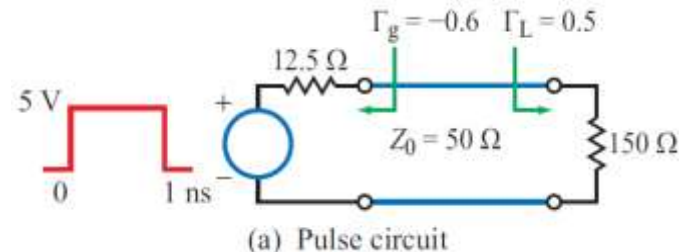
$$V_1^+ = \frac{V_{01} Z_0}{R_g + Z_0} = \frac{5 \times 50}{12.5 + 50} = 4 \text{ V.}$$



Flashback: Lossy Transmission Lines

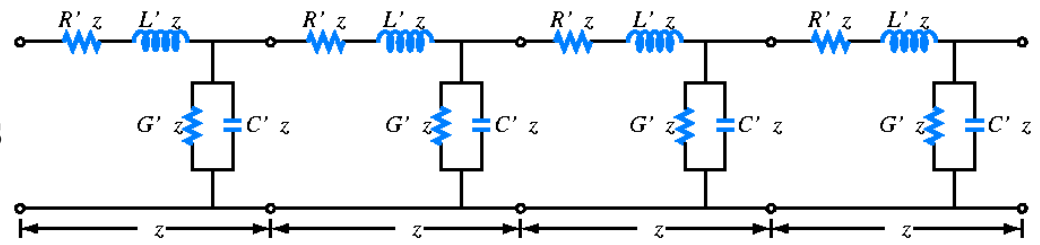

$$\tilde{V}(z) = V_0^+ e^{-\alpha z} e^{-j\beta z} \Rightarrow v(z,t) = V_0^+ e^{-\alpha z} \cos(\omega t - \beta z)$$

$$\gamma \equiv \sqrt{(R' + j\omega L') (G' + j\omega C')} = \alpha + j\beta$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

Note: Lossless was $R' = G' = 0$
 $\Rightarrow \alpha = 0, Z_0 \in \text{Reals}$

Another Special Case Lossy Line, but $\Rightarrow \frac{R'}{L'} = \frac{G'}{C'}$ You design this! (as engineers)



$$\Rightarrow \alpha = R' \sqrt{\frac{C'}{L'}}$$

$$\beta = \omega \sqrt{L' C'}$$

$$\Rightarrow v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L' C'}}$$

$$\text{and } Z_0 = \sqrt{\frac{L'}{C'}}$$

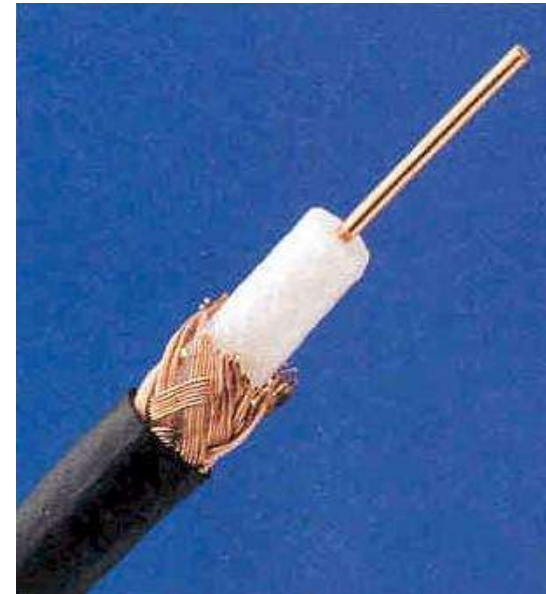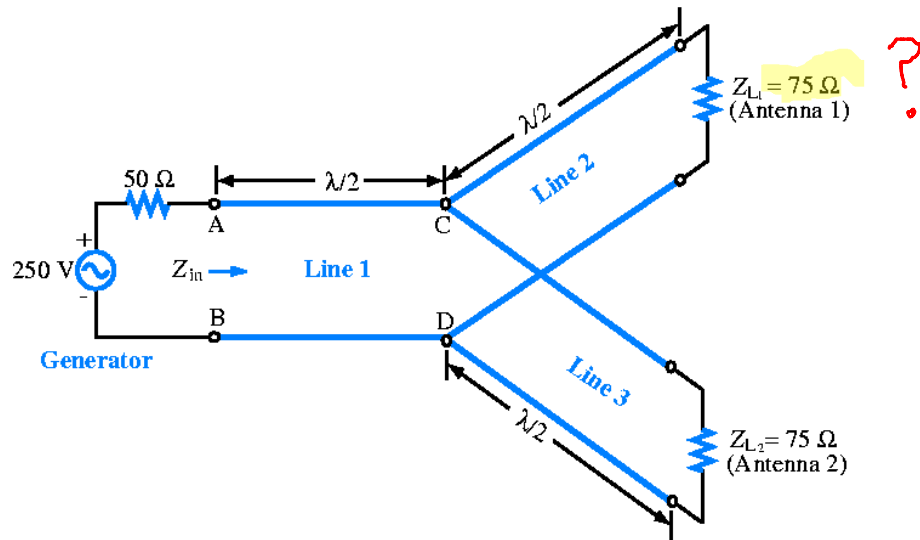So, for this special case,
 α, v_p & Z_0 are not functions of frequency!
 \Rightarrow Distortionless Line




- * Why coax vs. 2 wire???
- * What about multiple wire, various length, single ground plane???
- * Scalar vs. Vectors
...leads into next section (chapter); Vector Analysis!!! ☺

- 2) The phasor voltage on a transmission line is found to be $Ae^{\gamma z}$, where γ is the (complex) propagation constant. What is the voltage in the time domain?

- 3) A given shorted stub behaves like an open circuit at 600 MHz. What is the closest frequency at which it behaves like a short (assuming constant phase speed)?

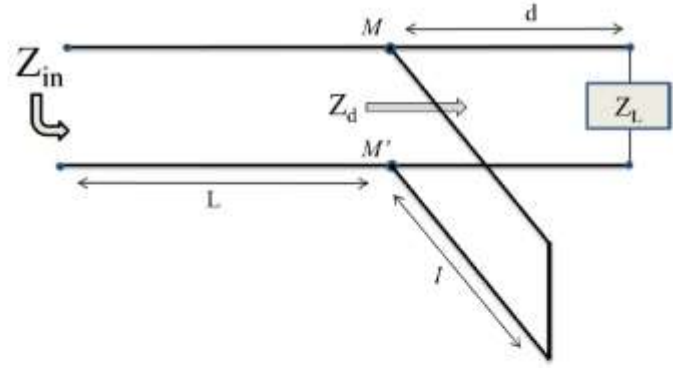4) (20 pts.) A given antenna can be represented by an equivalent load impedance of $100 - j50 \, \Omega$. We need to design a matching network in the configuration shown using lossless T-line ($Z_0=50\Omega$). The wavelength is known to be 100cm.



a) What is the frequency of operation? If you can't specify, can you give me an upper or lower limit?

$f =$ _____

b) Given $d=12.5$ cm, find the impedance looking just into that d -lengthed piece of line terminated by Z_L .

$Z_d =$ _____

c) Given Z_d , find the shortest length (l) of shorted stub that cancels out the reactance at point M .

$l =$ _____

d) Assuming your matching efforts all work, what is the input impedance (Z_{in}) seen by the driving network?

$Z_{in} =$ _____

3) Given a lossless transmission line of known intrinsic impedance, phase speed and length, can you determine the load impedance from measurements of the input impedance? Explain.